


Lecture 5: DC & Transient Response

Outline





- ☐ Pass Transistors
- ☐ DC Response
- ☐ Logic Levels and Noise Margins
- ☐ Transient Response
- ☐ RC Delay Models
- ☐ Delay Estimation

Pass Transistors

- ❑ We have assumed source is grounded
- ❑ What if source > 0 ?
 - e.g. pass transistor passing V_{DD}
- ❑ $V_g = V_{DD}$
 - If $V_s > V_{DD} - V_t$, $V_{gs} < V_t$
 - Hence transistor would turn itself off
- ❑ nMOS pass transistors pull no higher than $V_{DD} - V_{tn}$
 - Called a degraded “1”
 - Approach degraded value slowly (low I_{ds})
- ❑ pMOS pass transistors pull no lower than V_{tp}
- ❑ Transmission gates are needed to pass both 0 and 1

 

Pass Transistor Ckts

    

➤ As the source can rise to within a threshold voltage of the gate, the output of several transistors in series is no more degraded than that of a single transistor

DC Response

□ DC Response: V_{out} vs. V_{in} for a gate

□ Ex: Inverter

– When $V_{in} = 0$ $\rightarrow V_{out} = V_{DD}$

– When $V_{in} = V_{DD}$ $\rightarrow V_{out} = 0$


– In between, V_{out} depends on transistor size and current

– By KCL, must settle such that

$$I_{dsn} = |I_{dsp}|$$

– We could solve equations

 – But graphical solution gives more insight



Transistor Operation



- ❑ Current depends on region of transistor behavior
- ❑ For what V_{in} and V_{out} are nMOS and pMOS in
 - Cutoff?
 - Linear?
 - Saturation?

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

$$\beta = \mu C_{ox} \frac{W}{L}$$

nMOS Operation

| Cutoff | Linear | Saturated |
|-------------|-------------|-------------|
| $V_{gsn} <$ | $V_{gsn} >$ | $V_{gsn} >$ |
| | $V_{dsn} <$ | $V_{dsn} >$ |

  



pMOS Operation

| Cutoff | Linear | Saturated |
|--|---|---|
| $V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$ | $V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$ | $V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$ |

$$V_{tp} < 0$$


$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{dsp} = V_{out} - V_{DD}$$

 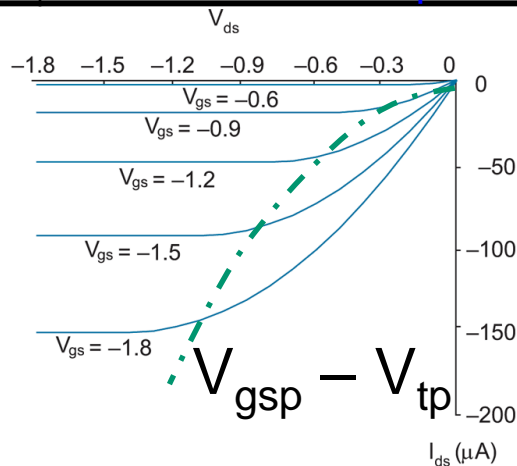


I-V Characteristics

 - ❑ Make pMOS is wider than nMOS such that $\beta_n = \beta_p$




Current vs. V_{out} , V_{in}

$$V_{gsp} = V_{in} - V_{DD}$$

 


Load Line Analysis

- For a given V_{in} :
 - Plot I_{dsn} , I_{dsp} vs. V_{out}
 - V_{out} must be where |currents| are equal in


 


Load Line Analysis

 

DC Transfer Curve

 
 
□ Transcribe points onto V_{in} vs. V_{out} plot



Operating Regions

□ Revisit transistor operating regions


| Region | nMOS | pMOS |
|--------|------|------|
| A | | |
| B | | |
| C | | |
| D | | |
| E | | |

  

| Summary of CMOS inverter operation | | | | |
|------------------------------------|--|-----------|-----------|-------------------------|
| Region | Condition | p-device | n-device | Output |
| A | $0 \leq V_{in} < V_{tn}$ | linear | cutoff | $V_{out} = V_{DD}$ |
| B | $V_{tn} \leq V_{in} < V_{DD}/2$ | linear | saturated | $V_{out} > V_{DD}/2$ |
| C | $V_{in} = V_{DD}/2$ | saturated | saturated | V_{out} drops sharply |
| D | $V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $ | saturated | linear | $V_{out} < V_{DD}/2$ |
| E | $V_{in} > V_{DD} - V_{tp} $ | cutoff | linear | $V_{out} = 0$ |


Beta Ratio

 - ❑ If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- ❑ Called *skewed gate*
- ❑ Other gates: collapse into equivalent inverter




Noise Margins

 - How much noise can a gate input see before it does not recognize the input?




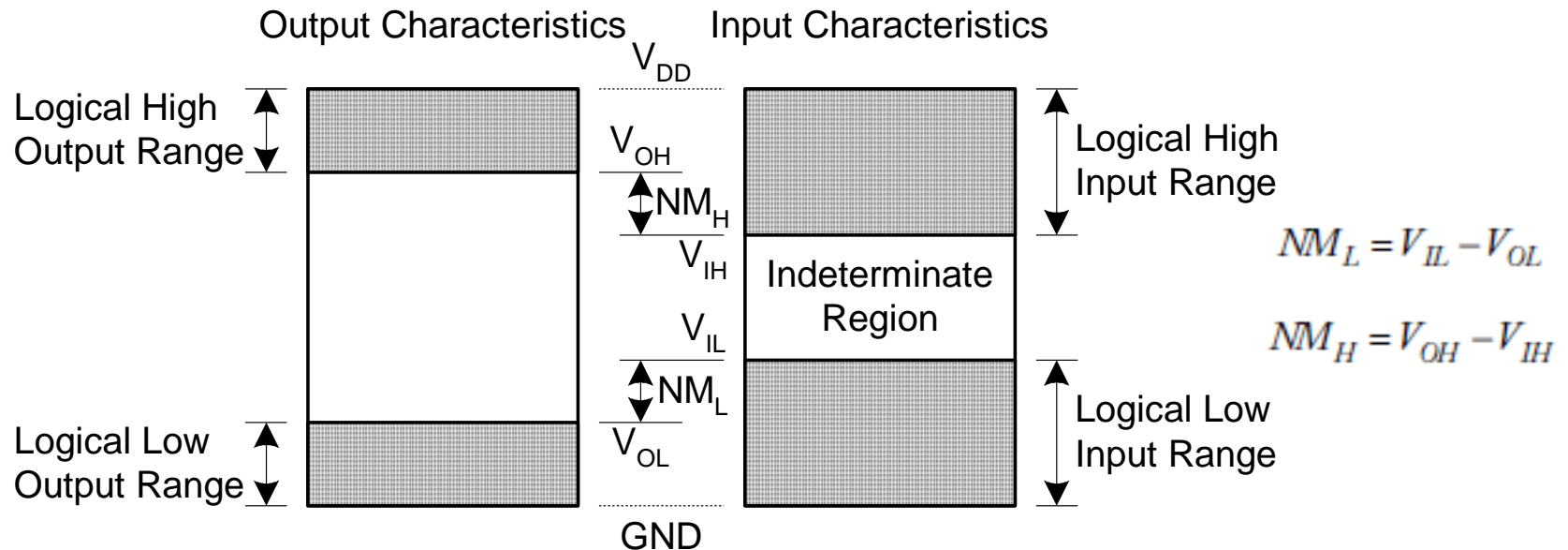V_{IH} = minimum HIGH input voltage
 V_{IL} = maximum LOW input voltage
 V_{OH} = minimum HIGH output voltage
 V_{OL} = maximum LOW output voltage



Logic Levels

 - ❑ To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristic



$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

where



V_{IH} = minimum HIGH input voltage

V_{IL} = maximum LOW input voltage

V_{OH} = minimum HIGH output voltage



V_{OL} = maximum LOW output voltage

  What is the impact of altering the PMOS width in comparison to the NMOS width on the DC char?



$$I_{DS} = \mu_p \frac{\epsilon_{ox} W}{t_{ox} L} (V_{gs} - V_t)^2$$

  If we increase (d) the width of PMOS compared to NMOS
 → for the same input voltage, a higher (I) output voltage is obtained




Impact of *skewing* transistor sizes on inverter noise margins

$$I_{dn} = \frac{\beta_n}{2} (V_{inv} - V_{tn})^2$$

$$I_{dp} = \frac{\beta_p}{2} (V_{inv} - V_{DD} - V_{tp})^2$$

 
$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}}$$



- Increasing (decreasing) PMOS width to NMOS width increases (decreases) the low noise margin and decreases (increases) the high noise margin

Transient Response

 - ❑ *DC analysis* tells us V_{out} if V_{in} is constant
- ❑ *Transient analysis* tells us $V_{out}(t)$ if $V_{in}(t)$ changes
 - Requires solving differential equations
- ❑ Input is usually considered to be a step or ramp
 - From 0 to V_{DD} or vice versa



$$I = C \frac{dV}{dt}$$


Inverter Step Response

□ Ex: find step response of inverter driving load cap

$$V_{in}(t) =$$

$$V_{out}(t < t_0) =$$


$$\frac{dV_{out}(t)}{dt} =$$

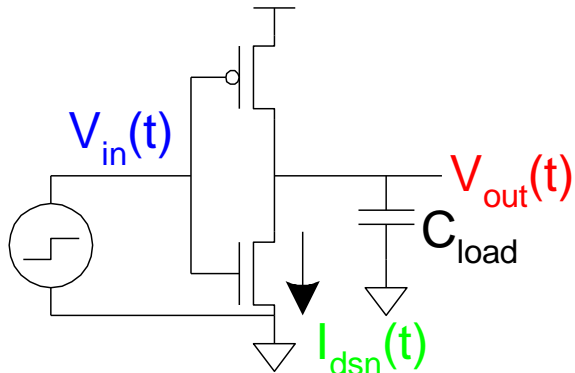

$$I_{dsn}(t) = \begin{cases} & t \leq t_0 \\ V_{out} > V_{DD} - V_t \\ V_{out} < V_{DD} - V_t \end{cases}$$


Delay Definitions

- ❑ t_{pdr} : *rising propagation delay*
 - From input to rising output crossing $V_{DD}/2$
- ❑ t_{pdf} : *falling propagation delay*
 - From input to falling output crossing $V_{DD}/2$
- ❑ t_{pd} : *average propagation delay*
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- ❑ t_r : *rise time*
 - From output crossing 0.2 V_{DD} to 0.8 V_{DD}
- ❑ t_f : *fall time*
 - From output crossing 0.8 V_{DD} to 0.2 V_{DD}

 


Delay Definitions

 - ❑ t_{cdr} : *rising contamination delay*
 - From input to rising output crossing $V_{DD}/2$
- ❑ t_{cdf} : *falling contamination delay*
 - From input to falling output crossing $V_{DD}/2$
- ❑ t_{cd} : *average contamination delay*
 - $t_{pd} = (t_{cdr} + t_{cdf})/2$




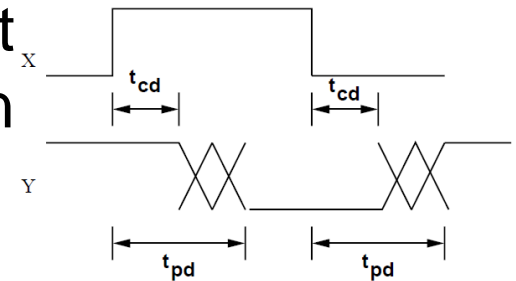When input changes the output maintains its old value for a duration called the contamination time
max-time and *min-time*



Simulated Inverter Delay

 - ❑ Solving differential equations by hand is too hard
- ❑ SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too!
- ❑ But simulations take time to write, may hide insight



Delay Estimation

- ❑ We would like to be able to easily estimate delay
 - Not as accurate as simulation
 - But easier to ask “What if?”
- ❑ The step response usually looks like a 1st order RC response with a decaying exponential.
- ❑ Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use *effective resistance* R
 - So that $t_{pd} = RC$
- ❑ Characterize transistors by finding their effective R
 - Depends on average current as gate switches

Effective Resistance

- ❑ Shockley models have limited value
 - Not accurate enough for modern transistors
 - Too complicated for much hand analysis
- ❑ Simplification: treat transistor as resistor
 - Replace $I_{ds}(V_{ds}, V_{gs})$ with effective resistance R
 - $I_{ds} = V_{ds}/R$
 - R averaged across switching of digital gate
- ❑ Too inaccurate to predict current at any given time
 - But good enough to predict RC delay

Transistor resistance

$$R = \frac{\partial I_{ds}}{\partial V_{ds}}^{-1}$$

In the linear region



$$I_{ds} \approx \beta(V_{gs} - V_t)V_{ds}$$

$$\rightarrow R \approx \frac{1}{\beta(V_{gs} - V_t)} = \frac{1}{\mu C_{ox}} \frac{L}{W} \frac{1}{(V_{gs} - V_t)}$$

- ❑ Not accurate, but at least shows that the resistance is proportional to L/W and decreases with V_{gs}
- ❑ If R/C are for a unit size transistor then a transistor of K unit width has KC capacitance and R/K resistance
- ❑ The resistance of a PMOS transistor = $2\times$ resistance of NMOS transistor of the same size

RC Delay Model

  - ❑ Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- ❑ Capacitance proportional to width
- ❑ Resistance inversely proportional to width



RC Values

❑ Capacitance

- $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$ of gate width in $0.6 \mu\text{m}$
- Gradually decline to $1 \text{ fF}/\mu\text{m}$ in 65 nm

❑ Resistance $\rightarrow R \approx \frac{1}{\beta(V_{gs}-V_t)} = \frac{1}{\mu C_{ox}} \frac{L}{W} \frac{1}{(V_{gs}-V_t)}$


- $R \approx 10 \text{ K}\Omega \cdot \mu\text{m}$ in $0.6 \mu\text{m}$ process
- Improves with shorter channel lengths
- $1.25 \text{ K}\Omega \cdot \mu\text{m}$ in 65 nm process

❑ Unit transistors

- May refer to minimum contacted device ($4/2 \lambda$)
- Or maybe $1 \mu\text{m}$ wide device
- Doesn't matter as long as you are consistent

Inverter Delay Estimate


 
- Estimate the delay of a fanout-of-1 inverter



$$d = 6RC$$

If the input A rises, the nMOS transistor will be ON and the pMOS OFF

Transient Response(I)

  


$$V_{out}(t) = V_{DD}e^{-t/RC}$$

$$t_{pd} = RC \ln 2 \approx 0.69 RC$$

$$\tau = RC$$

$$t_{pd} = RC$$


Transient Response(II)

 


$$V_{out}(t) = V_{pulse} \left(1 - e^{-t/RC} \right)$$

$$t_{pd} = RC \ln 2 \approx 0.69 RC$$

Delay Model Comparison

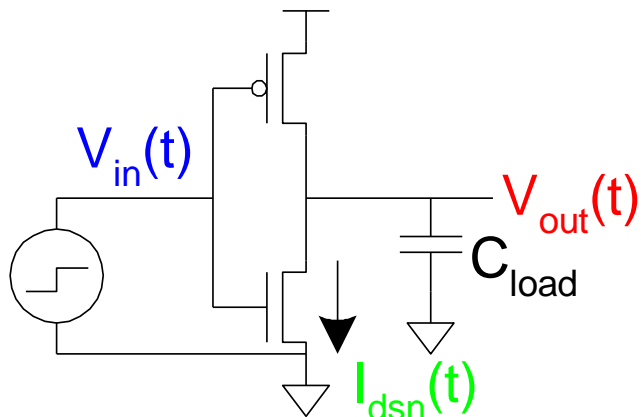


 $C_{load} = 20 \text{ fF}$
 $V_{DD} = 1.0 \text{ V}$
 $V_t = 0.3 \text{ V}$
 $t_{ox} = 10.5 \text{ \AA}$
 $\mu = 80 \text{ cm}^2/\text{V} \cdot \text{s}$



 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).



3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




Elmore Delay

- ❑ ON transistors look like resistors
- ❑ Pullup or pulldown network modeled as *RC ladder*
- ❑ Elmore delay of RC ladder




$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$




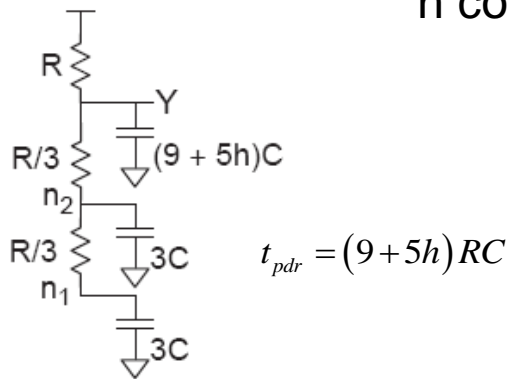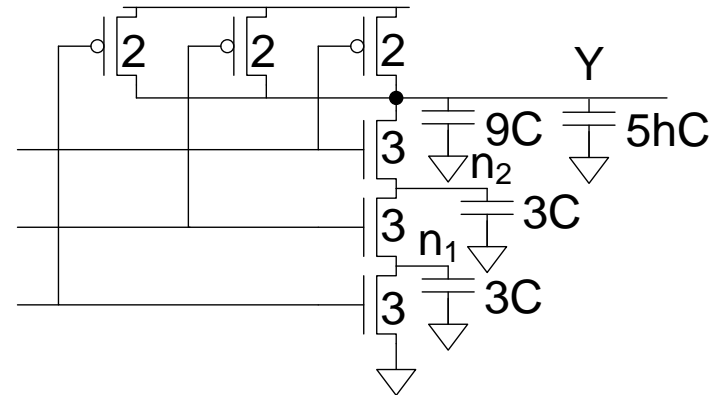 Example: 3-input NAND

- Estimate worst-case rising and falling delay of 3-input NAND driving h identical gates.



Rising

 

Falling



$$t_{pdf} = (3C)\left(\frac{R}{3}\right) + (3C)\left(\frac{R}{3} + \frac{R}{3}\right) + [(9 + 5h)C]\left(\frac{R}{3} + \frac{R}{3} + \frac{R}{3}\right) = (12 + 5h)RC$$

Delay Components

- ❑ Delay has two parts
 - *Parasitic delay*
 - 9 or 12 RC
 - Independent of load
 - *Effort delay*
 - 5h RC
 - Proportional to load capacitance

Contamination Delay

 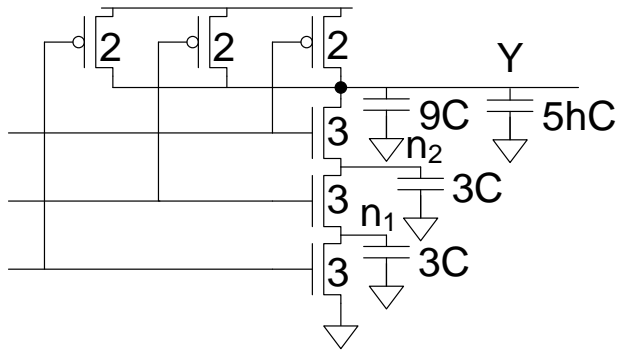
- ❑ Best-case (contamination) delay can be substantially less than propagation delay.
- ❑ Ex: If all three inputs fall simultaneously



$$t_{cdr} = \left[(9 + 5h)C \right] \left(\frac{R}{3} \right) = \left(3 + \frac{5}{3}h \right) RC$$

Diffusion Capacitance

 - ❑ We assumed contacted diffusion on every s / d.
- ❑ Good layout minimizes diffusion area
- ❑ Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by $2C$
 - Merged uncontacted diffusion might help too



Layout Comparison

❑ Which layout is better?

