

# Learning Outcomes

---

## ➤ **Small signal analysis and transistor biasing**

- Apply small signal models to the solution of complex circuits (e.g. cascodes, current conveyors), including pole-zero calculations;
- Design circuits to bias transistors in the correct operating regime;

## ➤ **Fundamental circuit design blocks and their performance**

- Perform analyses for fundamental circuit blocks, including **current mirrors** (for low-voltage, wide swing application), amplifiers (2 stage folded cascode, source degeneration etc.), bandgap references, **switched capacitor networks**, **Gm-C filters**, and drivers;
- Evaluate the benefits of specific circuit blocks to design solutions, given a range of non-orthogonal system specifications;
- **Frequency Response**

## ➤ **Analog-to-Digital Conversion(ADC) and Digital-to-Analog Conversion(DAC)**

## ➤ **Layout design**

---

# Learning Outcomes

BEHZAD  
RAZAVI


Fundamentals of Microelectronics



SECOND EDITION

WILEY

 
**Fundamental of Microelectronics**  
**Behzad Razavi**  
**2<sup>nd</sup> Edition**



**Design of Analog CMOS**  
**Integrated Circuits**  
**Behzad Razavi**  
**2<sup>nd</sup> Edition**

# IC Design Overview
 
## Global Integrated Circuit (IC) design Market



Mostly Silicon (CMOS) based devices


Source:  
Forbes, IC Insights  
<http://blogs-images.forbes.com/greatspeculations/files/2015/09/loT-PWC-Gartner-Graphic1.png>

Cray-2 Supercomputer






# Why Analog

---

 


- Real-world signals are analog: continuous in amplitude, and continuous in time.
- Modern signal processing has evolved to be digital or discrete-time. Most signal processing is performed in the digital domain.
- Most analog systems perform the sensing, amplification, transmission and reception of *real-world* signals, before they can be processed by digital systems.

# Why Analog?

 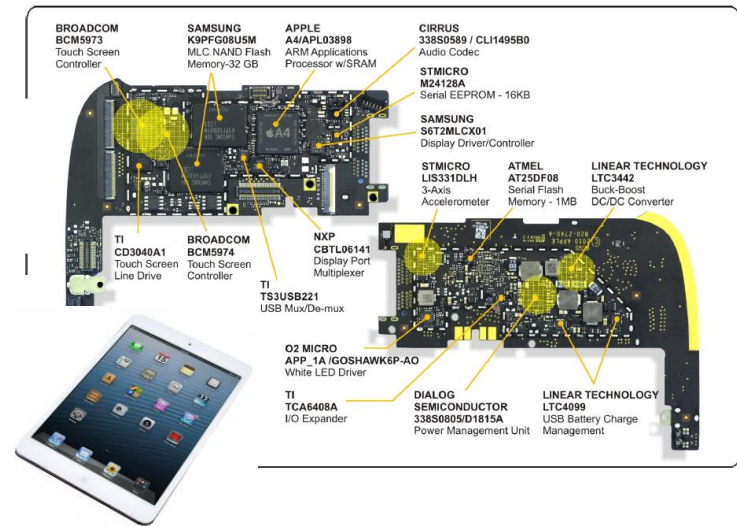 

# Moor's law and analog design


## Moore's Law and Beyond

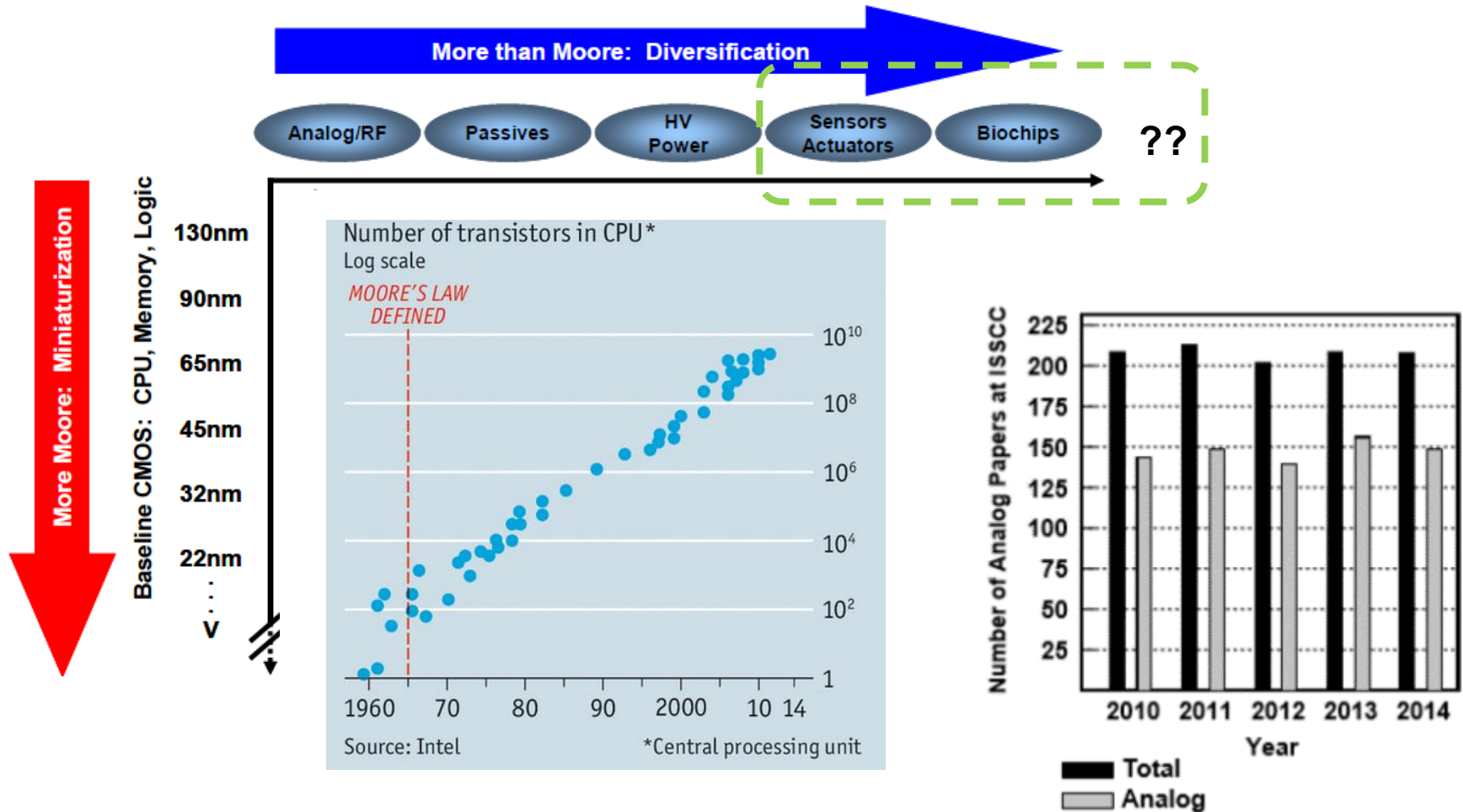


 
# A little history


- ... vacuum tubes, discrete components
- 1947: First integrated transistor
- 1953: Sonotone (hearing aid) contained 5 transistors
- 1950s: Fairchild, Texas instruments
- 1958: First Integrated circuits
- 1960s: MOS became popular
- 1965: Moore's Law ...




Used even  
in 1960s!



William Shockley,  
John Bardeen and  
Walter H. Brattain



 


First IC  
(Fairchild)

 

MOS IC  
(Intel)


# A little history

   

**William Shockley,  
John Bardeen and  
Walter H. Brattain**



 From lot's of Quantum mechanics to few simple equations



**Carver Mead  
Lyn Conway**




Formal rules  
of IC design




# Transistor Abstraction


Device

 


Circuit

 

Architecture



 


System

 


- Switching between levels of abstraction is necessary for
  - understanding the details of operation.
  - optimizing the overall performance.
- Interaction between all groups in industry is essential for high performance and low cost designs.

# Basic semiconductor devices

   





# Diode

 




Forward Bias




Reverse Bias

    



# Diode: Real

   

# Transistor

 


# Transistor

  





# Transistor

 

# Transistor

 


# Transistor

 


- As  $V_G$  increases from zero, holes in  $p$ -substrate are repelled leaving negative ions behind to form a depletion region.
- There are no charge carriers, so no current flow.

# Transistor

 


- Increasing  $V_G$  further increases the width of the depletion region and the potential at the oxide-silicon interface.
- Structure resembles voltage divider consisting of gate-oxide capacitor and depletion region capacitor in series.

# Transistor

 


- When interface potential reaches sufficiently positive value, electrons flow from the source to the interface and eventually to the drain.
- This creates a channel of charge carriers (inversion layer) beneath the gate oxide.
- The value of  $V_G$  at which the inversion layer occurs is the threshold voltage ( $V_{TH}$ ).

# Transistor: NMOS

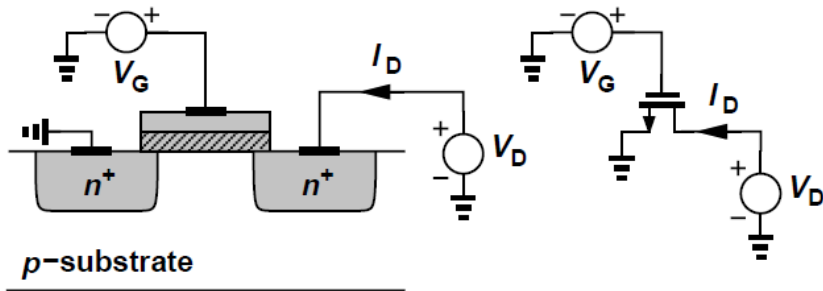


(a)

 


(b)
 
$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$



(c)

Deep triode region

 


(d)


$$V_{DS} \ll 2(V_{GS} - V_{TH}),$$

$$I_D \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) V_{DS}$$
 
$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$




 - overdrive voltage:  $V_{GS} - V_{TH}$
- With the condition,  $V_{DS} \ll 2(V_{GS} - V_{TH})$ , we say the device operates in the deep triode region.






# Transistor Switch


 


$$R_{eq} = \text{average}_{t=t_1 \dots t_2} (R_{on}(t)) = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} R_{on}(t) dt$$
$$\approx \frac{1}{2} (R_{on}(t_1) + R_{on}(t_2))$$

# Transistor Switch



 

  
$$\approx \frac{1}{2}(R_{on}(t_1) + R_{on}(t_2))$$



$$R_{eq} = \frac{1}{2} \left( \frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{5}{6} \lambda V_{DD} \right)$$




# Inverter

   

$$\begin{aligned} V_{out} &= V_{DD} - I_D R_D \\ &= V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})^2, \end{aligned}$$

$$\begin{aligned} V_{out,min} &= V_{DD} - R_D I_{D,max} \\ &= V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D [2(V_{DD} - V_{TH}) V_{out,min} - V_{out,min}^2]. \end{aligned}$$

# Inverter




 
 
 


$$\begin{aligned} V_{out} &= V_{DD} - I_D R_D \\ &= V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})^2, \end{aligned}$$



$$\begin{aligned} V_{out,min} &= V_{DD} - R_D I_{D,max} \\ &= V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D [2(V_{DD} - V_{TH}) V_{out,min} - V_{out,min}^2]. \end{aligned}$$

$$V_{out,min} \approx - \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH})}.$$



# Inverter

      

# Inverter

  





**Infinite Transition Region Gain**

  



**Finite Transition Region Gain**



# Inverter

   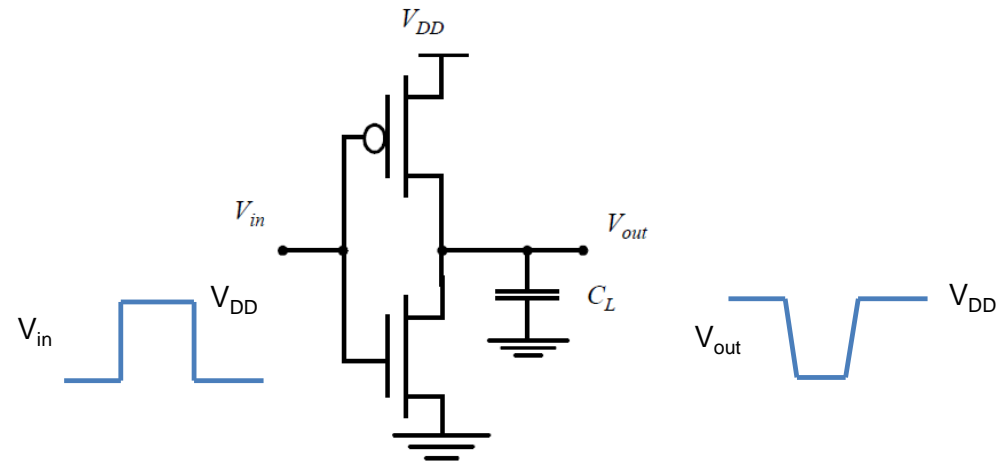

# Inverter VTC

  

$$I_{sat} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$I_{DSp} = -I_{DSn}$$

$$V_{GSn} = V_{in} ; V_{GSp} = V_{in} - V_{DD}$$

$$V_{DSn} = V_{out} ; V_{DSp} = V_{out} - V_{DD}$$

$$I_{DN} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$

$$I_{DP} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} ((V_{in} - V_{DD}) - V_{TH})^2$$

# Inverter VTC

Voltage Transfer Characteristics(VTC) of CMOS Inverter


$$V_{\text{inv}} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}}$$

$$V_{\text{inv}} = \frac{V_{DD} + V_{tp} + V_{tn} \frac{1}{r}}{1 + \frac{1}{r}}$$



Including velocity saturation

$$\beta = \frac{1}{2} \mu C_{ox} \frac{W}{L}$$

$$r = \beta_p / \beta_n$$

 

# Inverter VTC


 
 


Reducing  $V_{DD}$  improves gain.... but up to a certain limit



# Inverter Noise Margin

$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

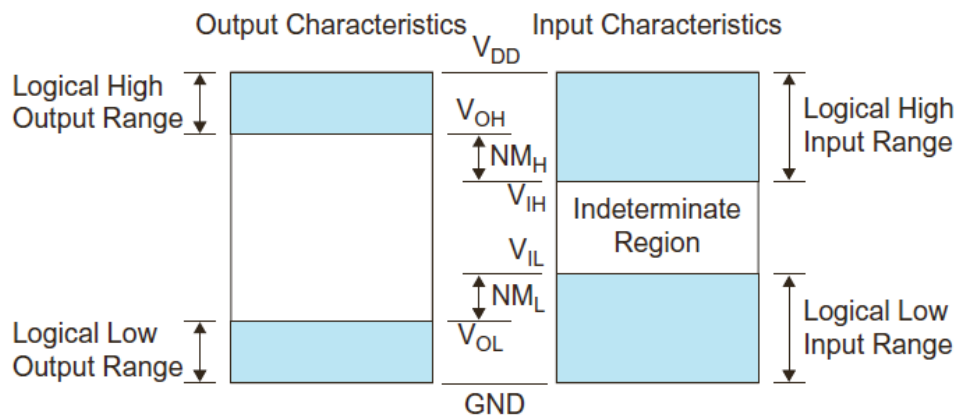  


# Inverter Power

  

$$\begin{aligned} P_{total} &= P_{dyn} + P_{stat} \\ &= P_{tran} + P_{sc} + P_{stat} \end{aligned}$$



# Inverter Power

 


$$\begin{aligned} E_{VDD} &= \int_0^{\infty} i_{VDD}(t) V_{DD} dt = V_{DD} \int_0^{\infty} C_L \frac{dv_{out}}{dt} dt \\ &= C_L V_{DD} \int_0^{V_{DD}} dv_{out} = C_L V_{DD}^2 \end{aligned}$$

$$E_C = \int_0^{\infty} i_{VDD}(t) v_{out} dt = \int_0^{\infty} C_L \frac{dv_{out}}{dt} v_{out} dt = C_L \int_0^{V_{DD}} v_{out} dv_{out} = \frac{C_L V_{DD}^2}{2}$$

$$P_{dyn} = C_L V_{DD}^2 f_{0 \rightarrow 1}$$

Voltage scaling is the most popular

# Inverter Delay

 

$$C_{lumped} \frac{dV_{out}}{dt} + \frac{V_{out} - V_{in}}{R_{driver}} = 0 \quad V_{out}(t) = (1 - e^{-t/\tau}) V$$




$$t = \ln(2)\tau = 0.69\tau$$

Time needed to rise 50% of final value

# Inverter Delay

$$t_{pHL} = \ln(2)R_{eqn}C_L = 0.69R_{eqn}C_L$$



$$t_{pLH} = 0.69R_{eqp}C_L$$

   

$$t_p = \frac{t_{pLH} + t_{pHL}}{2}$$

# Inverter Delay

Ring Oscillator

  


$$T = 2 \times t_p \times N$$

# Analog again!

---


# Current Source

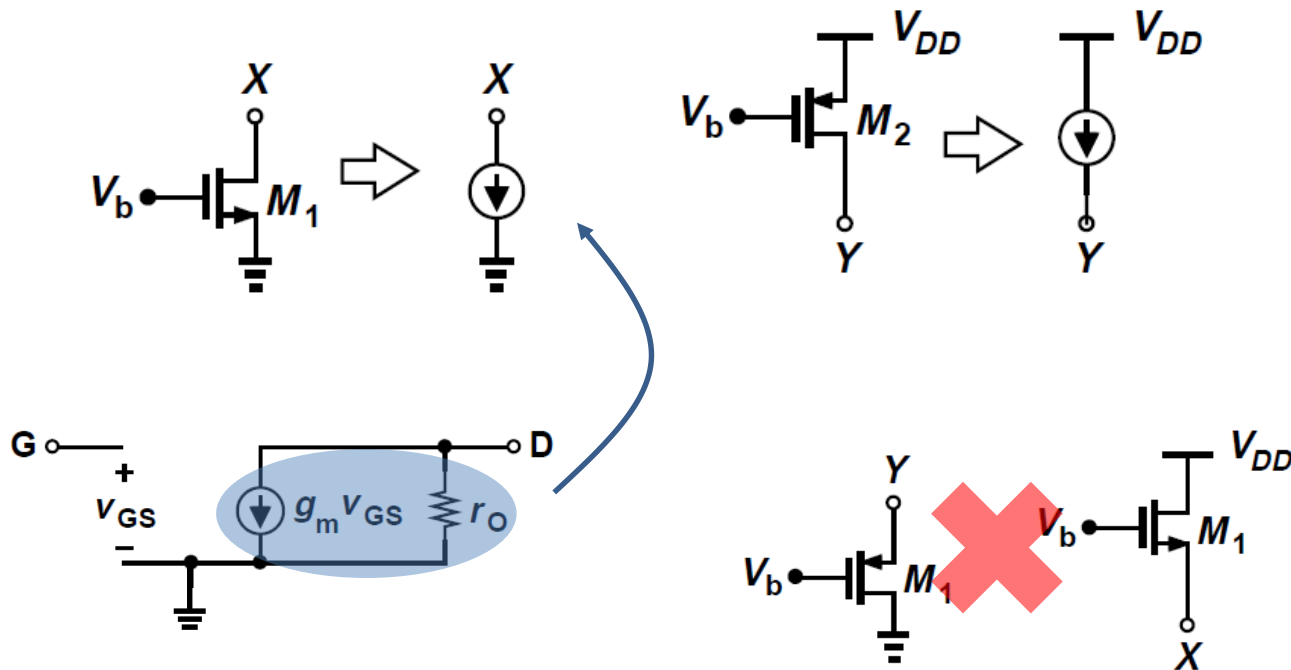

- Do not operate as current sources because variation of  $V_x$  or  $V_y$  directly changes the gate-source voltage of each transistor, thus changing the drain current considerably
 
# Small signal models

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$






$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \quad [\text{in saturation}]$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$


$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$

   

- $g_m$  represents the sensitivity of the device: for a high  $g_m$ , a small change in  $V_{GS}$  results in a large change in  $I_D$ .

# Small signal models

 

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$r_O = \frac{\partial V_{DS}}{\partial I_D}$$

$$= \frac{1}{\partial I_D / \partial V_{DS}}$$

$$= \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \cdot \lambda}$$





$$r_O = \frac{1}{\lambda I_D}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}}$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \left( -\frac{\partial V_{TH}}{\partial V_{BS}} \right)$$

$$g_{mb} = g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}$$

$$= \eta g_m$$

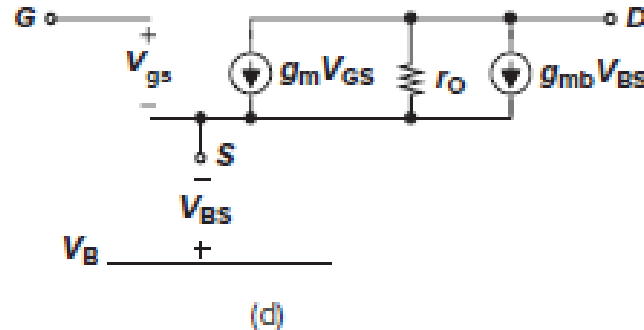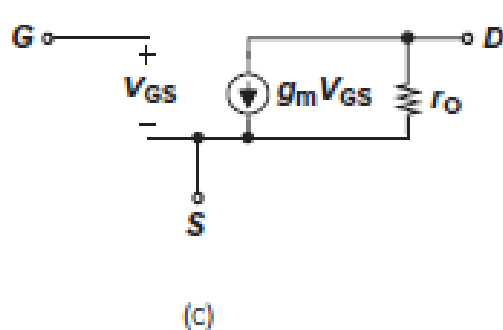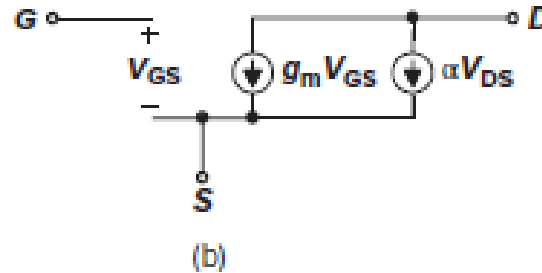 

$$V_{TH} = V_{TH0} + \gamma \left( \sqrt{2\Phi_F + V_{SB}} - \sqrt{2\Phi_F} \right)$$


$$\begin{aligned} \frac{\partial V_{TH}}{\partial V_{BS}} &= -\frac{\partial V_{TH}}{\partial V_{SB}} \\ &= -\frac{\gamma}{2} (2\Phi_F + V_{SB})^{-1/2} \end{aligned}$$

$\eta = g_{mb}/g_m$  and is typically around 0.25.


- Owing to channel-length modulation, the drain current also varies with the drain-source voltage
- The bulk potential influences the threshold voltage and hence the gate-source overdrive





# Complete MOS small-signal

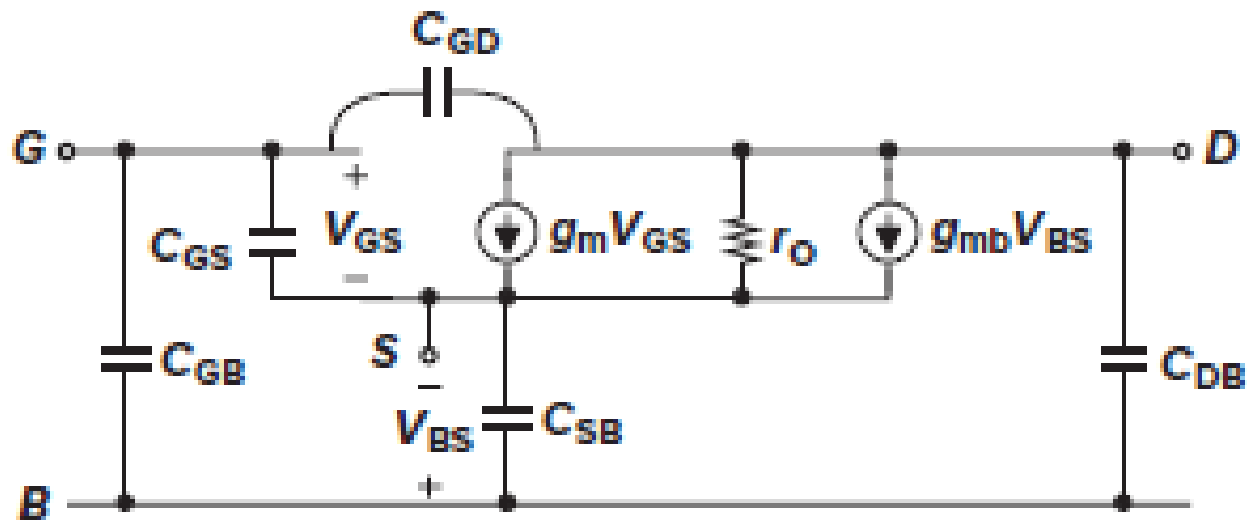

# Common Source Amplifier

 


$$v_o = -g_m v_{in} R_D$$

  

$$A_v = \frac{v_{out}}{v_{in}} = -g_m R_D; \quad R_{in} = \infty \quad R_{out} = R_D$$


# Common Source Amplifier

 

For large values of  $R_D$ , the effect of channel-length modulation in  $M_1$  becomes

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out})$$
 
$$\frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) (1 + \lambda V_{out}) - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}}$$



$$(1/2) \mu_n C_{ox} (W/L) (V_{in} - V_{TH})^2 \lambda = 1/r_O$$

$$A_v = -R_D g_m - \frac{R_D}{r_O} A_v$$



$$A_v = -g_m \frac{r_O R_D}{r_O + R_D}$$

$$A_v = -g_m (R_D || r_O)$$

$$R_{in} = \infty$$

$$R_{out} = R_D || r_O.$$

# CS Amplifier: Current-Source Load

  


$$A_v = -g_{m1}(r_{O1} || r_{O2})$$

$$R_{out} = r_{O1} || r_{O2}.$$

- In applications requiring a large voltage gain in a single stage, the relationship  $A_v = -g_m R_D$  suggests that we should increase the load impedance of the CS stage. With a resistor or diode-connected load, however, increasing the load resistance translates to a large dc drop across the load, thereby limiting the output voltage swing.


# CS Amplifier: Active Load

 

$$A_v = -g_{m1}(r_{O1} || r_{O2})$$

$$R_{out} = r_{O1} || r_{O2}.$$

 The PMOS device serves as a constant current source





PMOS Amplifier

$$A_v = -g_{m2}(r_{O1} || r_{O2})$$

PMOS  $M_2$  to operate as an *amplifying* device

# CS Amplifier: Diode Load

  


$$A_v = -g_{m1}(r_{o1} \parallel R_{O2})$$

$$A_v = -g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{O2} \parallel r_{O1} \right) \quad R_{out} = \frac{1}{g_{m2}} \parallel r_{O2} \parallel r_{O1}$$

- In some CMOS technologies, it is difficult to fabricate resistors with tightly controlled values or a reasonable physical size. Consequently, it is desirable to replace  $R_D$  with a MOS transistor


# CS Amplifier: Example

 

$$I_D = 1 \text{ mA}, \mu C_{ox} = 100 \mu\text{A/V}^2, V_{TH} = 0.5 \text{ V}$$

Find the gain and operating region of  $M_1$

# CS Amplifier: Example

 

How?

$$I_D = 1 \text{ mA}, \mu C_{ox} = 100 \mu\text{A/V}^2, V_{TH} = 0.5 \text{ V}$$

Find the gain and operating region of  $M_1$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

$$= \frac{1}{300 \Omega}$$

$$A_v = -g_m R_D$$

$$= 3.33.$$

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}}$$

$$= 1.1 \text{ V.}$$




$$V_{DS} = V_{DD} - I_D R_D = 0.8 \text{ V}$$

$$V_{GS} - V_{TH} = 0.6$$

$$V_{DS} > V_{GS} - V_{TH} \quad \text{In saturation!}$$






# Source Follower

   

$$g_m v_1 (r_o || R_L) = v_{out}$$

$$v_{in} = v_1 + v_{out}$$




# Source Follower

   

$$\begin{aligned} \frac{v_{out}}{v_{in}} &= \frac{g_m(r_o || R_L)}{1 + g_m(r_o || R_L)} \\ &= \frac{r_o || R_L}{\frac{1}{g_m} + r_o || R_L} \approx 1 \end{aligned}$$


Increase  $R_L$  (and  $r_o$ )

# Source Follower

   


$$\begin{aligned} \frac{v_{out}}{v_{in}} &= \frac{g_m(r_o || R_L)}{1 + g_m(r_o || R_L)} \\ &= \frac{r_o || R_L}{\frac{1}{g_m} + r_o || R_L} \\ &\approx 1 \end{aligned}$$

# Source Follower: Active Load

 

 
Find the gain and output impedance using small signal analysis



$$A_v = \frac{r_{O1} || r_{O2}}{\frac{1}{g_{m1}} + r_{O1} || r_{O2}}$$





If  $r_{O1} || r_{O2} \gg 1/g_{m1}$ , then  $A_v \approx 1$

# Source Follower: Application

 





- Our analysis of the common-source stage indicates that, to achieve a high voltage gain with limited supply voltage, the load impedance must be as large as possible. If such a stage is to drive a low-impedance load, then a “buffer” must be placed after the amplifier so as to drive the load with negligible reduction in gain. The source follower (also called the “common-drain” stage) can operate as a voltage buffer.

# Amplifier Biasing: CS

    


When  $V_{in}=0$ ,  $V_{GS}=?$ ,  $V_{DS}=?$

# Amplifier Biasing: SF

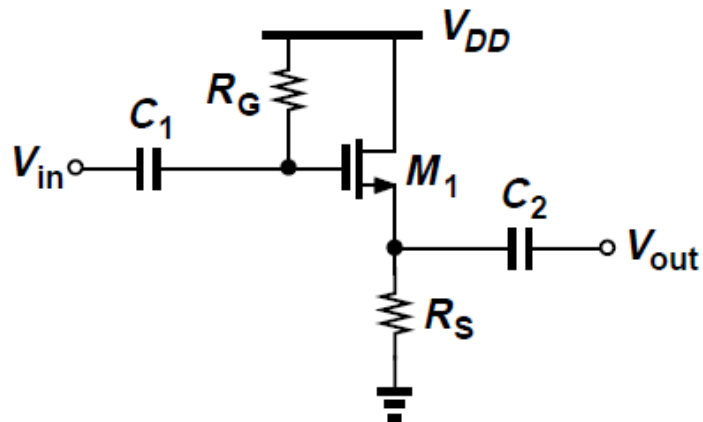   


When  $V_{in}=0$ ,  $V_{GS}=?$ ,  $V_{DS}=?$

# Current Mirror biasing

 




$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$
$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2$$

 Not a constant biasing!  $I_1$  depends on temperature and supply variation





# Current Mirror

   

$M_{REF}$  is always in saturation

$$I_{D,REF} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_{REF} (V_X - V_{TH})^2$$


$$I_{copy} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_X - V_{TH})^2$$

$$V_X = \sqrt{\frac{2I_{REF}}{\mu_n C_{ox} \left( \frac{W}{L} \right)}} + V_{TH1}$$

$$I_{copy} = \frac{\left( \frac{W}{L} \right)_1}{\left( \frac{W}{L} \right)_{REF}} I_{REF}$$

# Current Mirror biasing


SF Amplifier

 

$$I_1 = I_{REF} \frac{2}{3} = 0.2 \text{ mA}$$

What happens here?


CS Amplifier

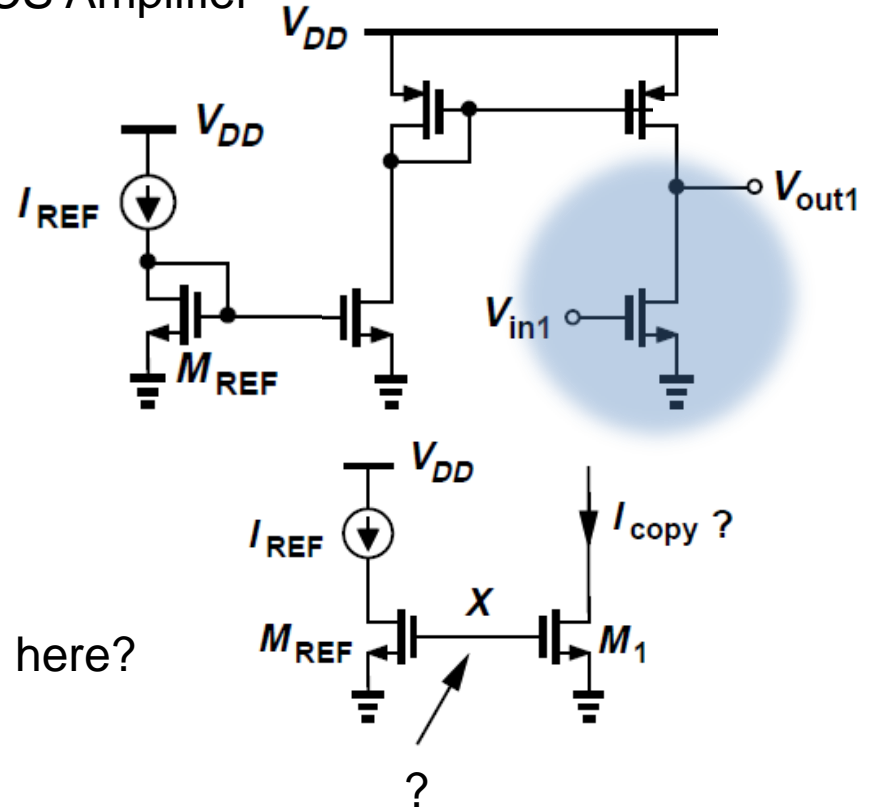


- This circuit is not a current mirror because only a diode-connected device can establish and hence a copy current independent of device parameters and temperature. Since the gates of  $M_{REF}$  and  $M_1$  are floating, they can assume any voltage, e.g., an initial condition created at node  $X$  when the power supply is turned on. In other words,  $I_{copy}$  is very poorly defined.
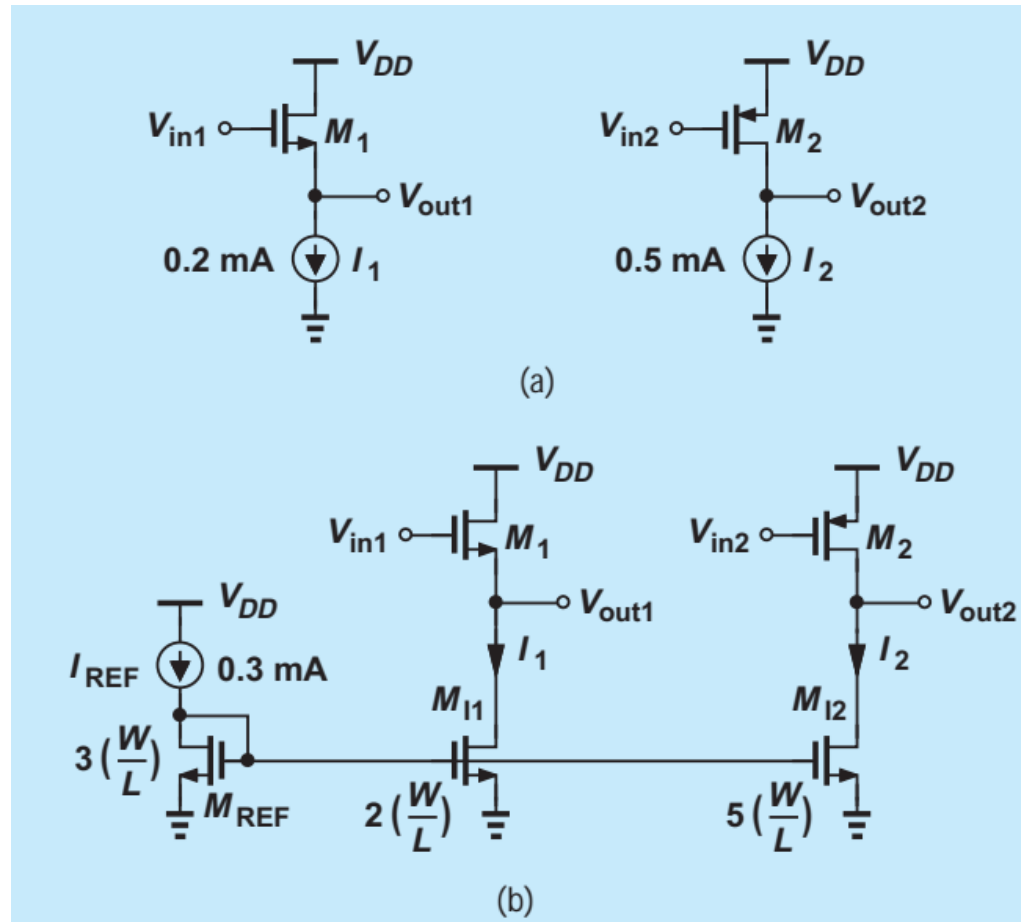
# Current Mirror biasing

- An integrated circuit employs the source follower and the common-source stage shown below. Design a current mirror that produces  $I_1$  and  $I_2$  from a 0.3-mA reference



# Cascode Gain Stage

 

$$A_v = -G_m R_{out}$$


$$\approx -g_{m1}[(1 + g_{m2}r_{O2})r_{O1} + r_{O2}]$$

$$\approx -g_{m1}r_{O1}g_{m2}r_{O2}.$$

$$R_{on} \approx g_{m2}r_{O2}r_{O1}$$


$$R_{op} \approx g_{m3}r_{O3}r_{O4}$$

$$A_v \approx -g_{m1}[(g_{m2}r_{O2}r_{O1}) || (g_{m3}r_{O3}r_{O4})]$$

 

$$R_{out} = (1 + g_{m1}r_{O2})r_{O1} + r_{O2}$$

$$\approx g_{m1}r_{O1}r_{O2},$$

 

- Cascode stages can have quite large gain for a single stage due to the large impedances at the output. To enable this high gain, the current sources connected to the output nodes are realised using high-quality cascode current mirrors. Normally this high gain is obtained without any degradation in speed.

# Cascode Gain Stage: Example

- The cascode amplifier incorporates the following device parameters:  $(W/L)_{1,2} = 30$ ,  $(W/L)_{3,4} = 40$ ,  $I_{D1} = \dots = I_{D4} = 0.5 \text{ mA}$ . If  $\mu_n C_{ox} = 100 \mu\text{A/V}^2$ ,  $\mu_p C_{ox} = 50 \mu\text{A/V}^2$ ,  $\lambda_n = 0.1 \text{ V}^{-1}$  and  $\lambda_p = 0.15 \text{ V}^{-1}$ , determine the voltage gain.

**Solution** With the particular choice of device parameters here,  $g_{m1} = g_{m2}$ ,  $r_{O1} = r_{O2}$ ,  $g_{m3} = g_{m4}$ , and  $r_{O3} = r_{O4}$ . We have

$$\begin{aligned} g_{m1,2} &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_{1,2} I_{D1,2}} \\ &= (577 \Omega)^{-1} \end{aligned}$$

and

$$g_{m3,4} = (707 \Omega)^{-1}.$$

Also,

$$\begin{aligned} r_{O1,2} &= \frac{1}{\lambda_n I_{D1,2}} \\ &= 20 \text{ k}\Omega \end{aligned}$$

and

$$r_{O3,4} = 13.3 \text{ k}\Omega.$$

$$R_{on} \approx 693 \text{ k}\Omega$$

$$R_{op} \approx 250 \text{ k}\Omega$$

and

$$\begin{aligned} A_v &= -g_{m1}(R_{on} || R_{op}) \\ &\approx -318. \end{aligned}$$