


Lecture 2: Circuits & Layout

Outline


- ☐ A Brief History
- ☐ CMOS Gate Design
- ☐ Pass Transistors
- ☐ CMOS Latches & Flip-Flops
- ☐ Standard Cell Layouts
- ☐ Stick Diagrams

The First Computer

 The Babbage
Difference Engine
(1832)
25.000 parts
cost: £17.470



 
ENIAC – The First Electronic Computer (1946)



The Transistor Revolution



 
**John
Bardeen,
Walter
Brattain,
and their
supervisor
William
Shockley.**




**First Transistor
Bell Labs
1948**

A Brief History

 - ❑ 1958: First integrated circuit
 - Flip-flop using two transistors
 - Built by Jack Kilby at Texas Instruments
- ❑ 2010
 - Intel Core i7 μ processor
 - 2.3 billion transistors
 - 64 Gb Flash memory
 - > 16 billion transistors




Courtesy Texas Instruments

 

[Trinh09]
© 2009 IEEE.


First Integrated Circuits

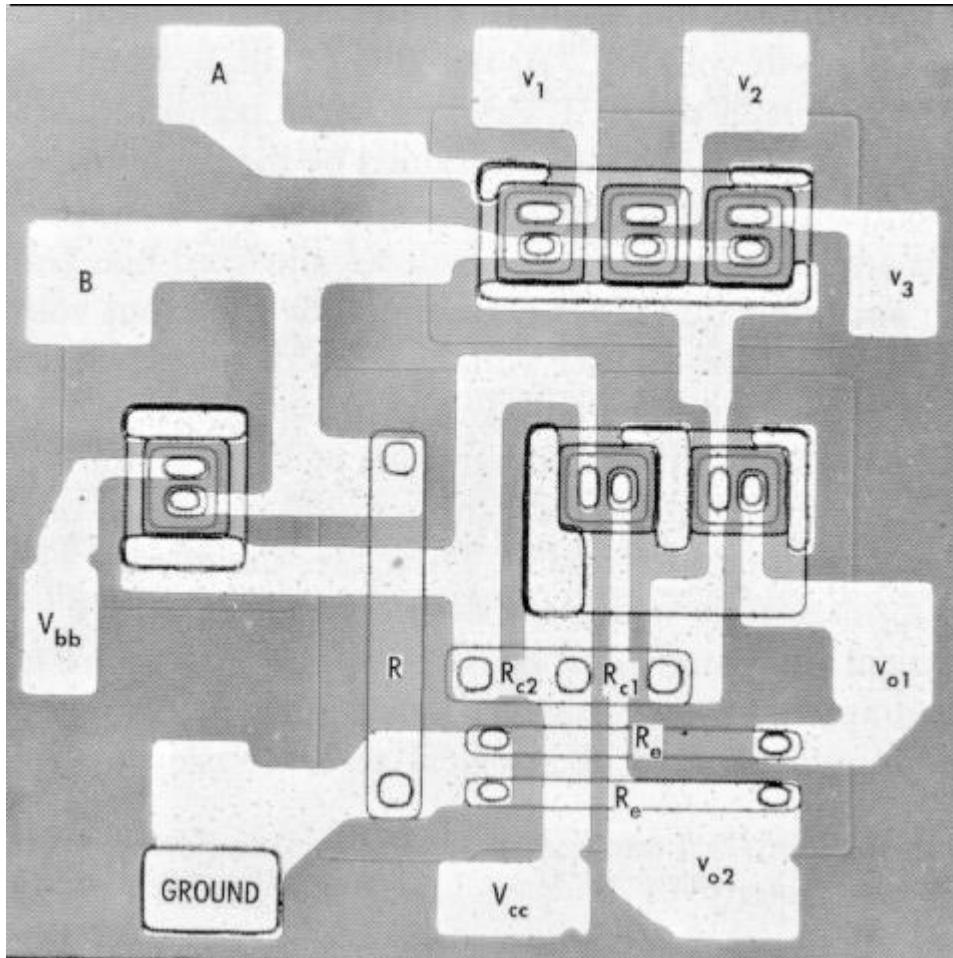

Bipolar Logic
1960's

ECL 3-input
NAND Gate
Motorola

Intel 4004 Microprocessor

 

1971
1000 transistors
1 MHz operation

Growth Rate

- ❑ 53% compound annual growth rate over 50 years
 - No other technology has grown so fast so long
- ❑ Driven by miniaturization of transistors
 - Smaller is cheaper, faster, lower in power!
 - Revolutionary effects on society




[Moore65]

Electronics Magazine


Annual Sales

 - ❑ $>10^{19}$ transistors manufactured in 2008
 - 1 billion for every human on the planet



Invention of the Transistor

 - ❑ Vacuum tubes ruled in first half of 20th century
Large, expensive, power-hungry, unreliable
- ❑ 1947: first point contact transistor
 - John Bardeen and Walter Brattain at Bell Labs
 - See *Crystal Fire*
by Riordan, Hodgeson




AT&T Archives.
Reprinted with
permission.

Transistor Types


- ❑ Bipolar transistors
 - npn or pnp silicon structure
 - Small current into very thin base layer controls large currents between emitter and collector
 - Base currents limit integration density
- ❑ Metal Oxide Semiconductor Field Effect Transistors
 - nMOS and pMOS MOSFETS
 - Voltage applied to insulated gate controls current between source and drain
 - Low power allows very high integration

MOS Integrated Circuits

- ❑ 1970's processes usually had only nMOS transistors
 - Inexpensive, but consume power while idle

 

[Vadasz69]
© 1969 IEEE.

 

Intel Museum.
Reprinted with permission.

Intel 1101 256-bit SRAM

Intel 4004 4-bit μ Proc


- ❑ 1980s-present: CMOS processes for low idle power

Moore's Law

- ❑ In 1965, Gordon Moore noted that the number of transistors on a chip doubled every 18 to 24 months.
- ❑ He made a prediction that semiconductor technology will double its effectiveness every 18 months

Moore's Law: Then

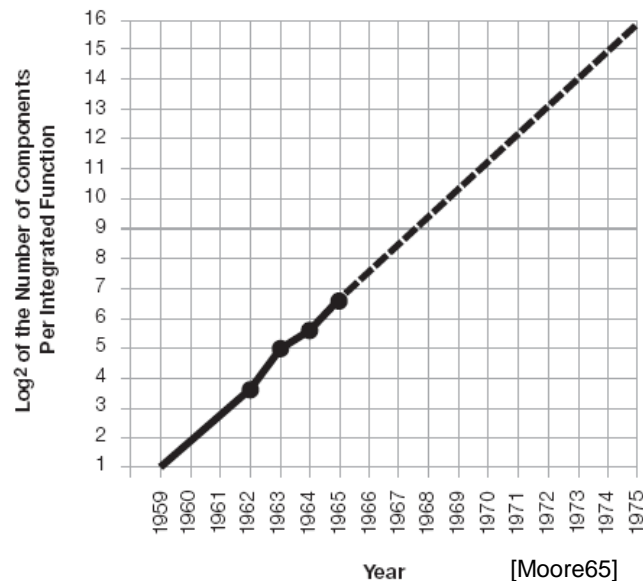- ❑ 1965: Gordon Moore plotted transistor on each chip
 - Fit straight line on semilog scale
 - Transistor counts have doubled every 26 months



Electronics Magazine

Integration Levels


SSI: 10 gates

MSI: 1000 gates


LSI: 10,000 gates

VLSI: > 10k gates

And Now...

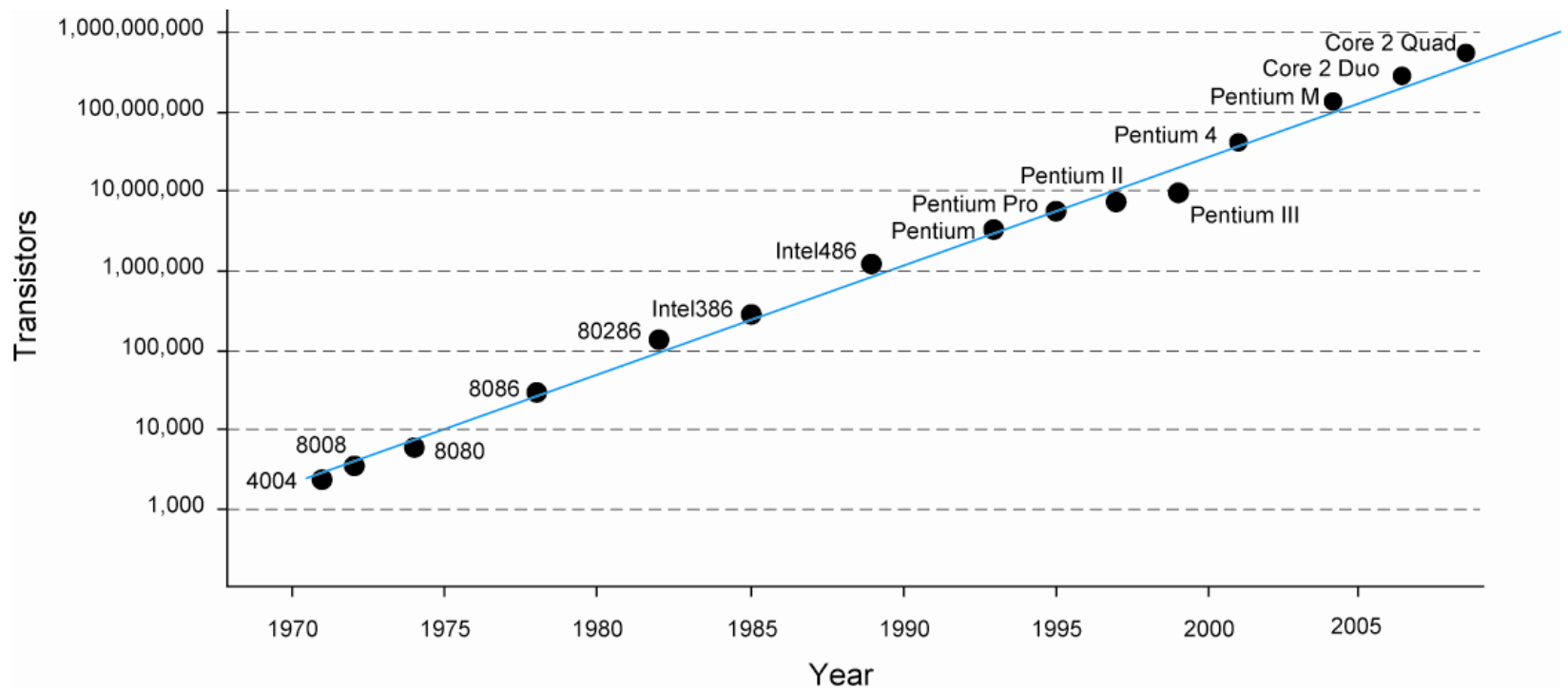


Evolution in Complexity

 

Feature Size

- Minimum feature size shrinking 30% every 2-3 years

 feature size of any semiconductor technology is defined as *the minimum length of the MOS transistor channel between the drain and the source*




Feature Size

TABLE 7.6 Predictions from the 2007 ITRS


Year	2009	2012	2015	2018	2021
Feature size (nm)	34	24	17	12	8.4
L_{gate} (nm)	20	14	10	7	5
V_{DD} (V)	1.0	0.9	0.8	0.7	0.65
Billions of transistors/die	1.5	3.1	6.2	12.4	24.7
Wiring levels	12	12	13	14	15
Maximum power (W)	198	198	198	198	198
DRAM capacity (Gb)	2	4	8	16	32
Flash capacity (Gb)	16	32	64	128	256

Feature Size

 


~40,000 (65-nm node) transistors could fit on cross-section

Die Size Growth

 


Die size grows by 14% to satisfy Moore's Law

Power Dissipation

 


Lead Microprocessors power continues to increase

Power density

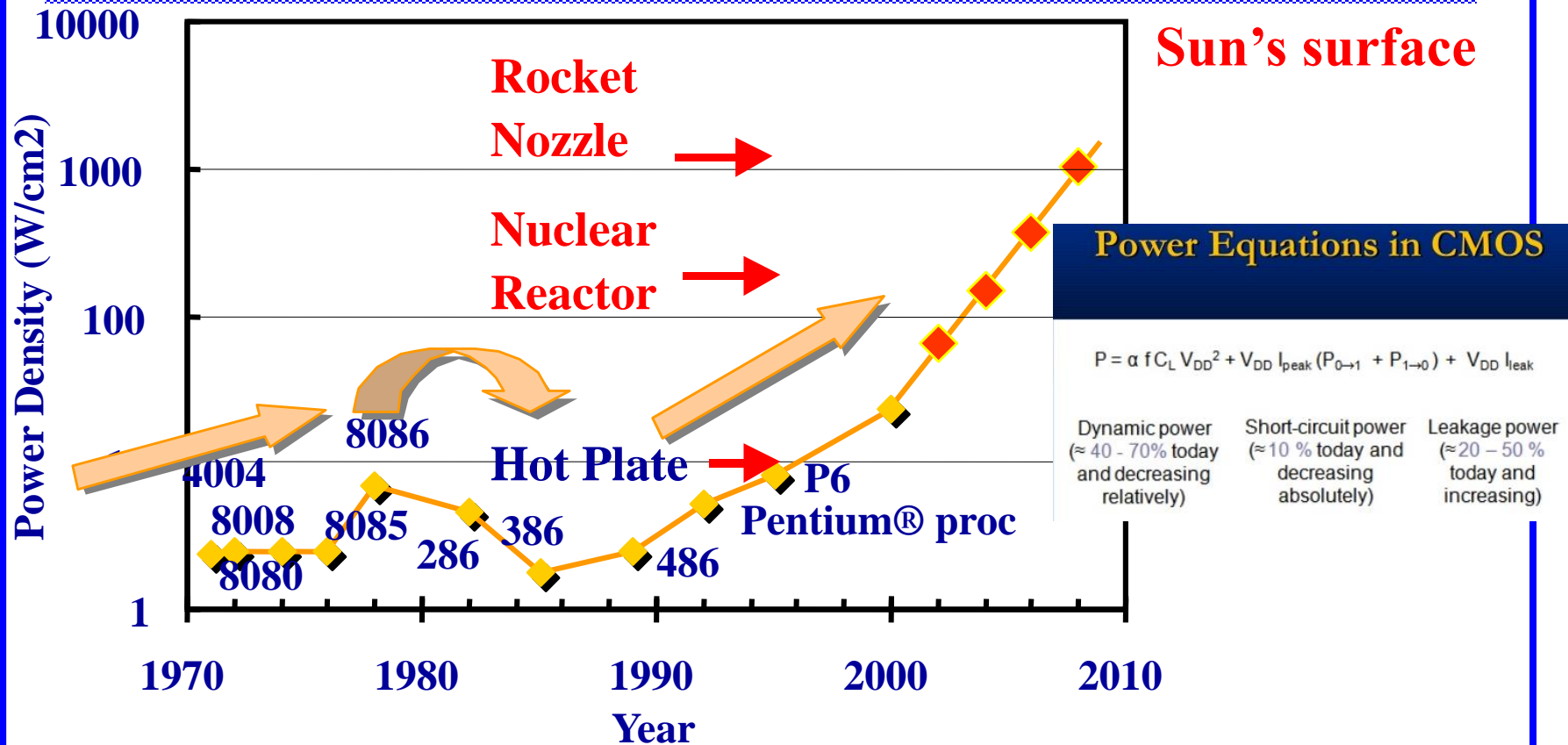

Power density too high to keep junctions at low temp

Productivity Trends

 

Source: Sematech

Complexity outpaces design productivity

Why Scaling?

- ❑ Technology shrinks by 0.7/generation
- ❑ With every generation can integrate 2x more functions per chip; chip cost does not increase significantly
- ❑ Cost of a function decreases by 2x
- ❑ But ...
 - How to design chips with more and more functions?
 - Design engineering population does not double every two years...
- ❑ Hence, a need for more efficient design methods
 - Exploit different levels of abstraction


Design Metrics

- ❑ How to evaluate performance of a digital circuit (gate, block, ...)?
 - Cost
 - Reliability
 - Scalability
 - Speed (delay, operating frequency)
 - Power dissipation
 - Energy to perform a function


Cost of Integrated Circuits

- ❑ NRE (non-recurrent engineering) costs
 - design time and effort, mask generation
 - one-time cost factor
- ❑ Recurrent costs
 - silicon processing, packaging, test
 - proportional to volume
 - proportional to chip area

NRE Cost is Increasing

 

Die Cost

 


Single die

Wafer



Going up to 12" (30cm)

Cost per Transistor

 


Yield


$$Y = \frac{\text{No. of good chips per wafer}}{\text{Total number of chips per wafer}} \times 100\%$$

$$\text{Die cost} = \frac{\text{Wafer cost}}{\text{Dies per wafer} \times \text{Die yield}}$$
 
$$\text{Dies per wafer} = \frac{\pi \times (\text{wafer diameter}/2)^2}{\text{die area}} - \frac{\pi \times \text{wafer diameter}}{\sqrt{2} \times \text{die area}}$$



Defects

 

$$\text{die yield} = \left(1 + \frac{\text{defects per unit area} \times \text{die area}}{\alpha} \right)^{-\alpha}$$

α is approximately 3

$$\text{die cost} = f(\text{die area})^4$$

Some Examples (1994)


Chip	Metal layers	Line width	Wafer cost	Def./cm ²	Area mm ²	Dies/wafer	Yield	Die cost
386DX	2	0.90	\$900	1.0	43	360	71%	\$4
486 DX2	3	0.80	\$1200	1.0	81	181	54%	\$12
Power PC 601	4	0.80	\$1700	1.3	121	115	28%	\$53
HP PA 7100	3	0.80	\$1300	1.0	196	66	27%	\$73
DEC Alpha	3	0.70	\$1500	1.2	234	53	19%	\$149
Super Sparc	3	0.70	\$1700	1.6	256	48	13%	\$272
Pentium	3	0.80	\$1500	1.5	296	40	9%	\$417

CMOS Gate Design

- Activity:
 - Sketch a 4-input CMOS NOR gate

Complementary CMOS

 
- ❑ Complementary CMOS logic gates
 - nMOS *pull-down network*
 - pMOS *pull-up network*
 - a.k.a. static CMOS



	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)


Series and Parallel

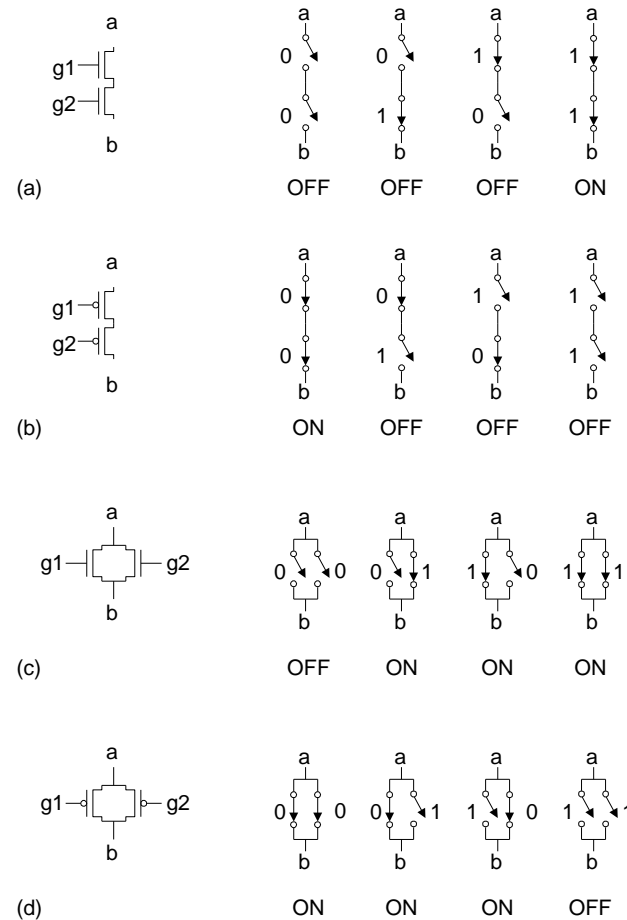- ❑ nMOS: 1 = ON
- ❑ pMOS: 0 = ON
- ❑ *Series*: both must be ON
- ❑ *Parallel*: either can be ON




Conduction Complement

 - ❑ Complementary CMOS gates always produce 0 or 1
- ❑ Ex: NAND gate
 - Series nMOS: $Y=0$ when both inputs are 1
 - Thus $Y=1$ when either input is 0
 - Requires parallel pMOS
- ❑ Rule of *Conduction Complements*
 - Pull-up network is complement of pull-down
 - Parallel \rightarrow series, series \rightarrow parallel




Compound Gates

 - ❑ *Compound gates can do any invertina function*
- ❑ Ex: $Y = \overline{A \cdot B + C \cdot D}$ (AND-AND-OR-INVERT, AOI22)





Example: O3AI

□ $Y = \overline{(A+B+C)} \cdot D$

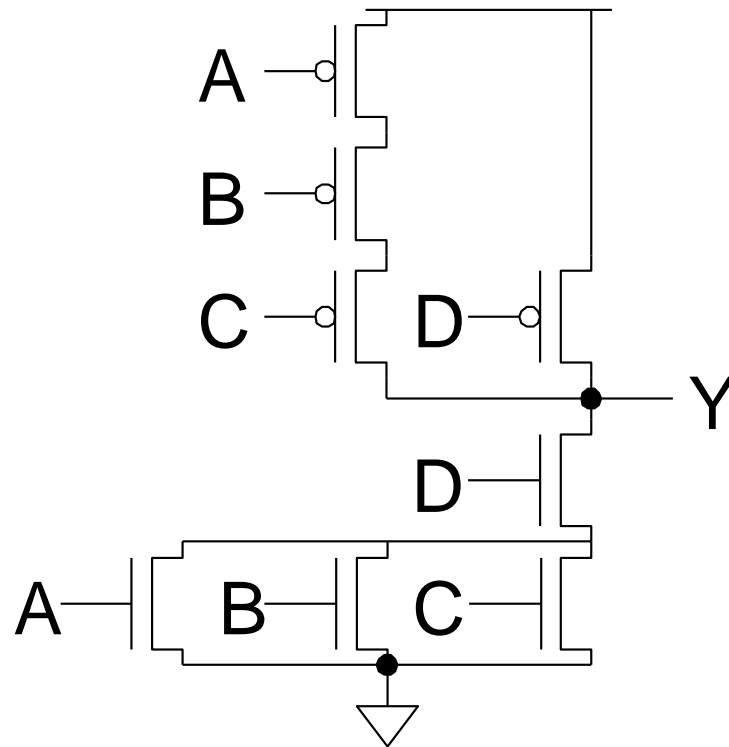










Signal Strength

  - ❑ *Strength* of signal
 - How close it approximates ideal voltage source
- ❑ V_{DD} and GND rails are strongest 1 and 0
- ❑ nMOS pass strong 0
 - But degraded or weak 1
- ❑ pMOS pass strong 1
 - But degraded or weak 0
- ❑ Thus nMOS are best for pull-down network




Pass Transistors

- Transistors can be used as switches

         


Transmission Gates

 
- ❑ Pass transistors produce degraded outputs
- ❑ *Transmission gates* pass both 0 and 1 well



$g = 0, gb = 1$

 

$g = 1, gb = 0$

 

Input




Output

$g = 1, gb = 0$

0 → strong 0

$g = 1, gb = 0$




1 → strong 1

   

Tristates


- ❑ *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	
0	1	
1	0	
1	1	

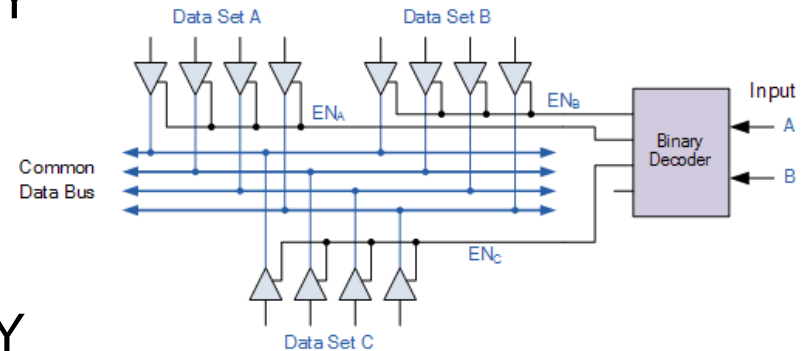  


Nonrestoring Tristate

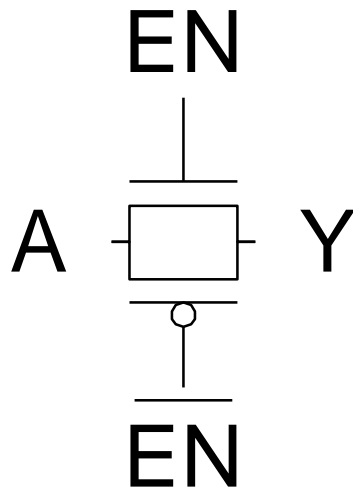- ❑ Transmission gate acts as tristate buffer
 - Only two transistors
 - But *nonrestoring*
 - Noise on A is passed on to Y



Tristate Inverter

 - ❑ Tristate inverter produces restored output
 - Violates conduction complement rule
 - Because we want a Z output



Tristates were once commonly used to allow multiple units to drive a common bus, as long as exactly one unit is enabled at a time.

- If multiple units drive the bus, contention occurs and power is wasted.
- If no units drive the bus, it can float to an invalid logic level that causes the receivers to waste power.
- Moreover, it can be difficult to switch enable signals at exactly the same time when they are distributed across a large chip. Delay between different enables switching can cause contention.


Given these problems, multiplexers are now preferred over tristate busses

Multiplexers

- ❑ 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	

 chooses input D0 when the select is 0 and input D1 when the select is 1.




Gate-Level Mux Design

- ❑ $Y = SD_1 + \bar{S}D_0$ (too many transistors)
- ❑ How many transistors are needed?


Transmission Gate Mux

 - ❑ Nonrestoring mux uses two transmission gates
 - Only 4 transistors





Inverting Mux

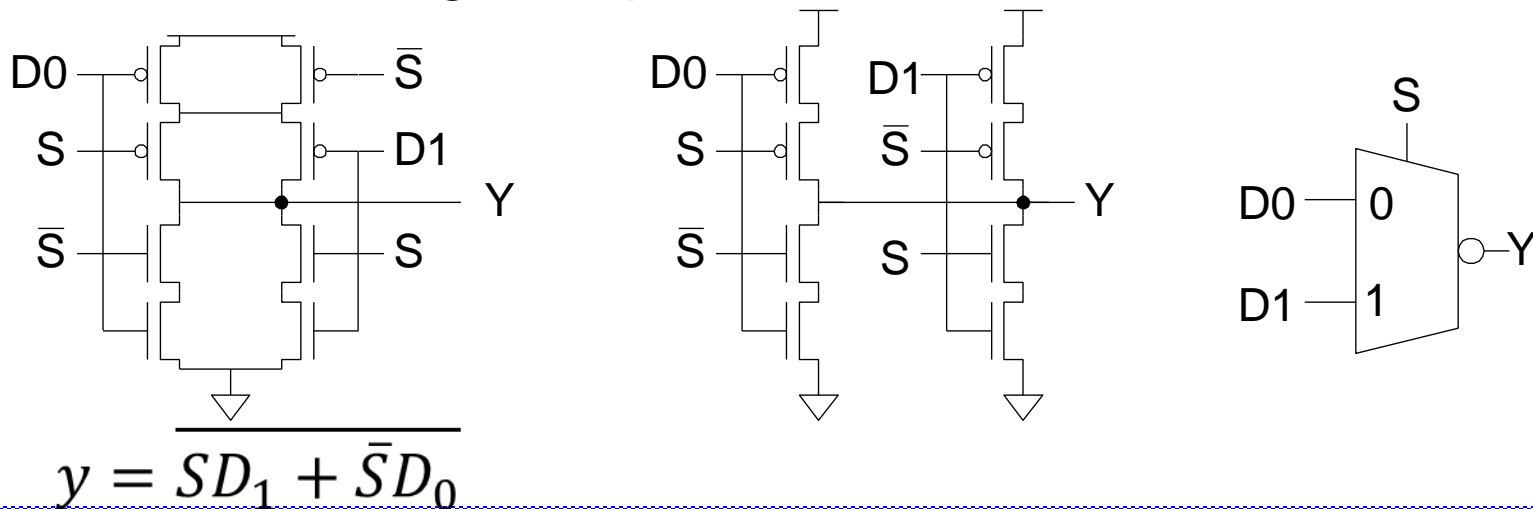- ❑ Inverting multiplexer
 - Use compound AOI22
 - Or pair of tristate inverters
 - Essentially the same thing
- ❑ Noninverting multiplexer adds an inverter




  4:1 Multiplexer

- ❑ 4:1 mux chooses one of 4 inputs using two selects
 - Two levels of 2:1 muxes
 - Or four tristates




4:1 Multiplexer

 

S1	S0	Z
0	0	A
0	1	B
1	0	C
1	1	D



D Latch

 - ❑ When $\text{CLK} = 1$, latch is *transparent*
 - D flows through to Q like a buffer
- ❑ When $\text{CLK} = 0$, the latch is *opaque*
 - Q holds its old value independent of D
- ❑ a.k.a. *transparent latch* or *level-sensitive latch*






D Latch Design

- ❑ Multiplexer chooses D or old Q

  


D Latch Operation

   

When $CLK = 1$, the latch is transparent and D flows through to Q (Figure 1.31(c)). When CLK falls to 0, the latch becomes opaque. A feedback path around the inverter pair is established to hold the current state of Q indefinitely.


D Flip-flop

 - ❑ When CLK rises, D is copied to Q
- ❑ At all other times, Q holds its value
- ❑ a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*




D Flip-flop Design

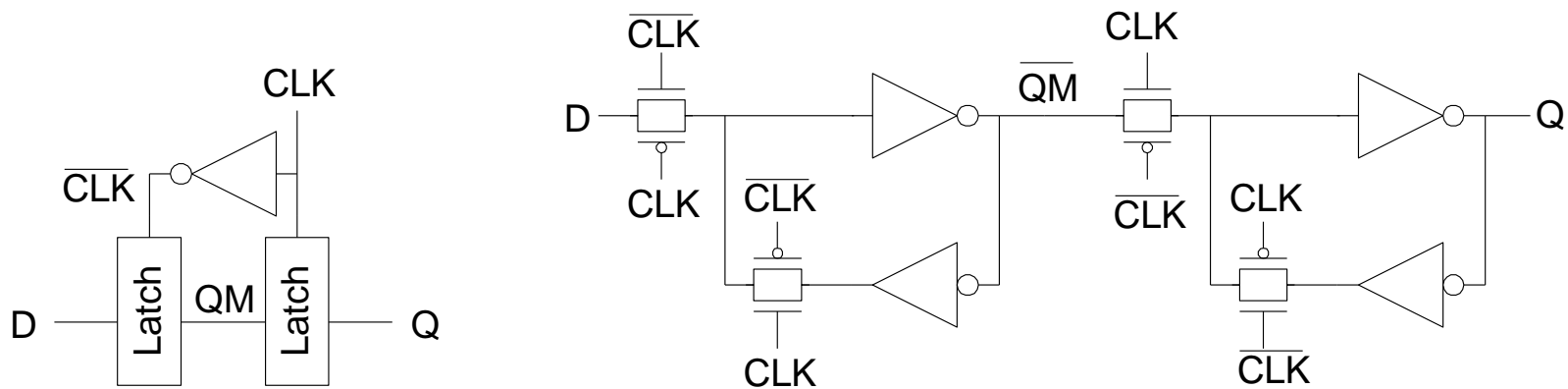- ❑ Built from master and slave D latches




D Flip-flop Operation

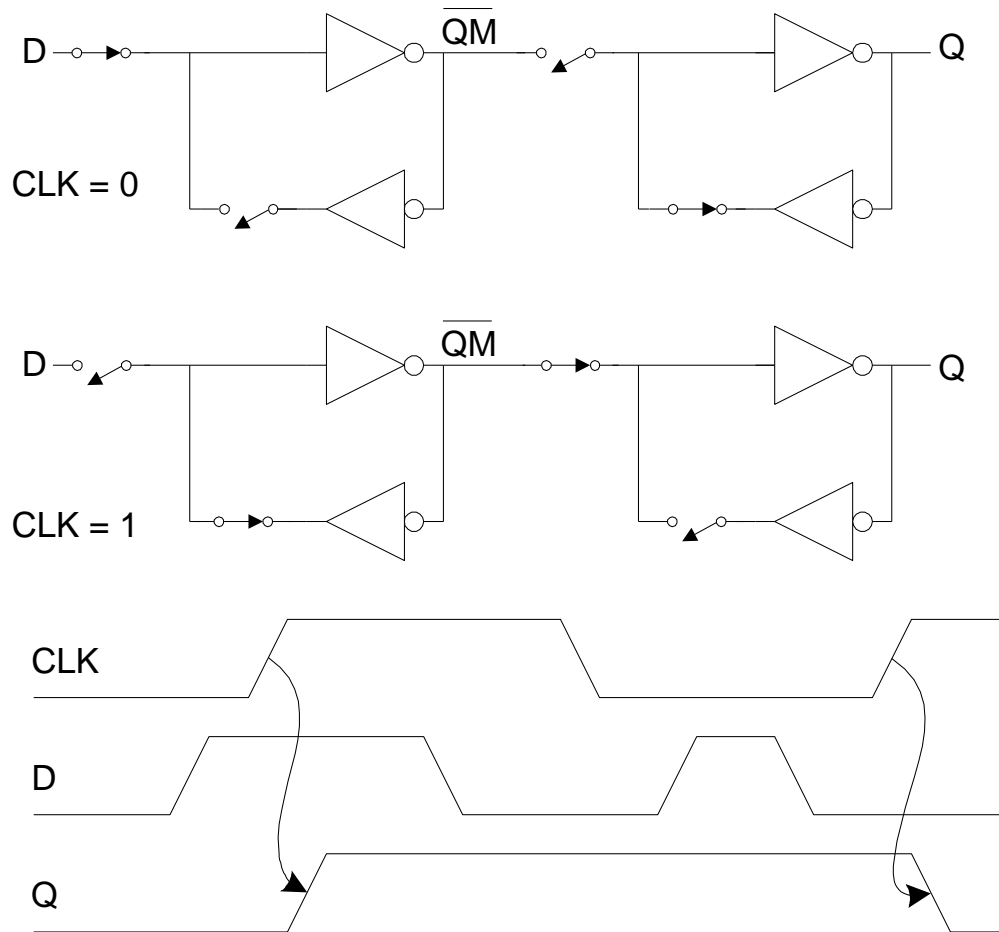

While CLK is low, the master negative-level-sensitive latch output ($\overline{Q_M}$) follows the D input while the slave positive-level-sensitive latch holds the previous value. When the clock transitions from 0 to 1, the master latch becomes opaque and holds the D value at the time of the clock transition. The slave latch becomes transparent, passing the stored master value ($\overline{Q_M}$) to the output of the slave latch (Q). The D input is blocked from affecting the output because the master is disconnected from the D input. When the clock transitions from 1 to 0, the slave latch holds its value and the master starts sampling the input again.


Race Condition

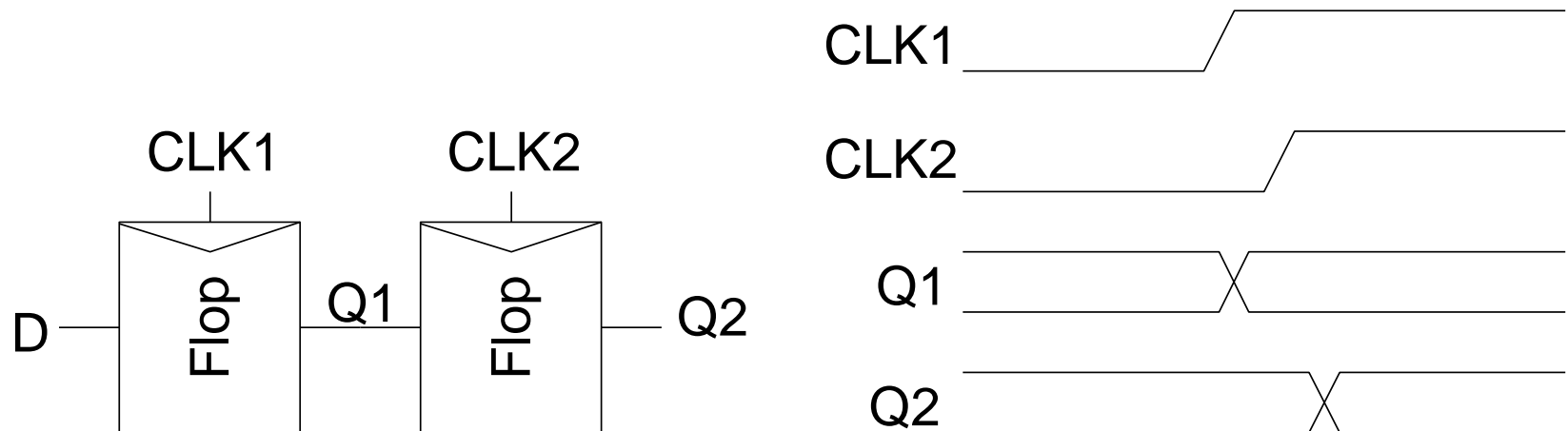- ❑ Back-to-back flops can malfunction from clock skew
 - Second flip-flop fires late
 - Sees first flip-flop change and captures its result
 - Called *hold-time failure* or *race condition*



Nonoverlapping Clocks

 
- ❑ Nonoverlapping clocks can prevent races
 - As long as nonoverlap exceeds clock skew
- ❑ We will use them in this class for safe design
 - Industry manages skew more carefully instead



Gate Layout


- ❑ Layout can be very time consuming
 - Design gates to fit together nicely
 - Build a library of standard cells
- ❑ Standard cell design methodology
 - V_{DD} and GND should abut (standard height)
 - Adjacent gates should satisfy design rules
 - nMOS at bottom and pMOS at top
 - All gates include well and substrate contacts

Example: Inverter

 

 
Example: NAND3

- ❑ Horizontal N-diffusion and p-diffusion strips
- ❑ Vertical polysilicon gates
- ❑ Metal1 V_{DD} rail at top
- ❑ Metal1 GND rail at bottom
- ❑ 32λ by 40λ




Stick Diagrams

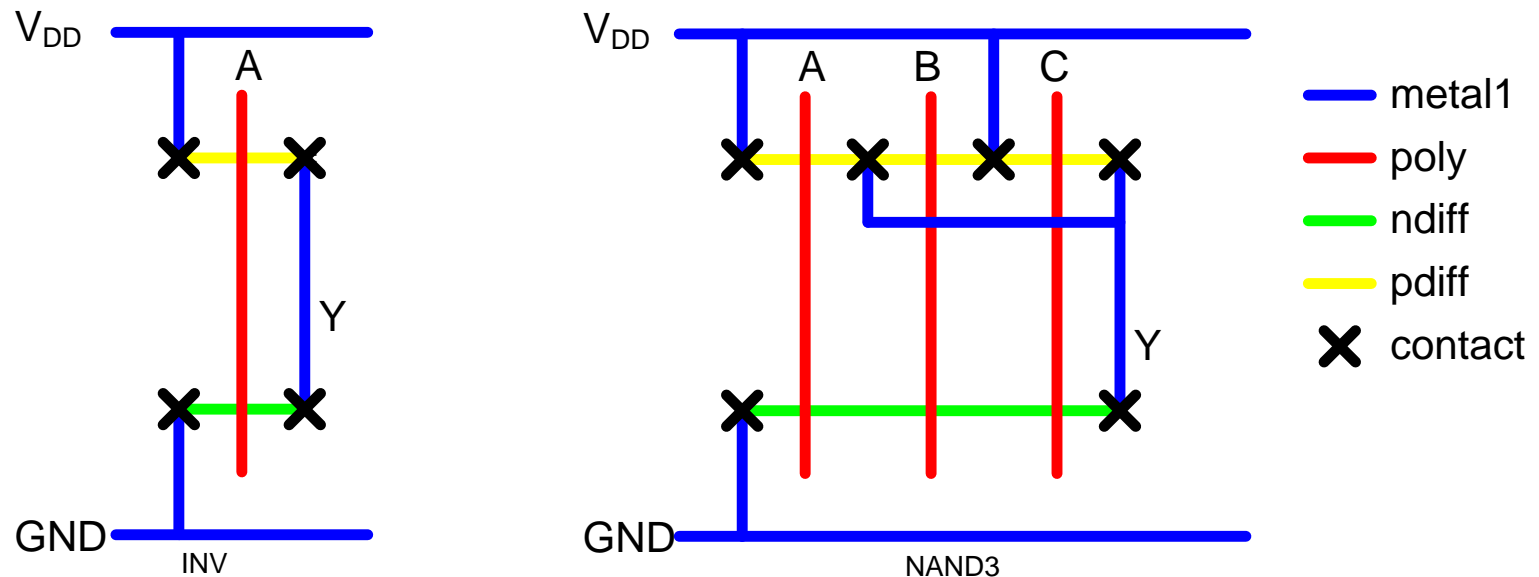- *Stick diagrams* help plan layout quickly
 - Need not be to scale
 - Draw with color pencils or dry-erase markers




Wiring Tracks

 - ❑ A *wiring track* is the space required for a wire
 - 4λ width, 4λ spacing from neighbor = 8λ pitch
- ❑ Transistors also consume one wiring track




Well spacing

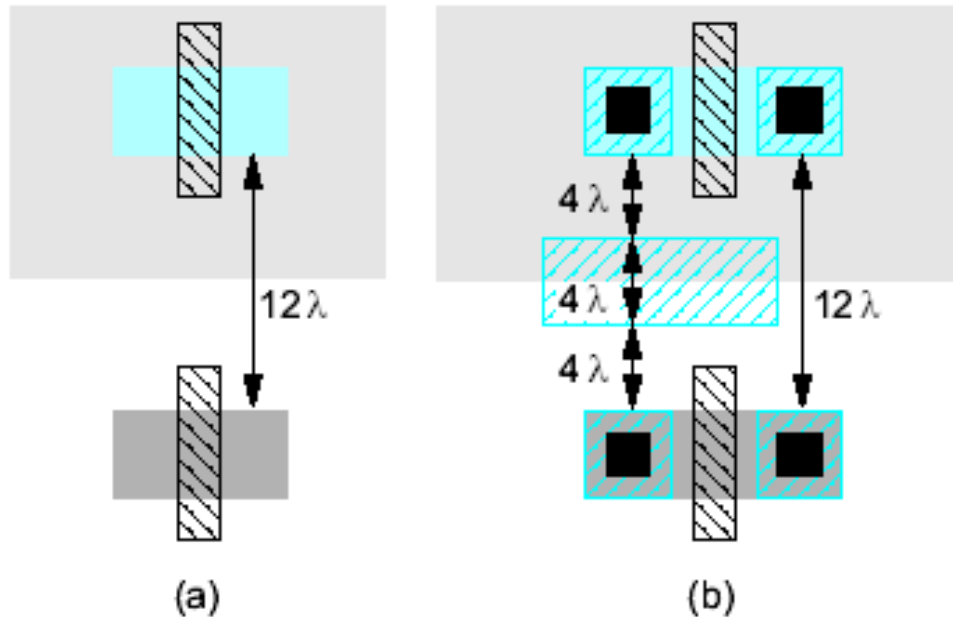- ❑ Wells must surround transistors by 6λ
 - Implies 12λ between opposite transistor flavors
 - Leaves room for one wire track



Area Estimation

 - ❑ Estimate area by counting wiring tracks
 - Multiply by 8 to express in λ



Example: O3AI

- Sketch a stick diagram for O3AI and estimate area

$$- Y = \overline{(A+B+C)} \cdot D$$

