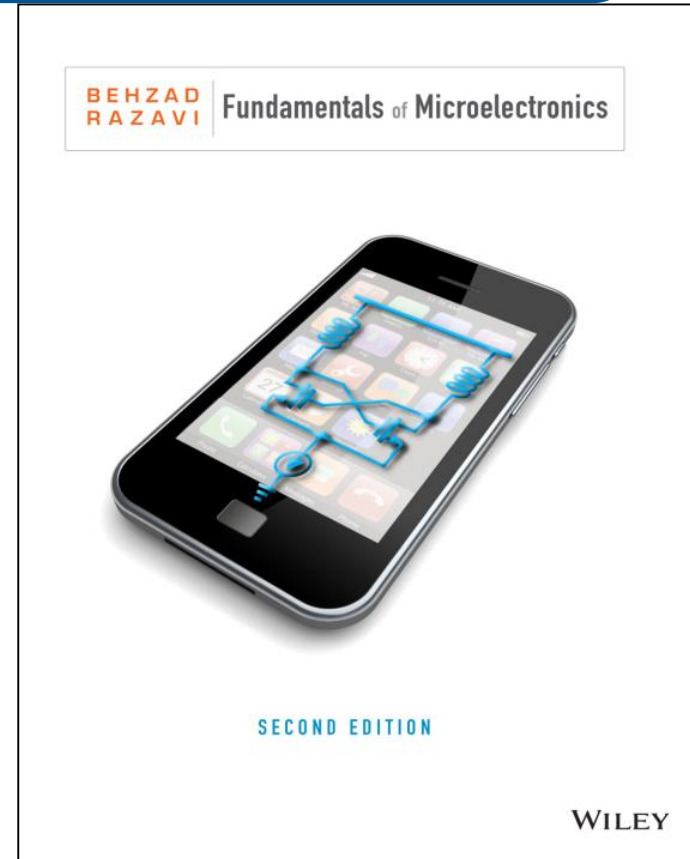


Frequency Response

- **Fundamental Concepts**
- **High-Frequency Models of Transistors**
- **Analysis Procedure**
- **Frequency Response of CS Stages**
- **Frequency Response of CG Stages**
- **Frequency Response of Followers**
- **Frequency Response of Cascode Stage**
- **Frequency Response of Differential Pairs**
- **Additional Examples**



Ref books:

Behzad Razavi, “Fundamentals of Microelectronics, 2nd Edition”, Chapter 11

Behzad Razavi, “Design of Analog CMOS Integrated Circuits, 2nd Edition”, Chapter 6

Outline

Fundamental Concepts

- Bode's Rules
- Association of Poles with Nodes
- Miller's Theorem



High-Frequency Models of Transistors



- MOS Model
- Transit Frequency



Frequency Response of Circuits

- CS Stages
- CG Stages
- Followers
- Cascode Stage
- Differential Pair

High Frequency Roll-off of Amplifier

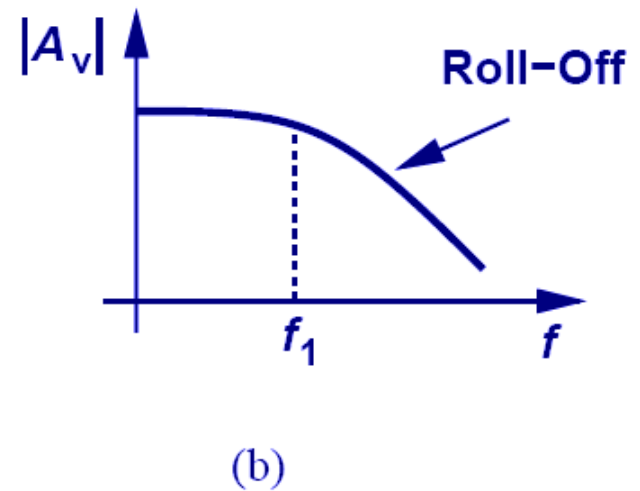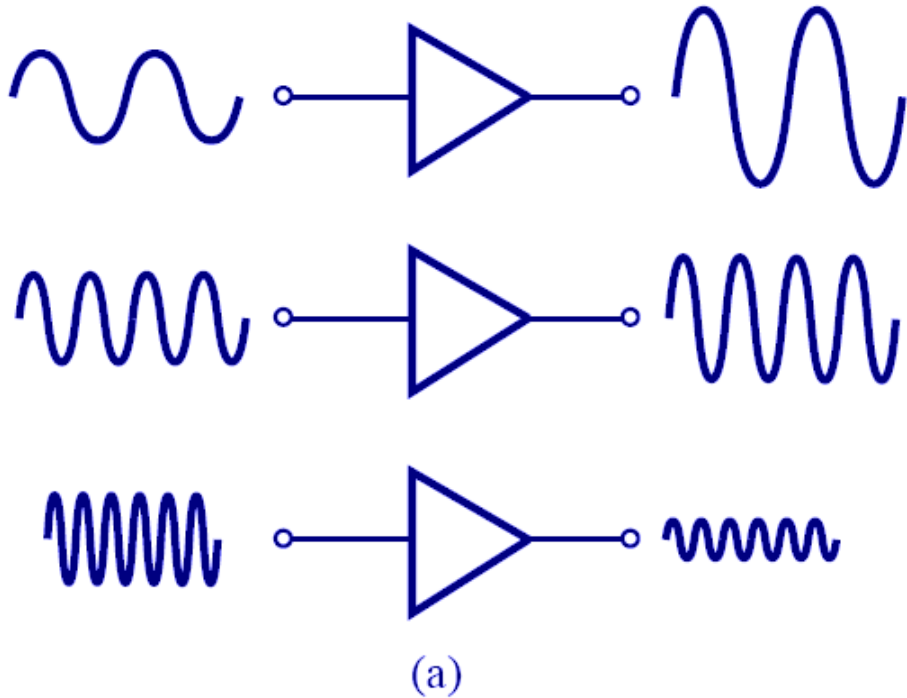

➤ As frequency of operation increases, the gain of amplifier decreases. This chapter analyzes this problem.


Example: Human Voice I

Natural Voice



(a)

Telephone System

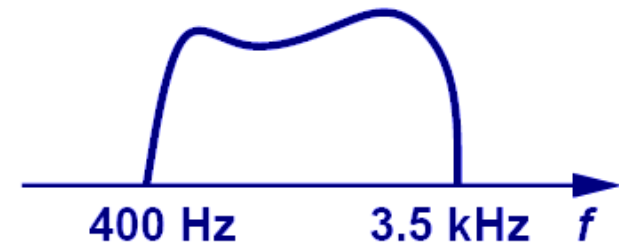


(b)


- Natural human voice spans a frequency range from 20Hz to 20KHz, however conventional telephone system passes frequencies from 400Hz to 3.5KHz. Therefore phone conversation differs from face-to-face conversation.

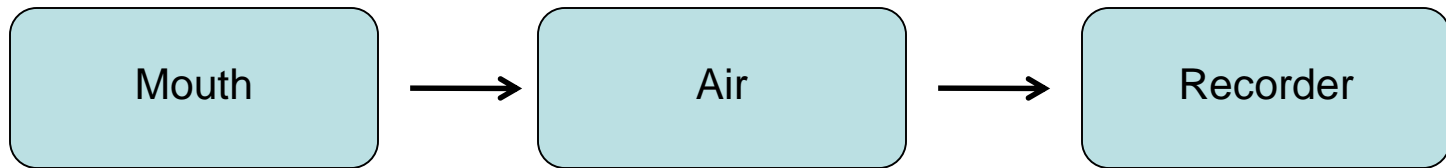Example: Human Voice II

Path traveled by the human voice to the voice recorder



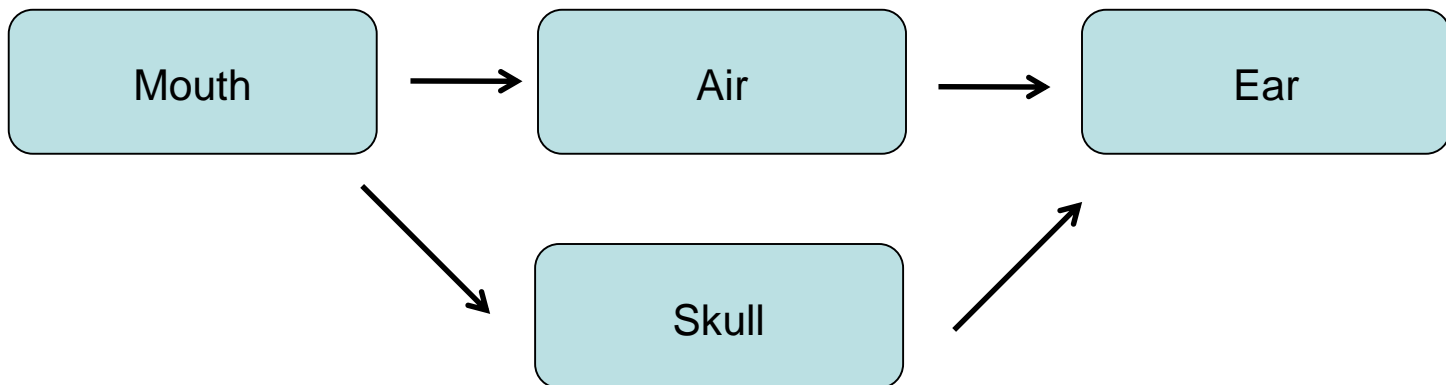Path traveled by the human voice to the human ear




➤ Since the paths are different, the results will also be different.

Example: Video Signal



(a)

High Bandwidth


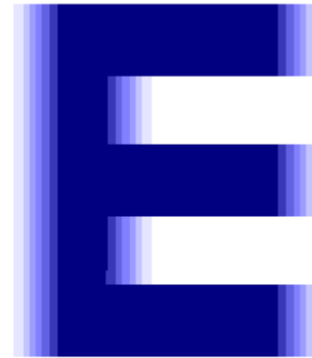


(b)

Low Bandwidth


- Video signals without sufficient bandwidth become fuzzy as they fail to abruptly change the contrast of pictures from complete white into complete black.

Gain Roll-off: Simple Low-pass Filter

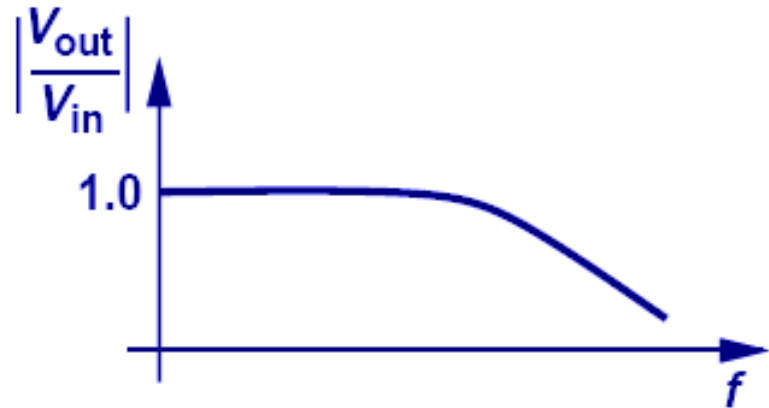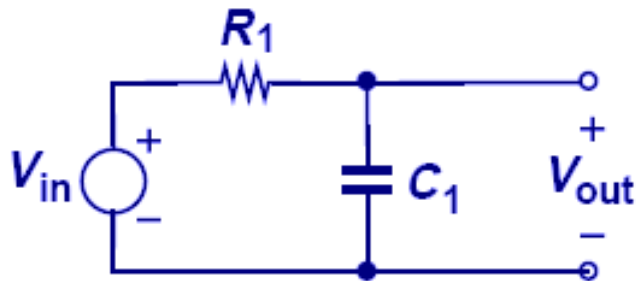


- In this simple example, as frequency increases the impedance of C_1 decreases and the voltage divider consists of C_1 and R_1 attenuates V_{in} to a greater extent at the output.

Gain Roll-off: Common Source

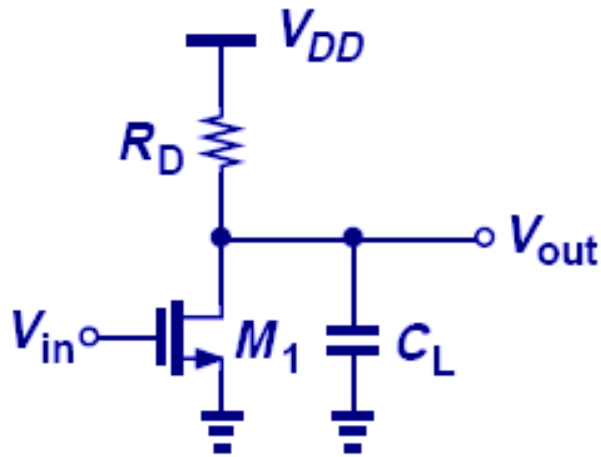

(a)

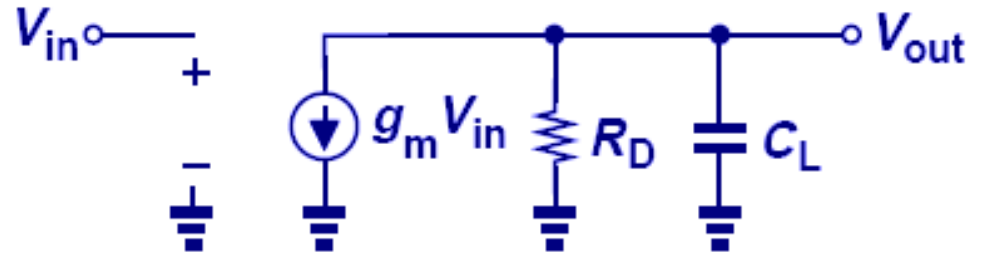


(b)

$$V_{out} = -g_m V_{in} \left(R_D \parallel \frac{1}{C_L s} \right)$$

- The capacitive load, C_L , is the culprit for gain roll-off since at high frequency, it will “steal” away some signal current and shunt it to ground.

Frequency Response of the CS Stage

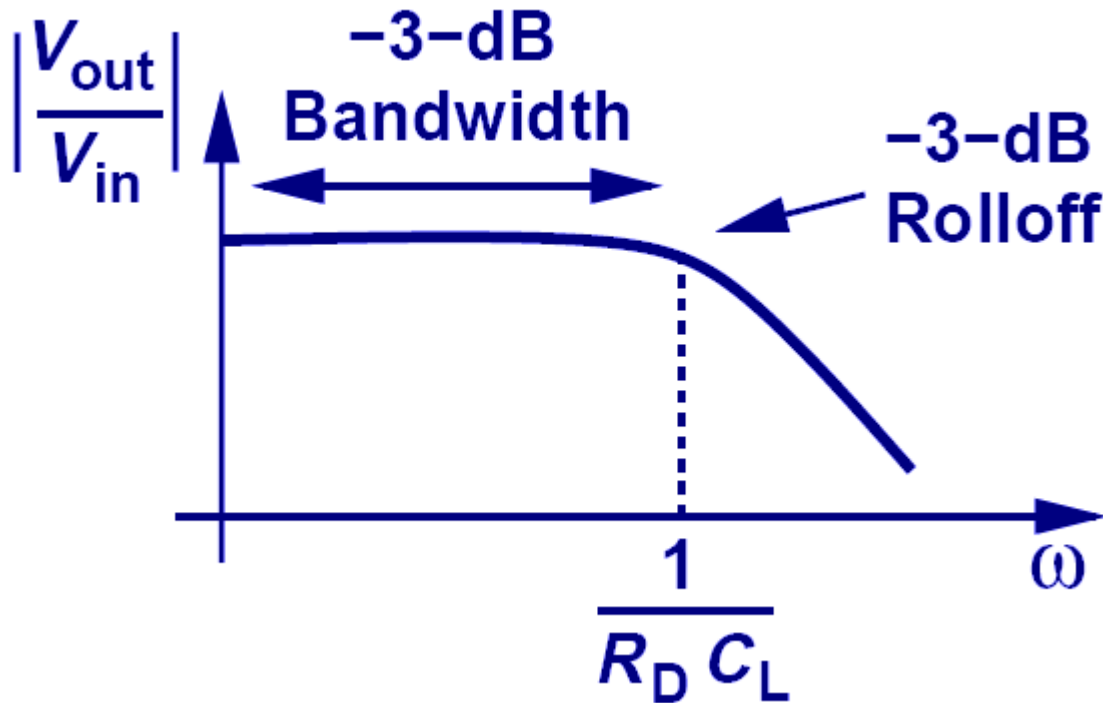


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{R_D^2 C_L^2 \omega^2 + 1}}$$

$$\omega = 1/(R_D C_L) \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{2}}$$

$$20 \log(1/\sqrt{2}) = -3 \text{ dB}$$

- At low frequency, the capacitor is effectively open and the gain is flat. As frequency increases, the capacitor tends to a short and the gain starts to decrease. A special frequency is $\omega = 1/(R_D C_L)$, where the gain drops by 3dB.

Example: Figure of Merit

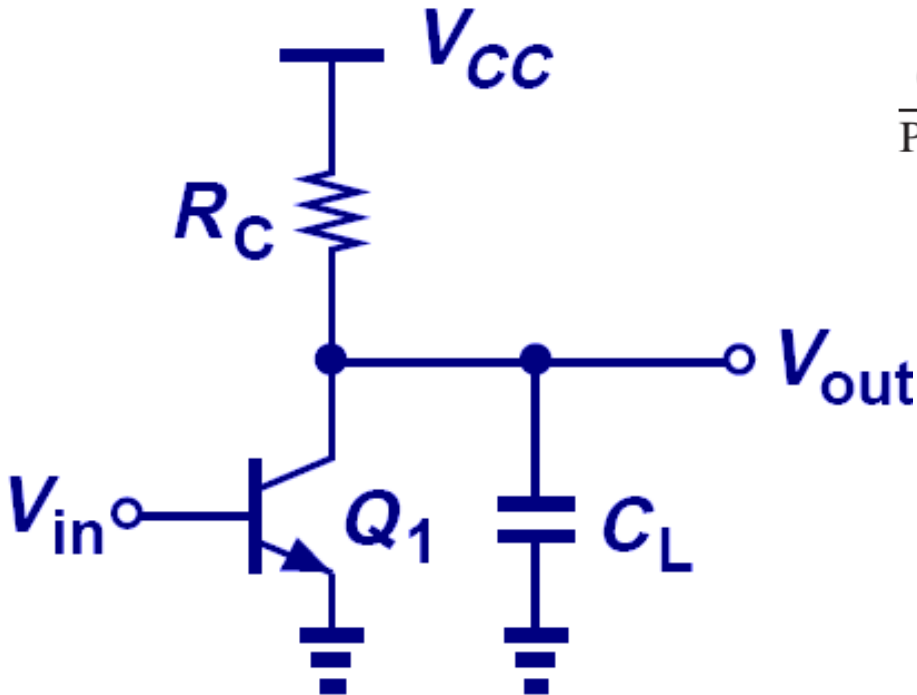


$$\frac{\text{Gain} \times \text{Bandwidth}}{\text{Power Consumption}} = \frac{\frac{I_C}{V_T} R_C \times \frac{1}{R_C C_L}}{I_C \cdot V_{CC}}$$
$$= \frac{1}{V_T \cdot V_{CC}} \frac{1}{C_L}.$$

$$F.O.M. = \frac{1}{V_T V_{CC} C_L}$$


$$V_T = \frac{kT}{q} = 25.8mV$$

- This metric quantifies a circuit's gain, bandwidth, and power dissipation. In the bipolar case, low temperature, supply, and load capacitance mark a superior figure of merit.

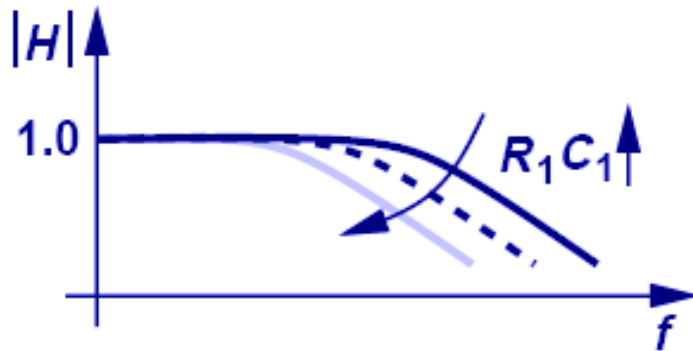Example: Relationship between Frequency Response and Step Response



(a)

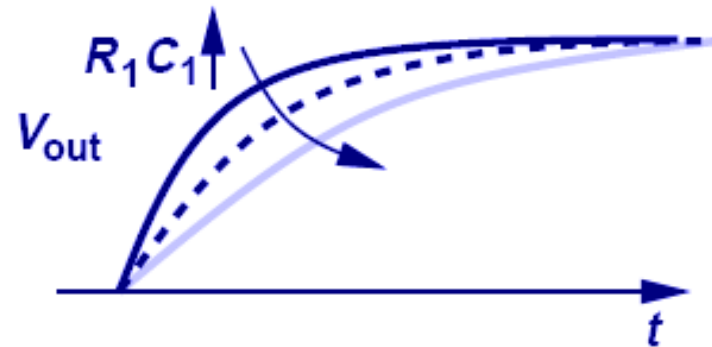

(b)

$$|H(s = j\omega)| = \frac{1}{\sqrt{R_1^2 C_1^2 \omega^2 + 1}}$$

$$V_{out}(t) = V_0 \left(1 - \exp \frac{-t}{R_1 C_1} \right) u(t)$$


➤ The relationship is such that as R_1C_1 increases, the bandwidth *drops* and the step response becomes *slower*.

Bode Plot

$$H(s) = A_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right) \dots}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \dots}$$

- When we hit a zero, ω_{zj} , the Bode magnitude rises with a slope of +20dB/dec.
- When we hit a pole, ω_{pj} , the Bode magnitude falls with a slope of -20dB/dec


Example: Bode Plot

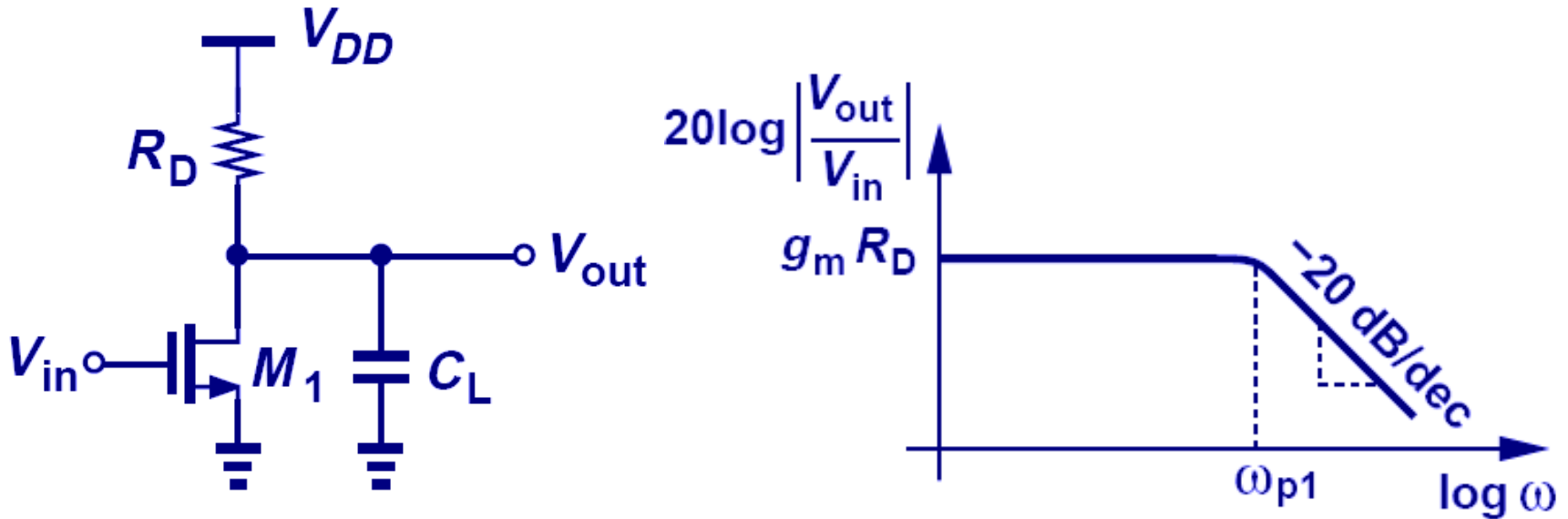

$$|\omega_{p1}| = \frac{1}{R_D C_L}$$

- The circuit only has one pole (no zero) at $1/(R_D C_L)$, so the slope drops from 0 to -20 dB/dec as we pass ω_{p1} .

Pole Identification Example I

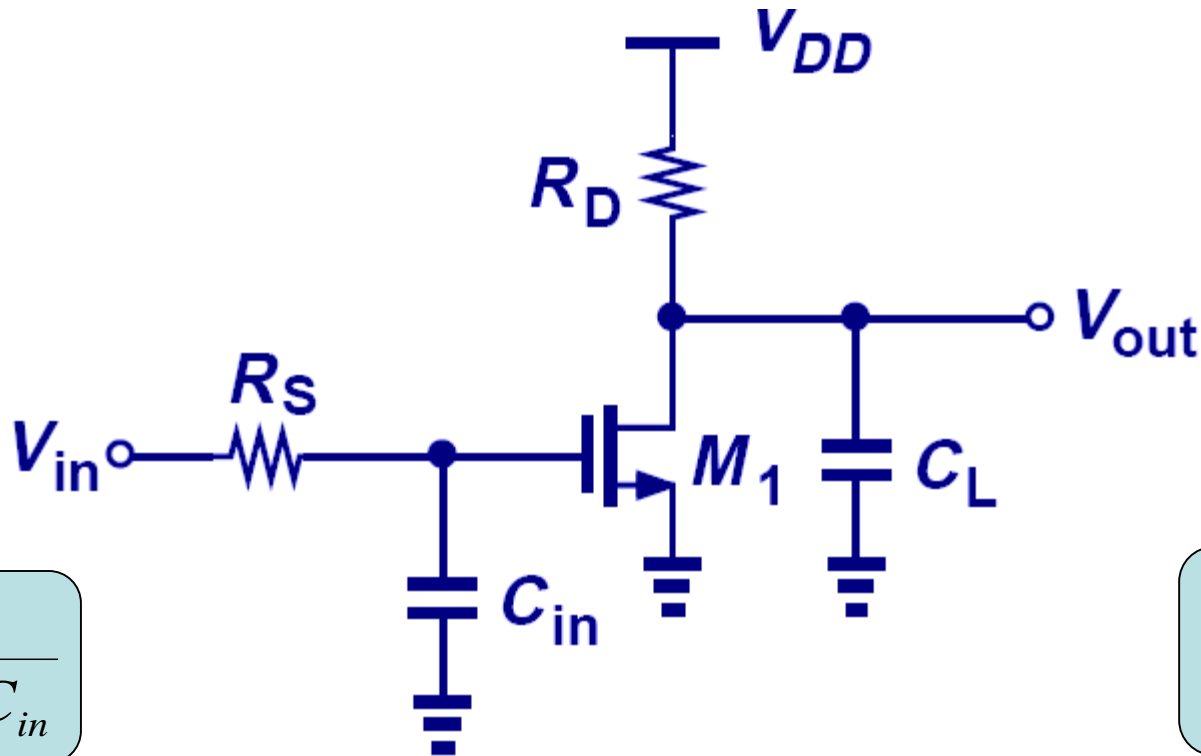


$$|\omega_{p1}| = \frac{1}{R_S C_{in}}$$

$$|\omega_{p2}| = \frac{1}{R_D C_L}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{\left(1 + \omega^2 / \omega_{p1}^2\right) \left(1 + \omega^2 / \omega_{p2}^2\right)}}$$


Pole Identification Example II

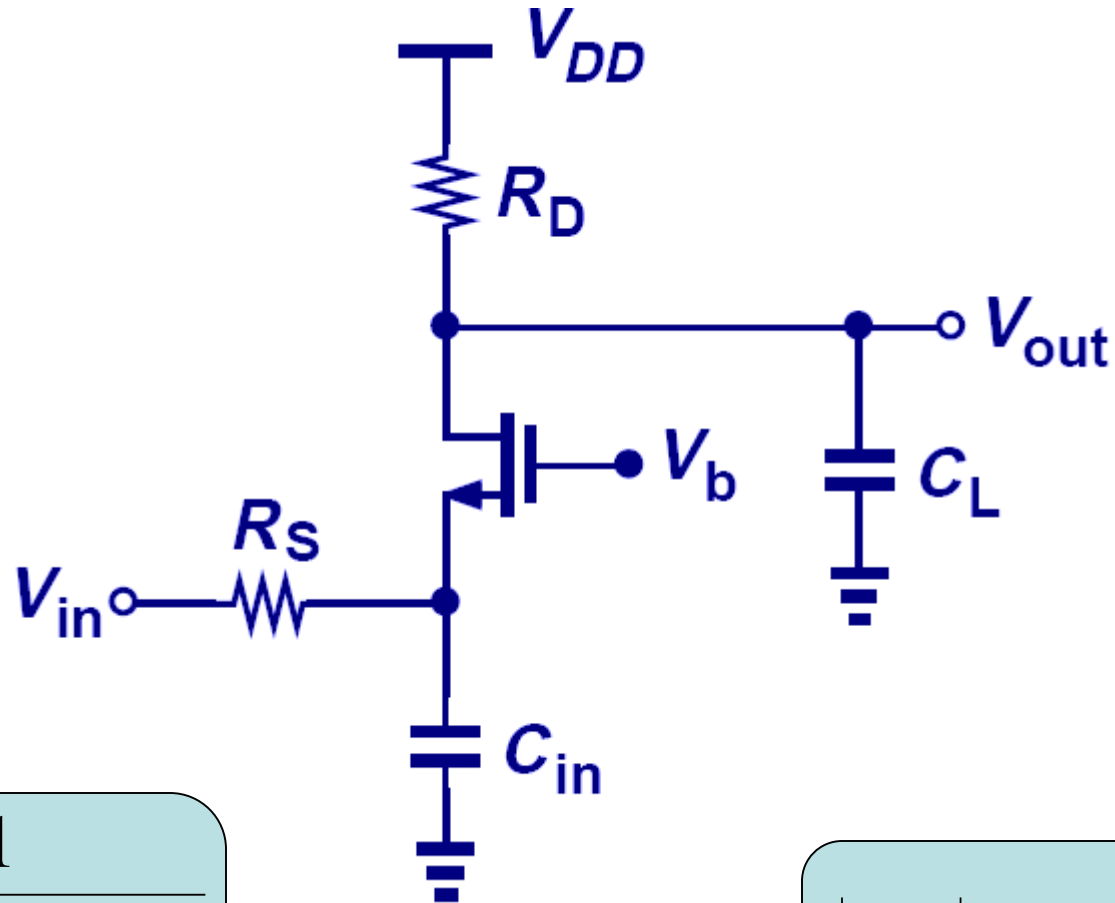

$$|\omega_{p1}| = \frac{1}{\left(R_S \parallel \frac{1}{g_m} \right) C_{in}}$$


$$|\omega_{p2}| = \frac{1}{R_D C_L}$$

Circuit with Floating Capacitor

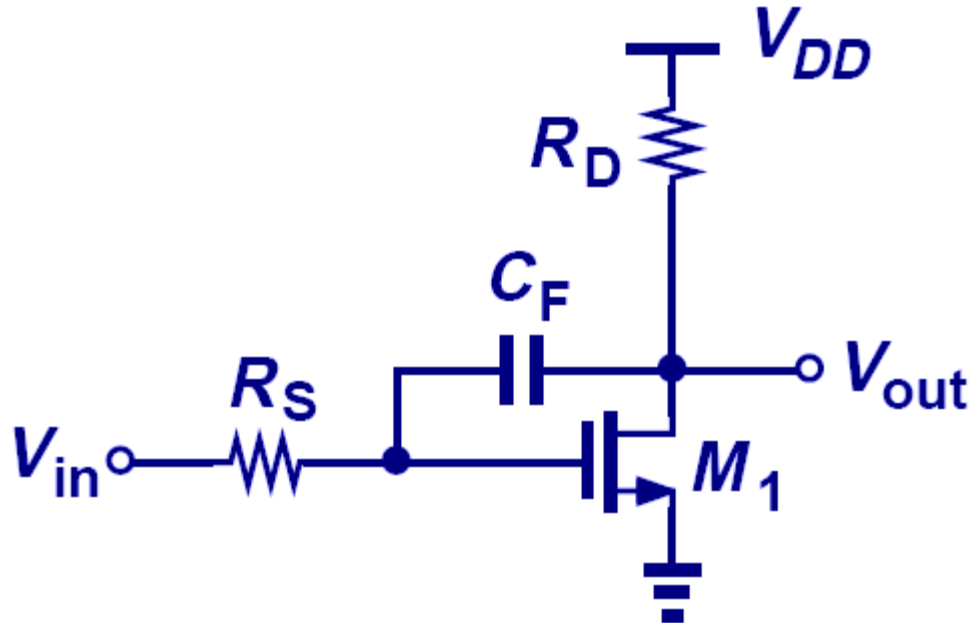

- The pole of a circuit is computed by finding the effective resistance and capacitance from a node to GROUND.
- The circuit above creates a problem since neither terminal of C_F is grounded.

Miller's Theorem

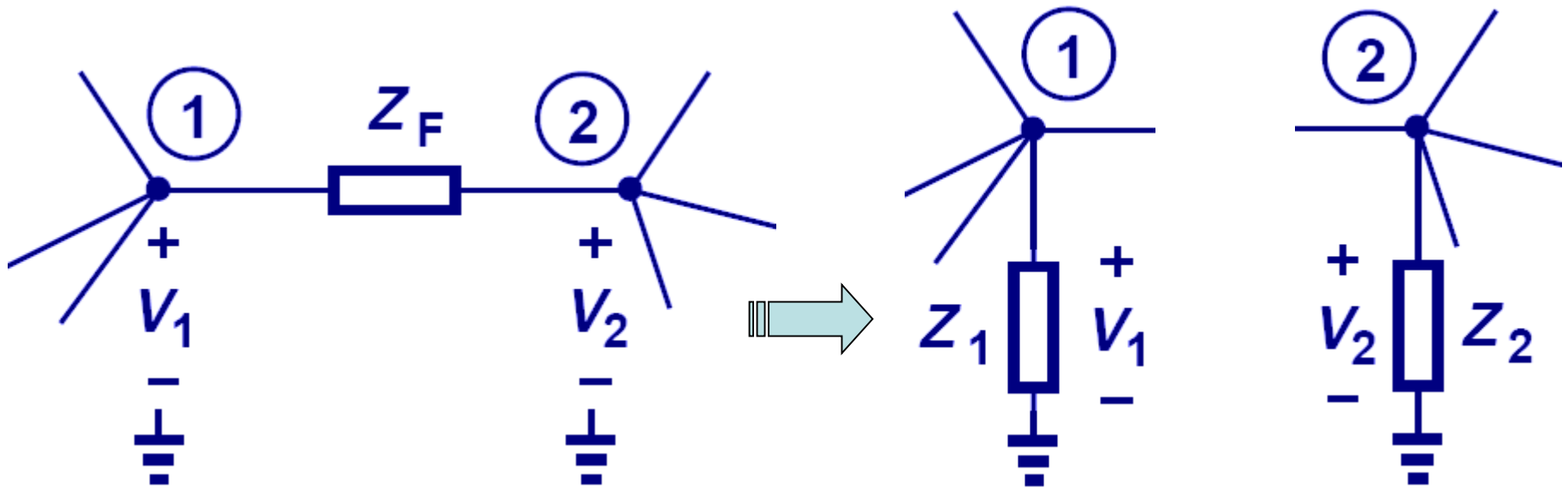


$$Z_1 = \frac{Z_F}{1 - A_v}$$

$$Z_2 = \frac{Z_F}{1 - 1/A_v}$$



➤ If A_v is the gain from node 1 to 2, then a floating impedance Z_F can be converted to two grounded impedances Z_1 and Z_2 .

Miller Multiplication

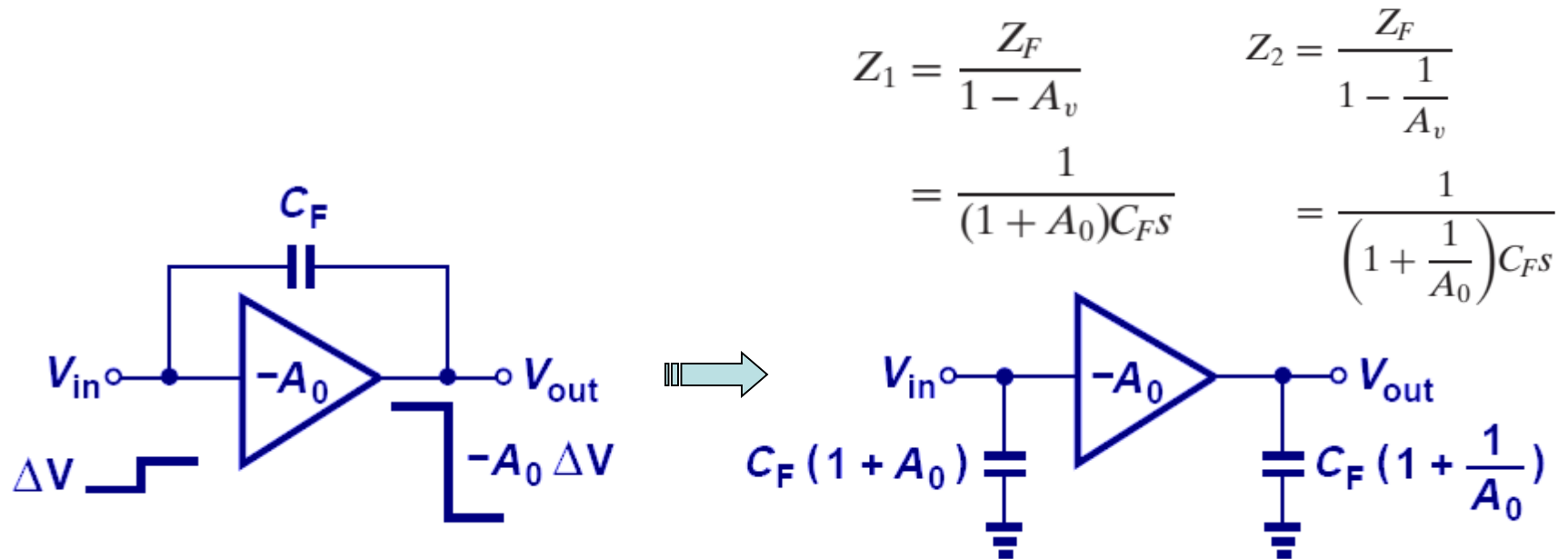

- With Miller's theorem, we can separate the floating capacitor. However, the input capacitor is larger than the original floating capacitor. We call this Miller multiplication.


Example: Miller Theorem

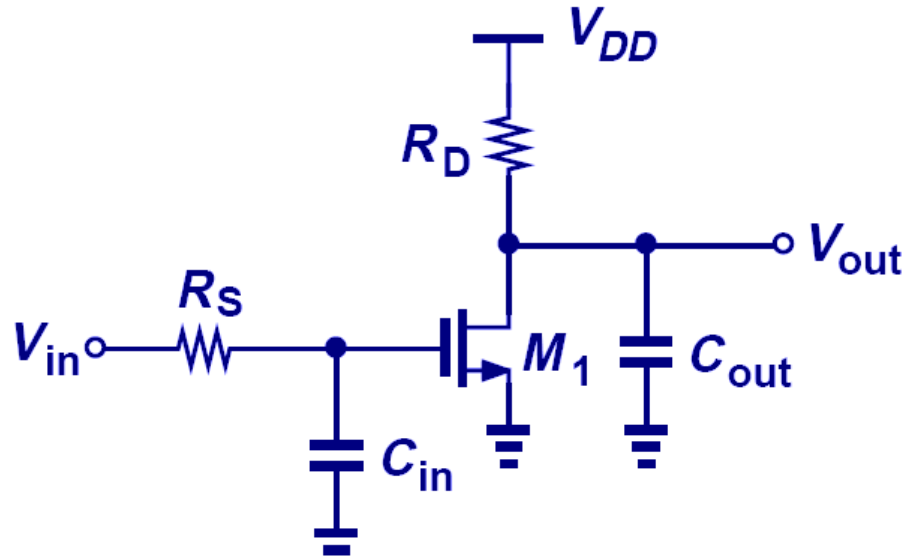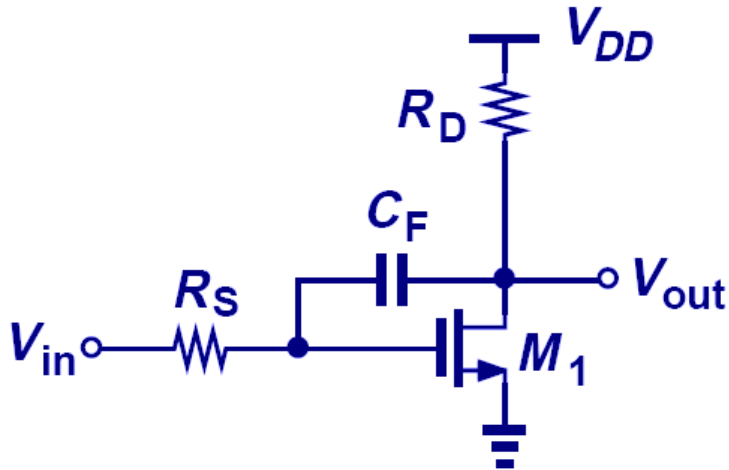


$$\omega_{in} = \frac{1}{R_S (1 + g_m R_D) C_F}$$

$$\omega_{out} = \frac{1}{R_D \left(1 + \frac{1}{g_m R_D} \right) C_F}$$

High-Pass Filter Response

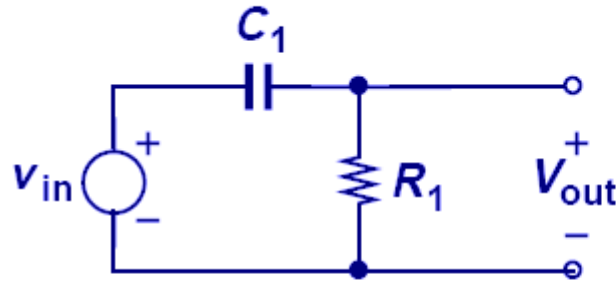

(a)

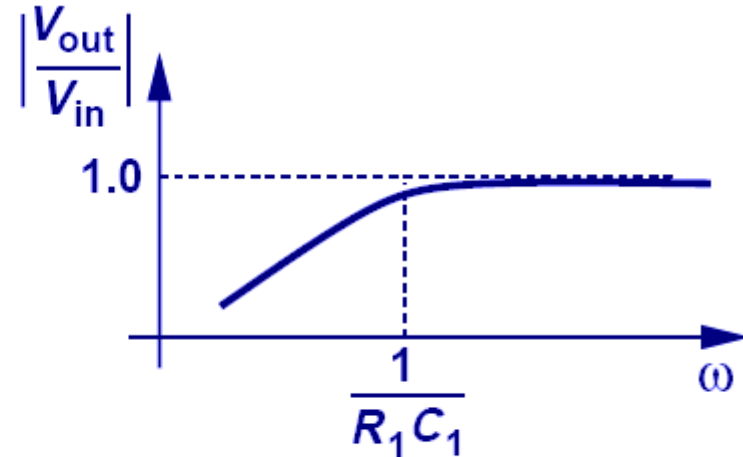


(b)

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{R_1 C_1 \omega}{\sqrt{R_1^2 C_1^2 \omega^2 + 1}}$$

- The voltage division between a resistor and a capacitor can be configured such that the gain at low frequency is reduced.

Example: Audio Amplifier

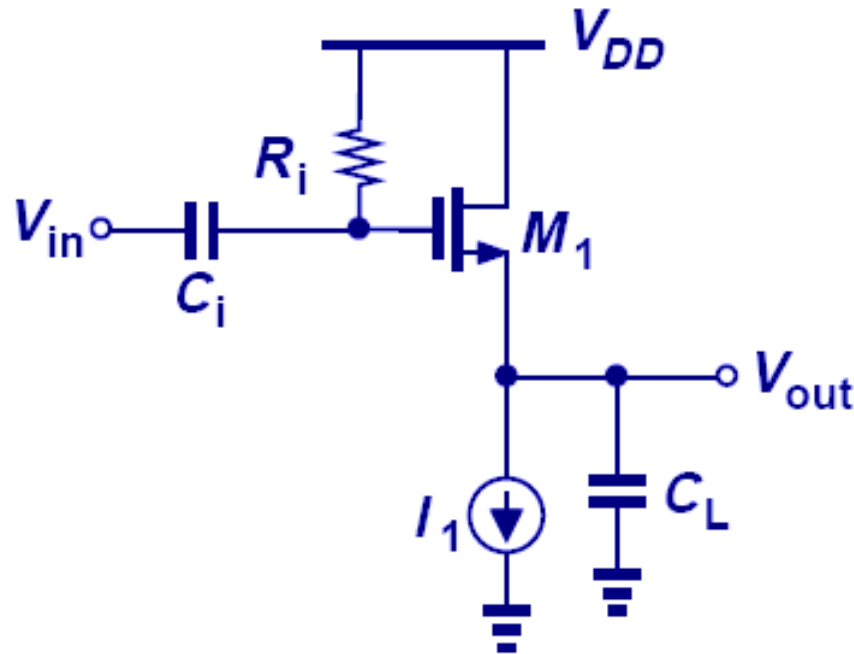

$$C_i = 79.6nF$$


$$C_L = 39.8nF$$

$$R_i = 100K\Omega$$

$$g_m = 1/200\Omega$$


- In order to successfully pass audio band frequencies (20 Hz-20 KHz), large input and output capacitances are needed.

Capacitive Coupling vs. Direct Coupling

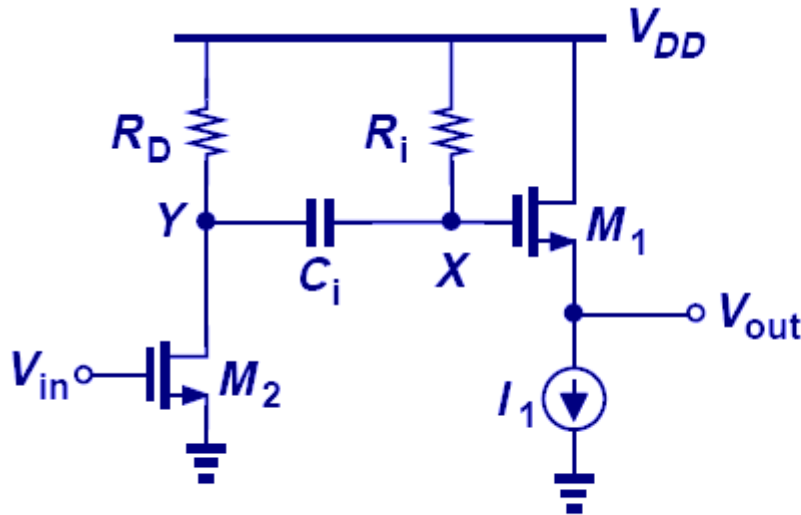

(a)

Capacitive Coupling

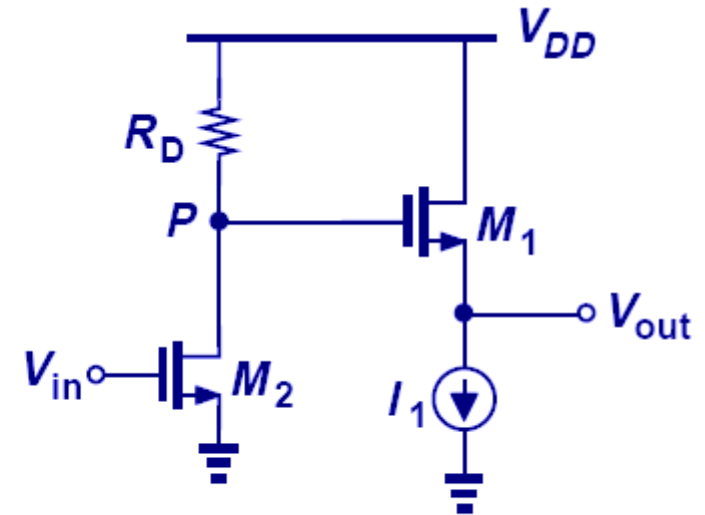


(b)


Direct Coupling

- Capacitive coupling, also known as AC coupling, passes AC signals from Y to X while blocking DC contents.
- This technique allows independent bias conditions between stages. Direct coupling does not.

Typical Frequency Response

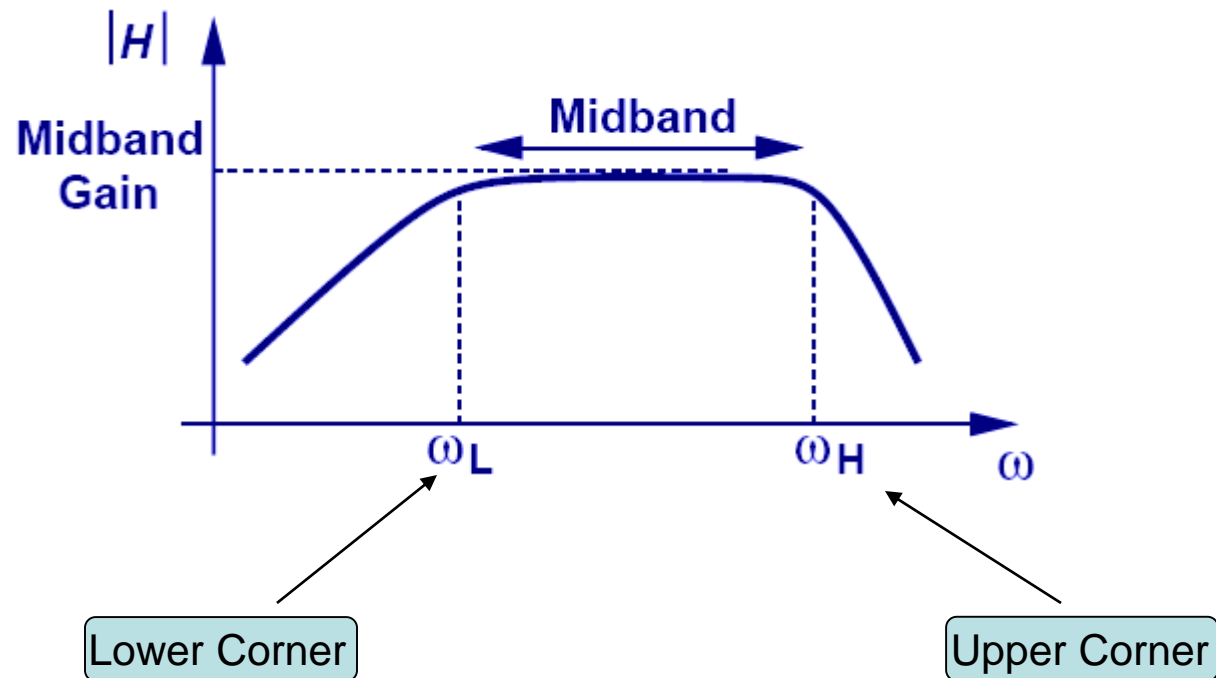


MOS Intrinsic Capacitances

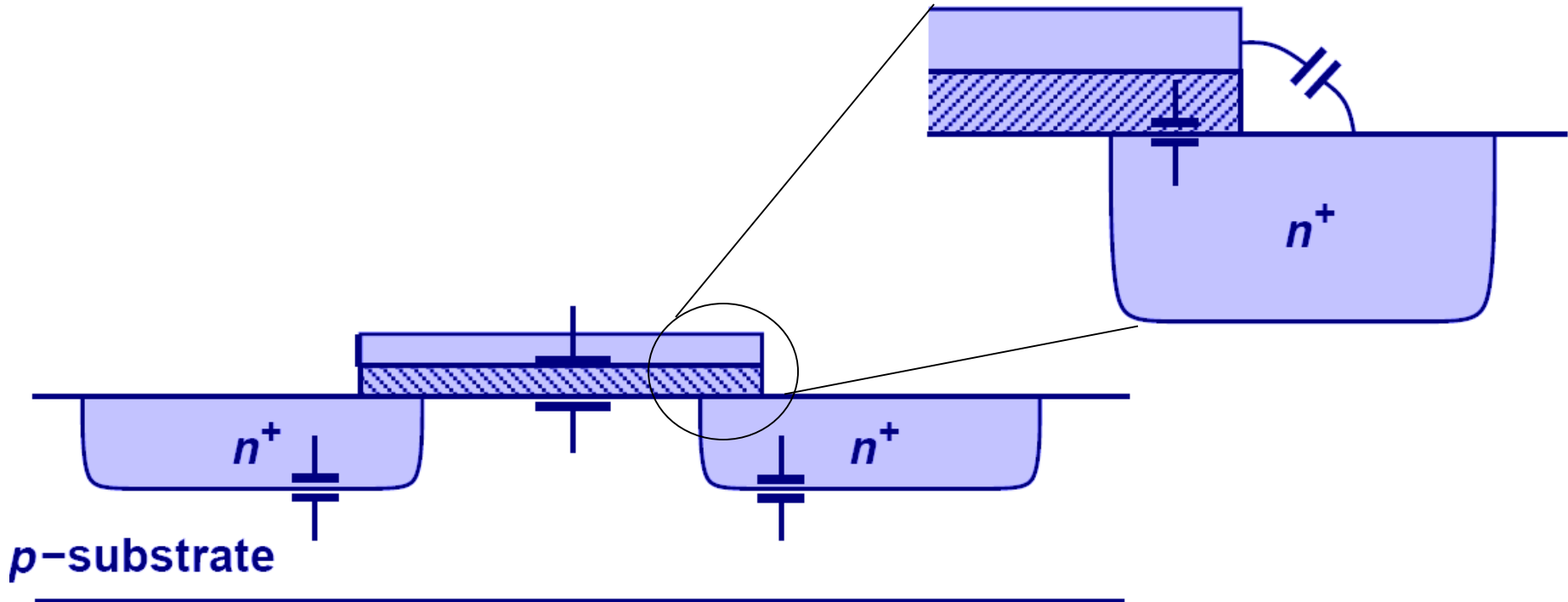


- For a MOS, there exist oxide capacitance from gate to channel, junction capacitances from source/drain to substrate, and overlap capacitance from gate to source/drain.

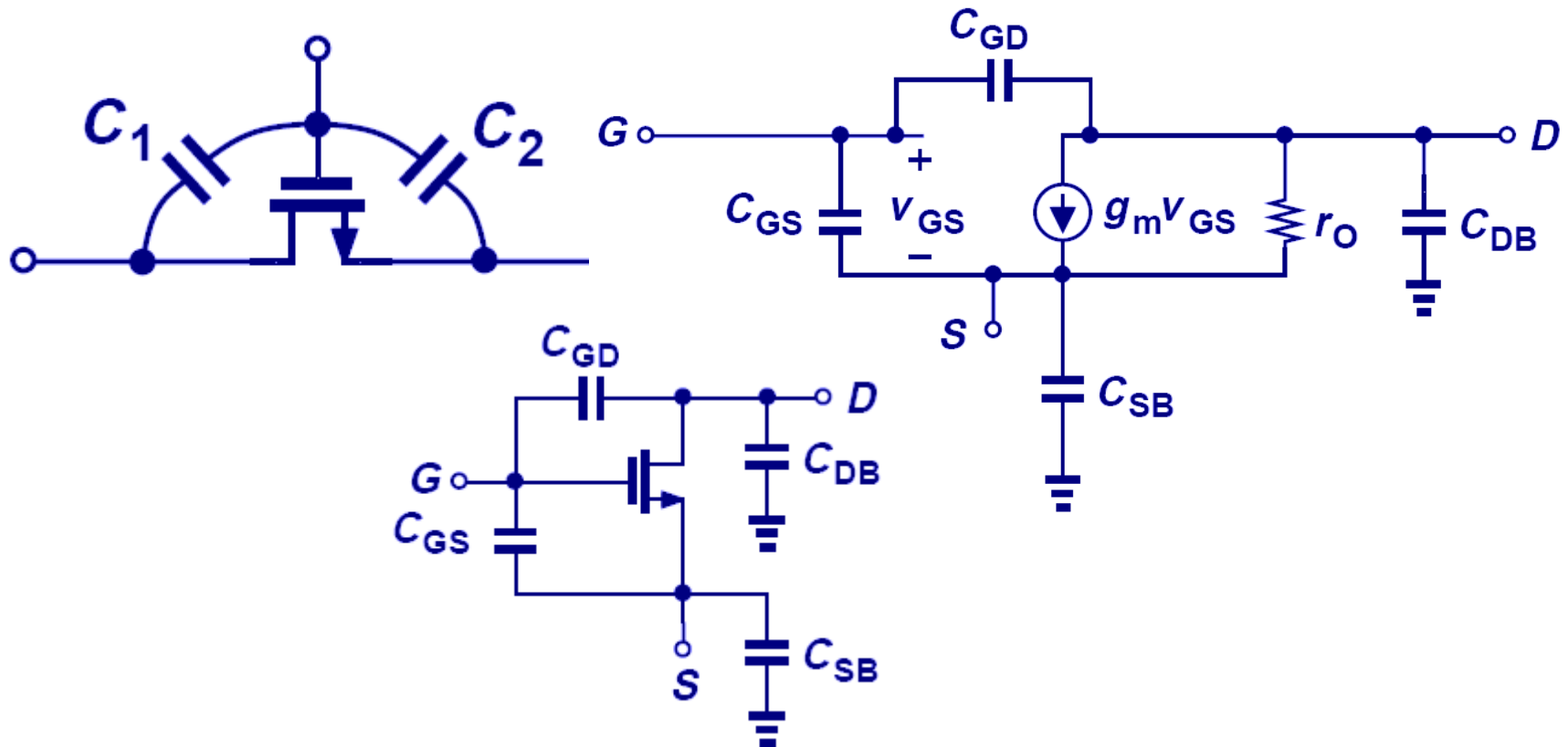Gate Oxide Capacitance Partition and Full Model




- The gate oxide capacitance is often partitioned between source and drain. In saturation, $C_2 \sim C_{\text{gate}}$, and $C_1 \sim 0$. They are in parallel with the overlap capacitance to form C_{GS} and C_{GD} .


Example: Capacitance Identification

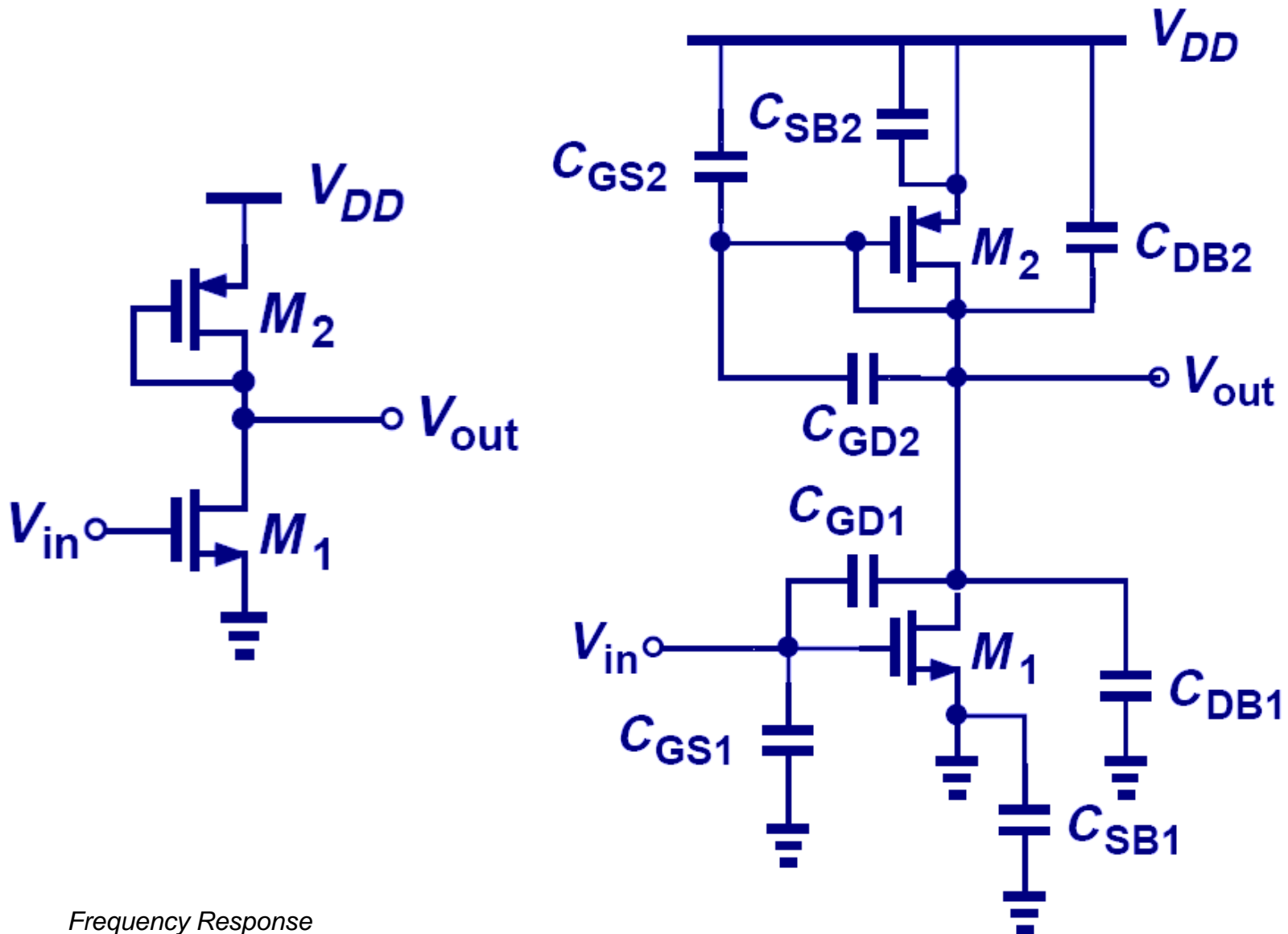

Transit Frequency

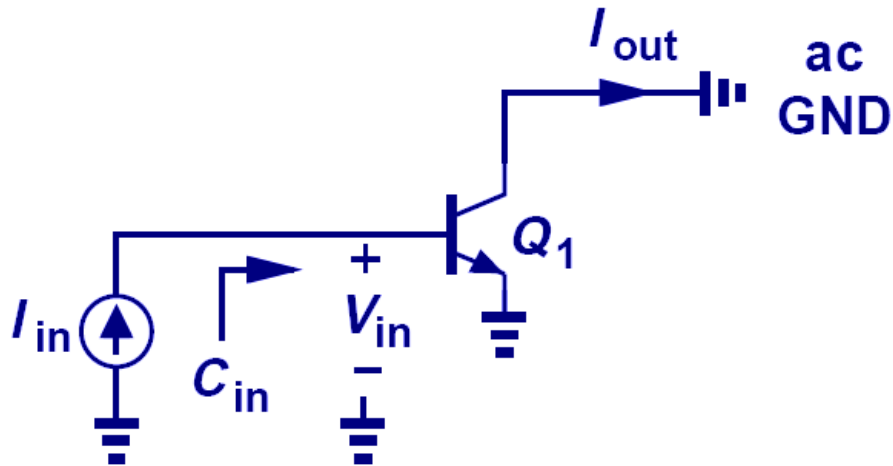


$$2\pi f_T = \frac{g_m}{C_\pi}$$

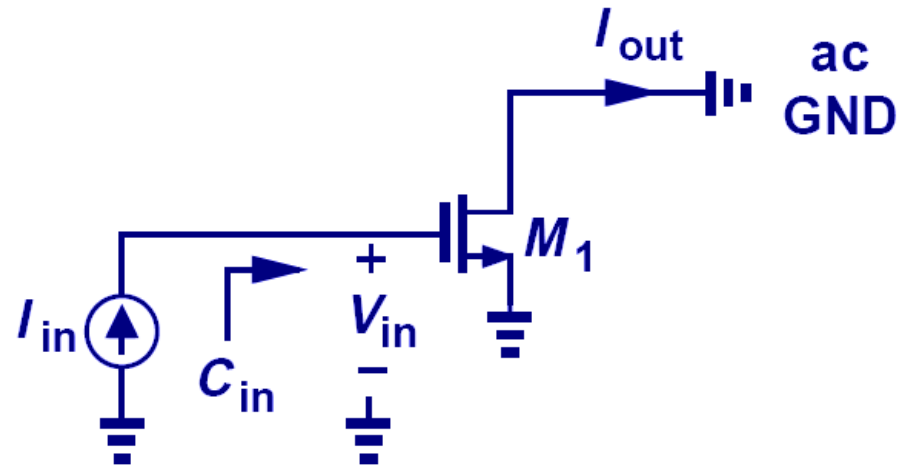

$$2\pi f_T = \frac{g_m}{C_{GS}}$$

➤ Transit frequency, f_T , is defined as the frequency where the current gain from input to output drops to 1.

Example: Transit Frequency Calculation

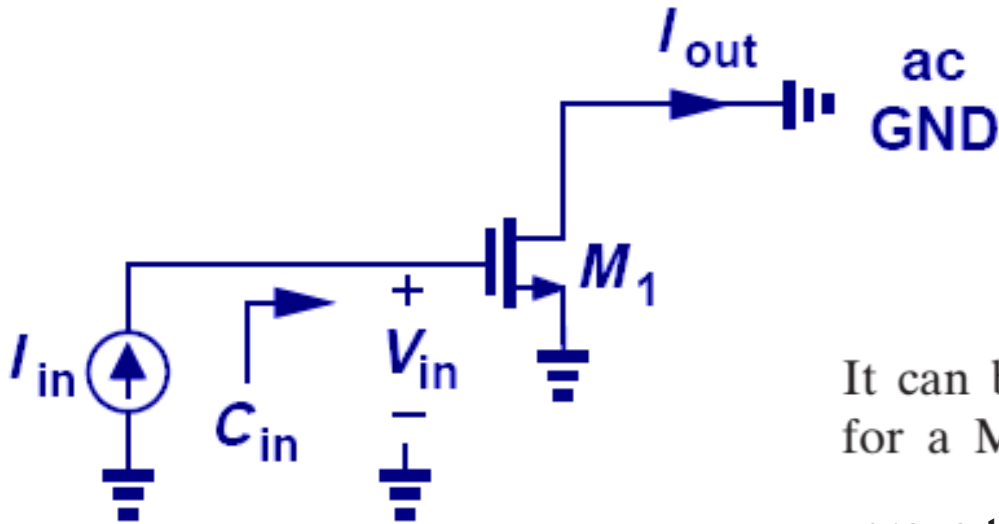

It can be shown that $C_{GS} \approx (2/3)WLC_{ox}$ for a MOSFET operating in saturation.

prove that:

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

Note that f_T increases with the overdrive voltage and the $\frac{1}{L^2}$

$$L = 65nm$$

$$V_{GS} - V_{TH} = 100mV$$

$$\mu_n = 400cm^2/(V.s)$$

$$f_T = 226GHz$$

Example: Transit Frequency Calculation

- The minimum channel length of MOSFETs has been scaled from 1 μm in the late 1980s to 65 nm today. Also, the inevitable reduction of the supply voltage has reduced the gate-source overdrive voltage from about 400 mV to 100 mV. By what factor has the f_T of MOSFETs increased?

Solution:

It can be proved that
$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

Thus, the transit frequency has increased by approximately a factor of 59. For example, if $\mu_n = 400 \text{ cm}^2/(\text{V}\cdot\text{s})$, then 65 nm devices having an overdrive of 100 mV exhibit an f_T of 226 GHz.


Analysis Summary

- The frequency response refers to the magnitude of the transfer function.
- Bode's approximation simplifies the plotting of the frequency response if poles and zeros are known.
- In general, it is possible to associate a pole with each node in the signal path.
- Miller's theorem helps to decompose floating capacitors into grounded elements.
- Bipolar and MOS devices exhibit various capacitances that limit the speed of circuits.

High Frequency Circuit Analysis Procedure

- Determine which capacitor impact the low-frequency region of the response and calculate the low-frequency pole (neglect transistor capacitance).
- Calculate the midband gain by replacing the capacitors with short circuits (neglect transistor capacitance).
- Include transistor capacitances.
- Merge capacitors connected to AC grounds and omit those that play no role in the circuit.
- Determine the high-frequency poles and zeros.
- Plot the frequency response using Bode's rules or exact analysis.

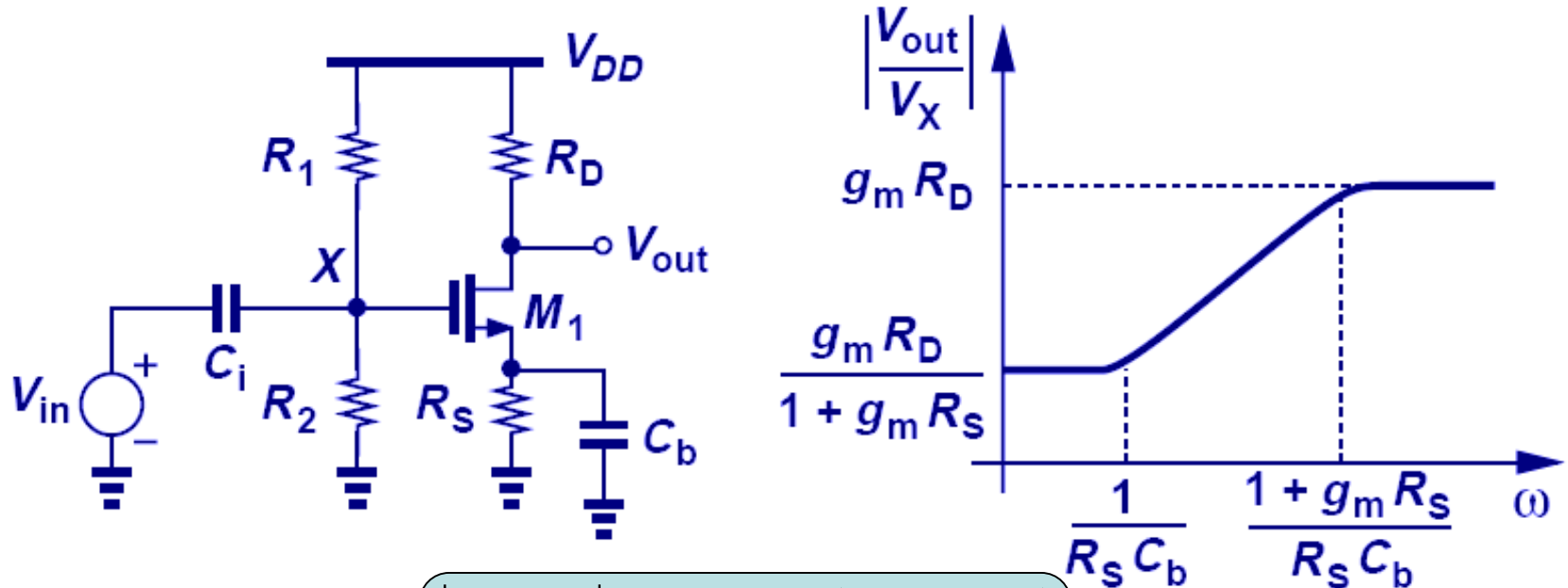
Frequency Response of CS Stage with Bypassed Degeneration






$$\left| \frac{V_{out}}{V_X}(s) \right| = \frac{-g_m R_D (R_S C_b s + 1)}{R_S C_b s + g_m R_S + 1}$$

- In order to increase the midband gain, a capacitor C_b is placed in parallel with R_S .
- The pole frequency must be well below the lowest signal frequency to avoid the effect of degeneration.


Small signal equivalents of CS stage

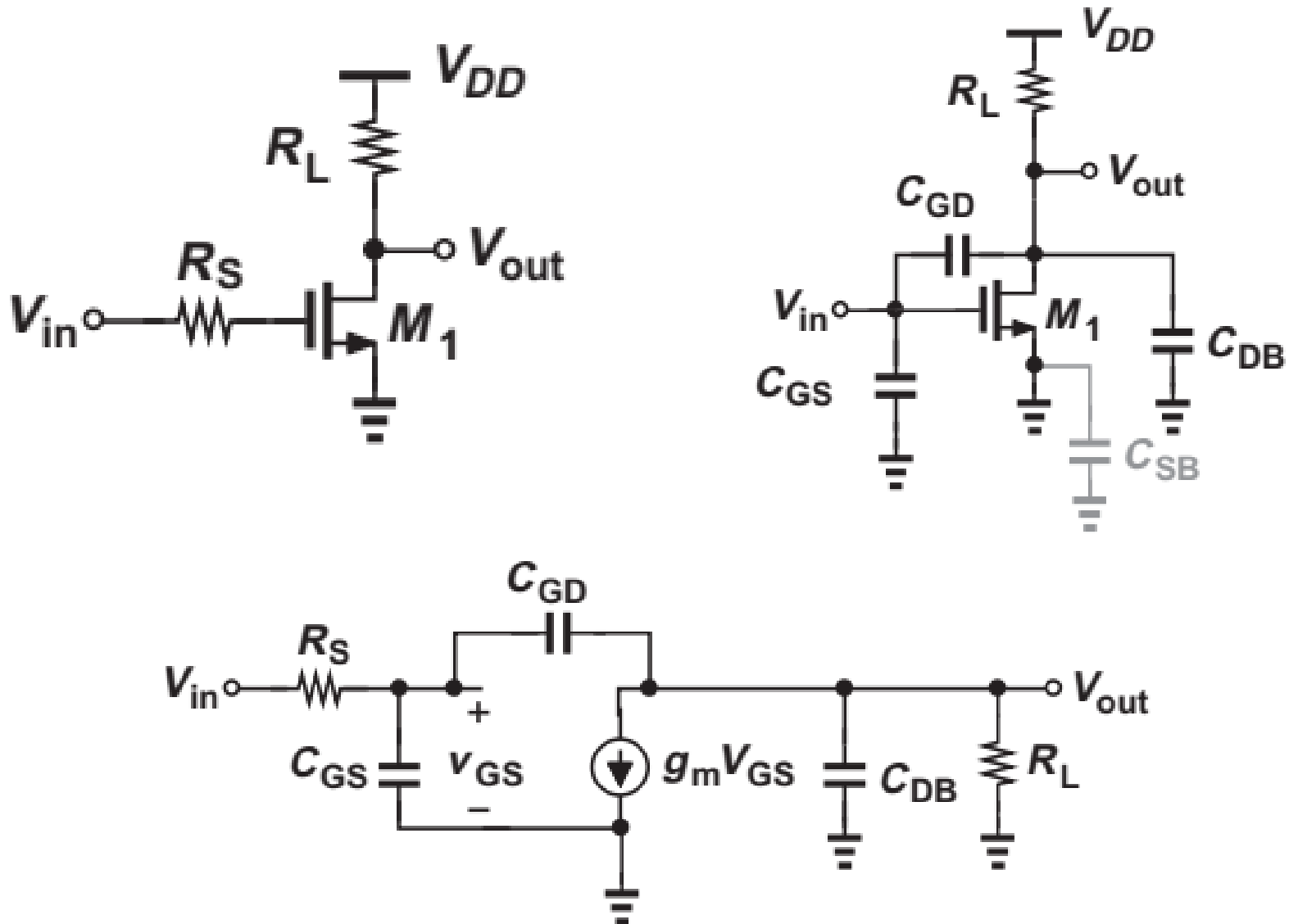

Unified Model for CE and CS Stages

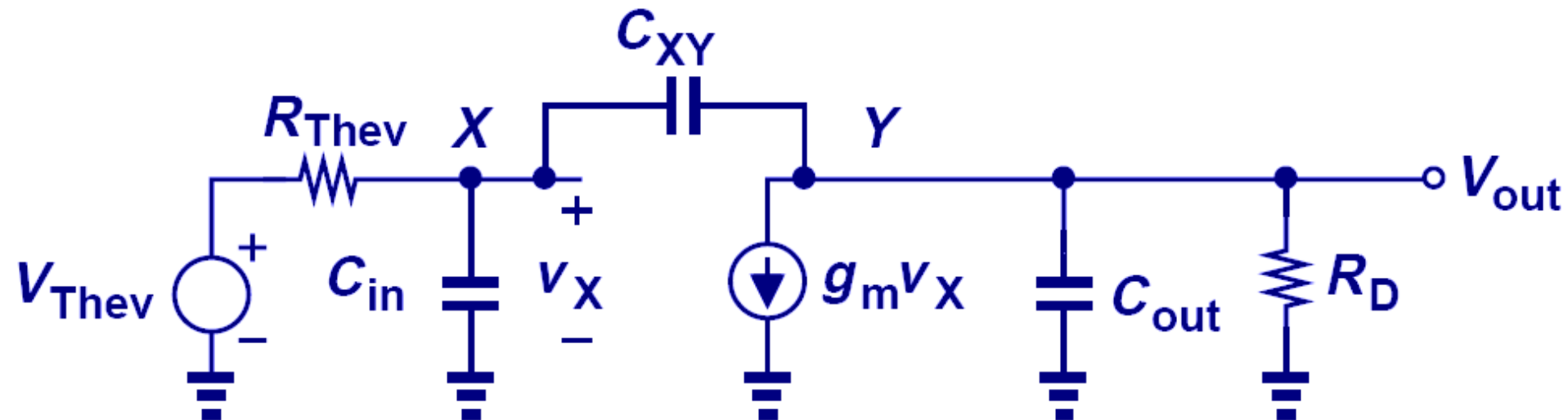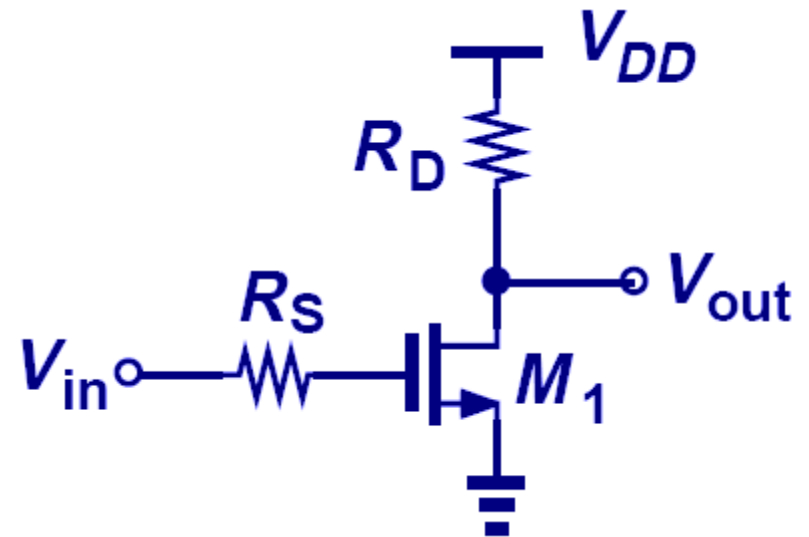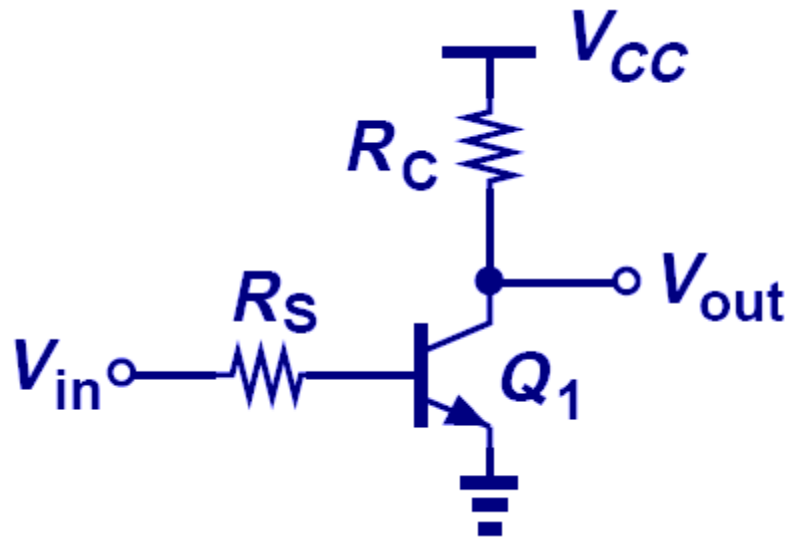

Unified Model Using Miller's Theorem

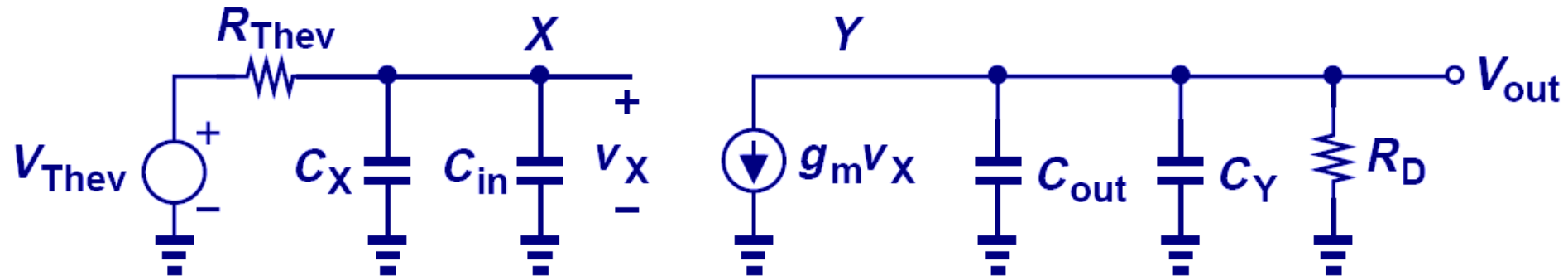

CS Stage

$$V_{Thev} = V_{in}$$

$$R_{Thev} = R_S$$


$$C_X = C_{GD} (1 + g_m R_D)$$

$$C_Y = C_{GD} \left(1 + \frac{1}{g_m R_D} \right)$$

$$|\omega_{p,in}| = \frac{1}{R_{Thev} [C_{in} + (1 + g_m R_L) C_{XY}]}$$

$$|\omega_{p,out}| = \frac{1}{R_L \left[C_{out} + \left(1 + \frac{1}{g_m R_L} \right) C_{XY} \right]}$$

Example: Half Width CS Stage

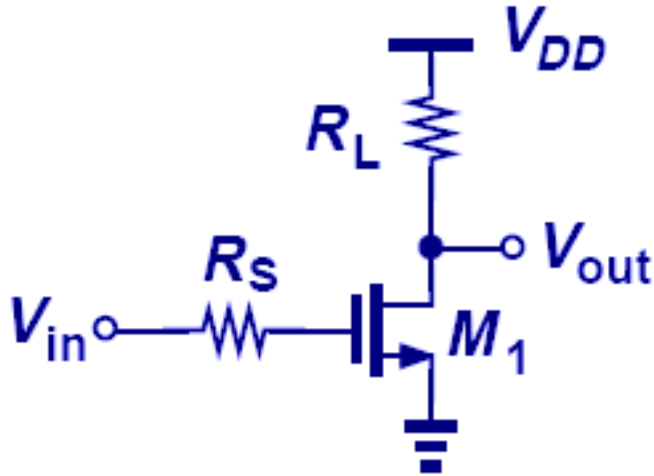

$$W \downarrow 2X$$

All capacitors are halved

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}.$$

$$|\omega_{p,in}| = \frac{1}{R_S \left[\frac{C_{in}}{2} + \left(1 + \frac{g_m R_L}{2} \right) \frac{C_{XY}}{2} \right]}$$

$$|\omega_{p,out}| = \frac{1}{R_L \left[\frac{C_{out}}{2} + \left(1 + \frac{2}{g_m R_L} \right) \frac{C_{XY}}{2} \right]}$$


Direct Analysis of CS Stages

$$|\omega_z| = \frac{g_m}{C_{XY}}$$

$$|\omega_{p1}| = \frac{1}{(1 + g_m R_L) C_{XY} R_{Thev} + R_{Thev} C_{in} + R_L (C_{XY} + C_{out})}$$
$$|\omega_{p2}| = \frac{(1 + g_m R_L) C_{XY} R_{Thev} + R_{Thev} C_{in} + R_L (C_{XY} + C_{out})}{R_{Thev} R_L (C_{in} C_{XY} + C_{out} C_{XY} + C_{in} C_{out})}$$

➤ **Direct analysis yields different pole locations and an extra zero.**


Example: CS Direct Analysis

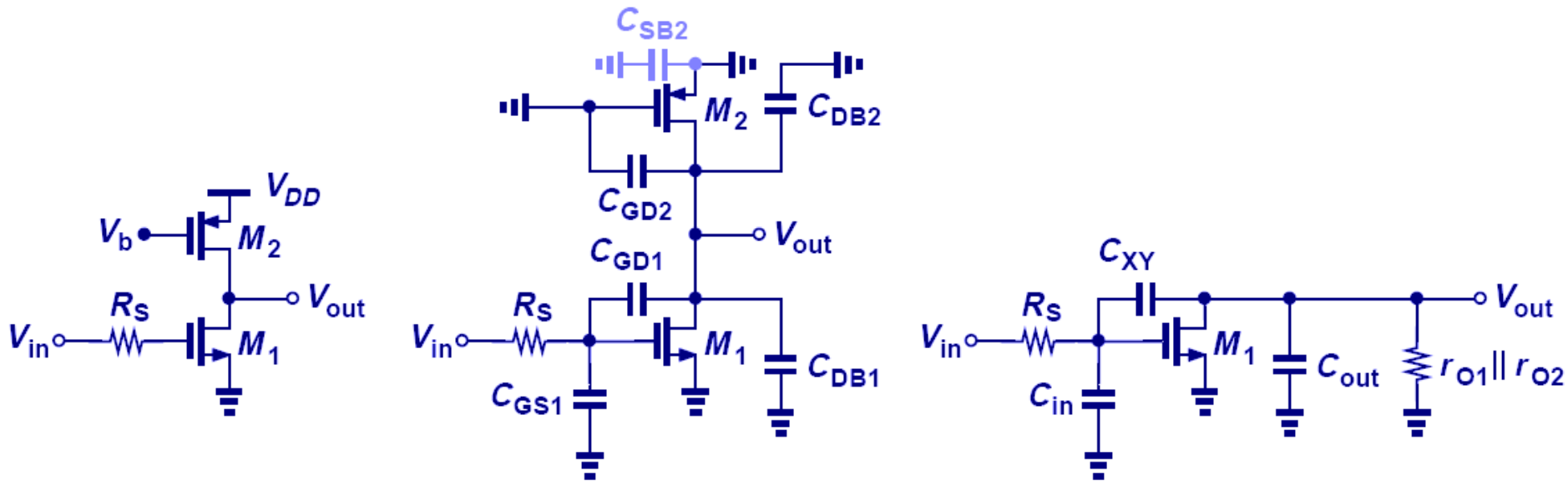

$$\omega_{p1} \approx \frac{1}{[1 + g_{m1}(r_{O1} \parallel r_{O2})]C_{XY}R_S + R_S C_{in} + (r_{O1} \parallel r_{O2})(C_{XY} + C_{out})}$$

$$\omega_{p2} \approx \frac{[1 + g_{m1}(r_{O1} \parallel r_{O2})]C_{XY}R_S + R_S C_{in} + (r_{O1} \parallel r_{O2})(C_{XY} + C_{out})}{R_S (r_{O1} \parallel r_{O2})(C_{in} C_{XY} + C_{out} C_{XY} + C_{in} C_{out})}$$

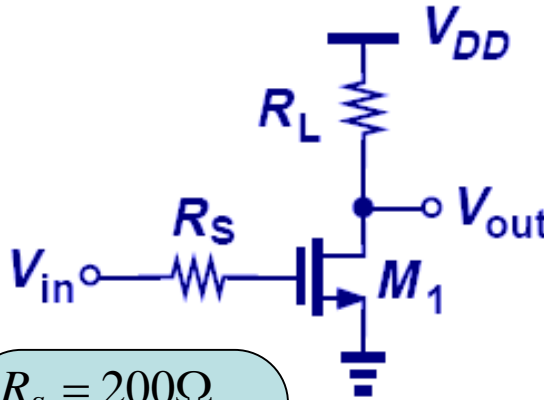Example: Comparison Between Different Methods



$$R_S = 200\Omega$$

$$C_{GS} = 250\text{fF}$$


$$C_{GD} = 80\text{fF}$$

$$C_{DB} = 100\text{fF}$$

$$g_m = (150\Omega)^{-1}$$

$$\lambda = 0$$

$$R_L = 2\text{K}\Omega$$

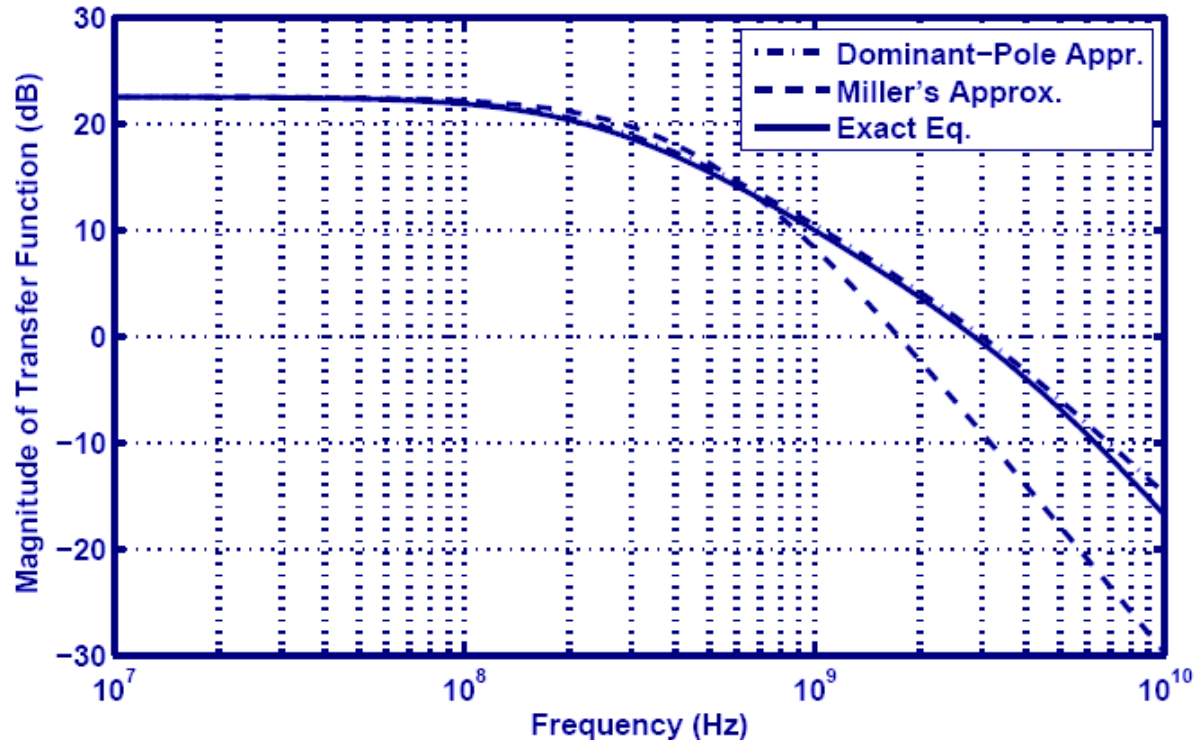

Miller's

$$|\omega_{p,in}| = 2\pi \times (571\text{MHz})$$

$$|\omega_{p,out}| = 2\pi \times (428\text{MHz})$$

Frequency Response

Exact

$$|\omega_{p,in}| = 2\pi \times (264\text{MHz})$$


$$|\omega_{p,out}| = 2\pi \times (4.53\text{GHz})$$

Dominant Pole

$$|\omega_{p,in}| = 2\pi \times (249\text{MHz})$$


$$|\omega_{p,out}| = 2\pi \times (4.79\text{GHz})$$

Input Impedance of CS Stages

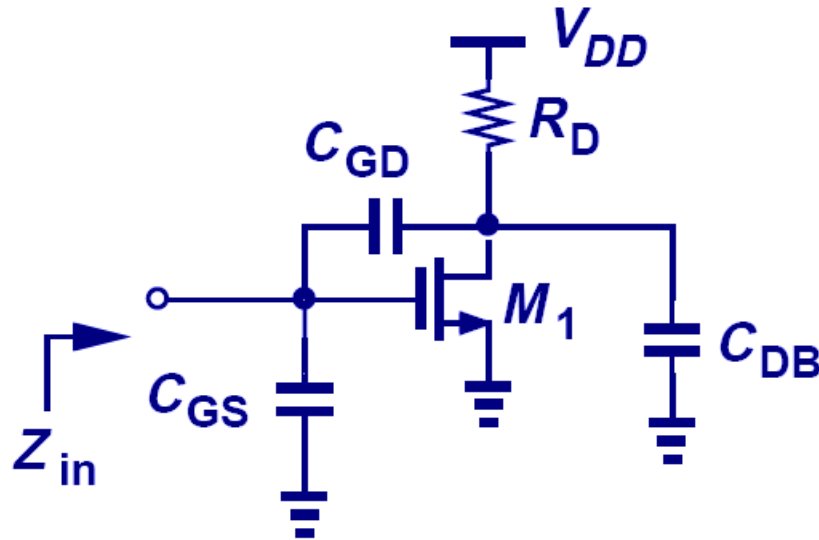

$$Z_{in} \approx \frac{1}{[C_{GS} + (1 + g_m R_D)C_{GD}]s}$$

Frequency Response of CG Stage

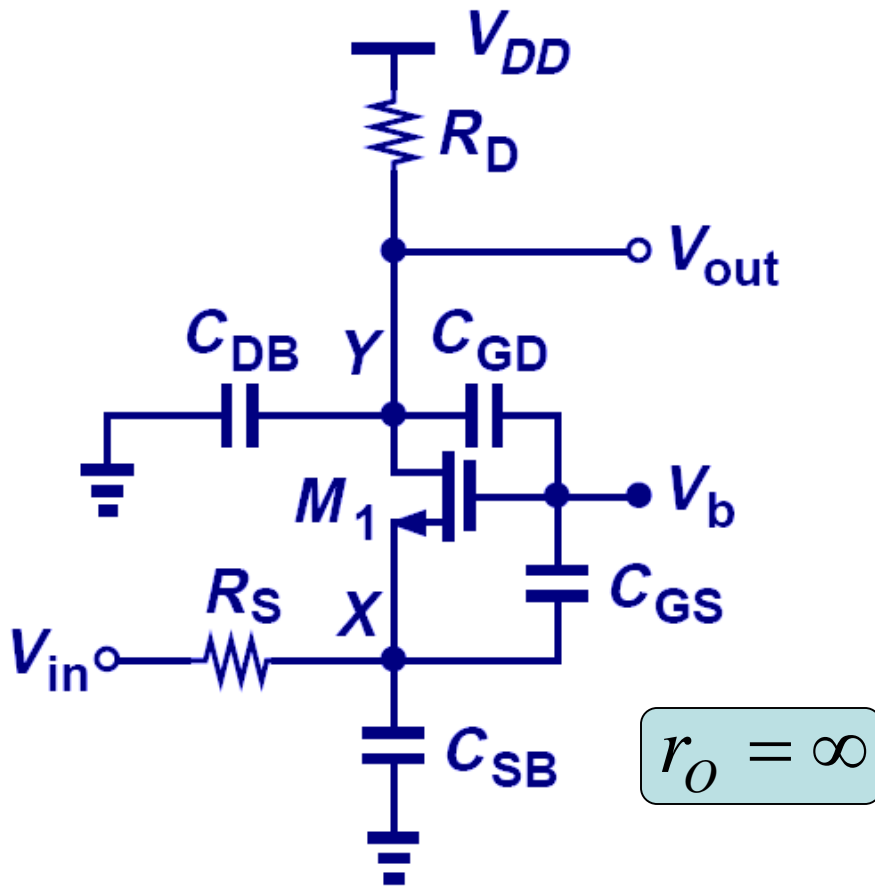

$$\omega_{p,X} = \frac{1}{\left(R_S \parallel \frac{1}{g_m} \right) C_X}$$


$$C_X = C_{GS} + C_{SB}$$

$$\omega_{p,Y} = \frac{1}{R_D C_Y}$$

$$C_Y = C_{GD} + C_{DB}$$



➤ Similar to a CB stage, the input pole is on the order of f_T , so rarely a speed bottleneck.

Example: CG Stage Pole Identification

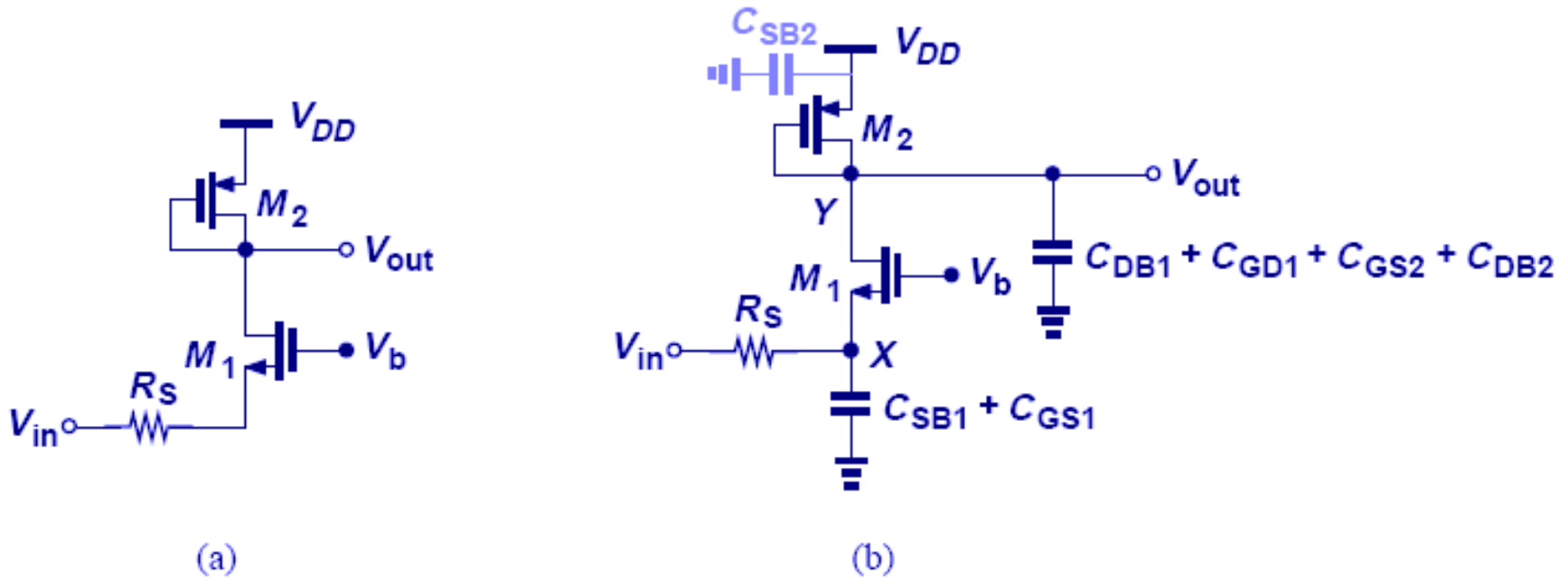

$$\omega_{p,X} = \frac{1}{\left(R_S \parallel \frac{1}{g_{m1}} \right) (C_{SB1} + C_{GS1})} \quad \omega_{p,Y} = \frac{1}{\frac{1}{g_{m2}} (C_{DB1} + C_{GD1} + C_{GS2} + C_{DB2})}$$

Example: Frequency Response of CG Stage

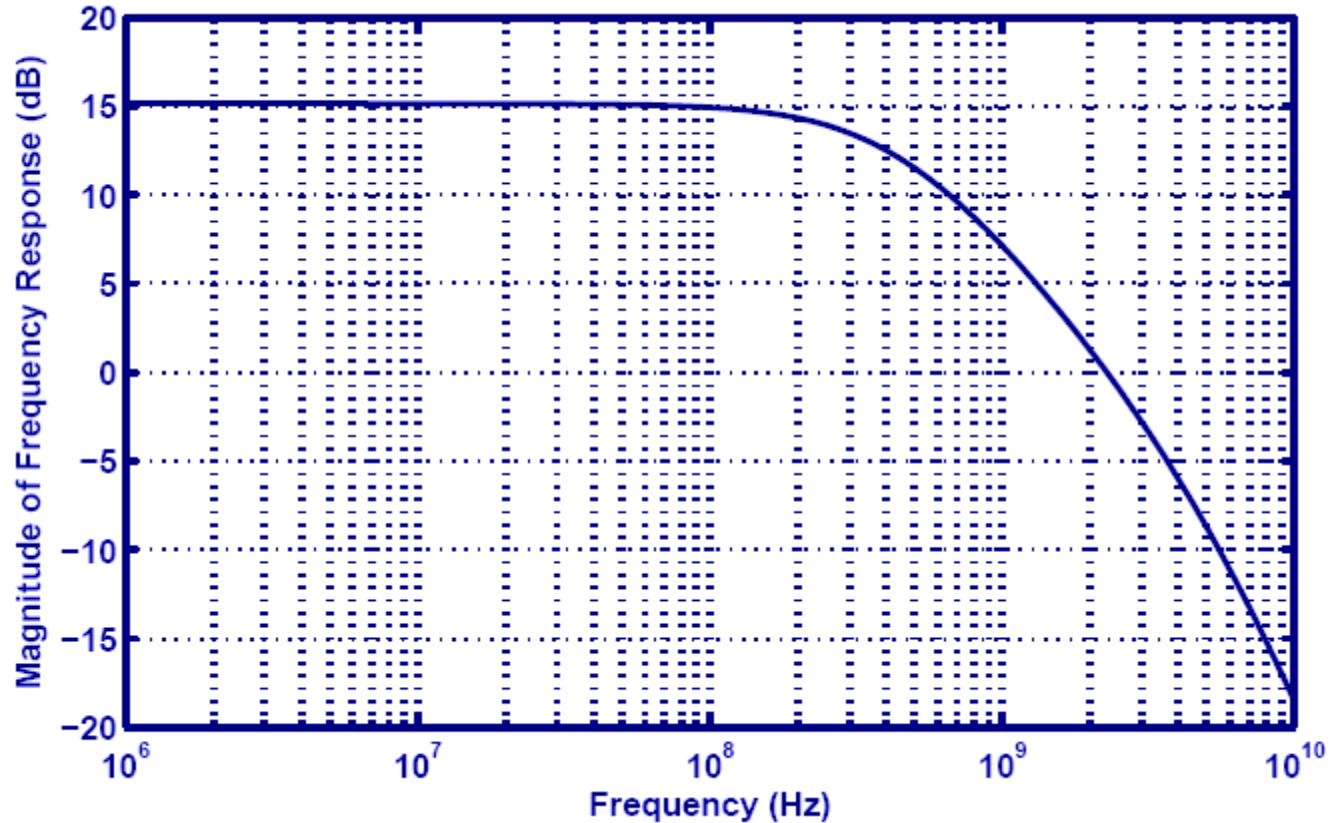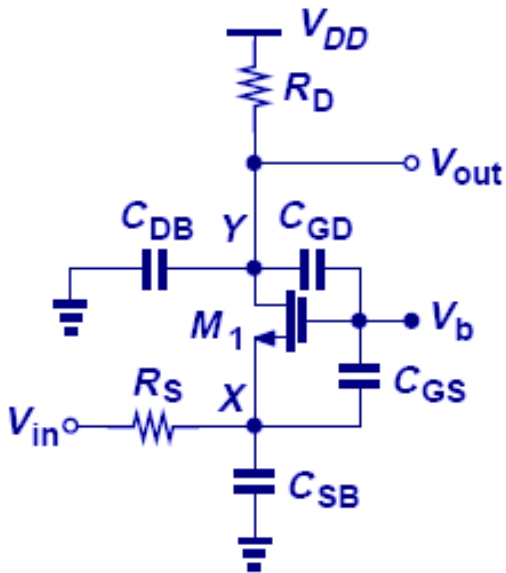

$$R_S = 200\Omega$$

$$C_{GS} = 250\text{fF}$$

$$C_{GD} = 80\text{fF}$$

$$C_{DB} = 100\text{fF}$$

$$g_m = (150\Omega)^{-1}$$


$$\lambda = 0$$

$$R_d = 2\text{K}\Omega$$

$$|\omega_{p,X}| = 2\pi \times (5.31\text{GHz})$$



$$|\omega_{p,Y}| = 2\pi \times (442\text{MHz})$$

Source Followers

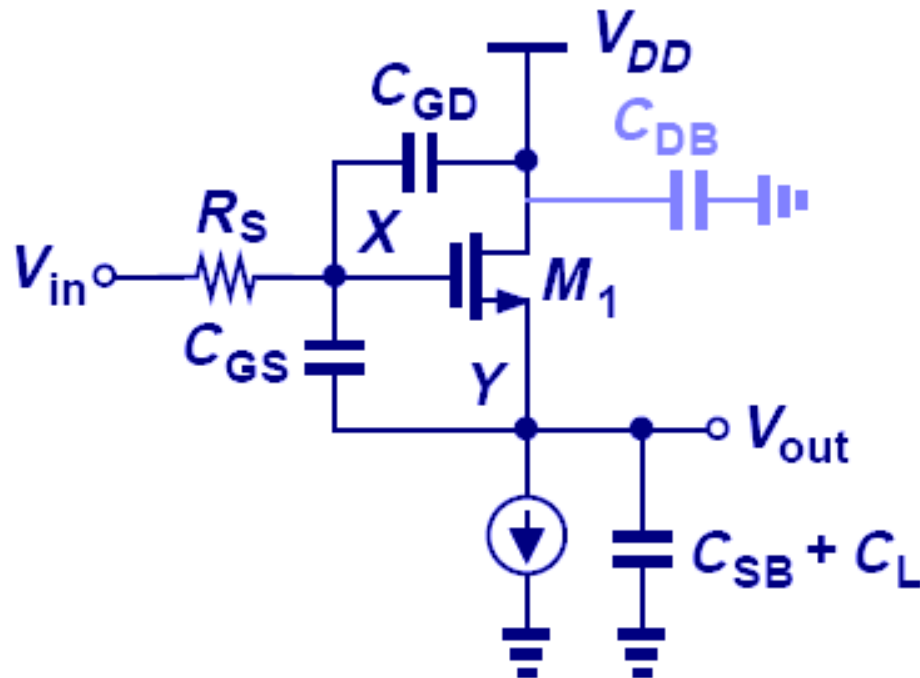

- The following will discuss the frequency response of source followers using direct analysis.

Direct Analysis of Source Follower Stage

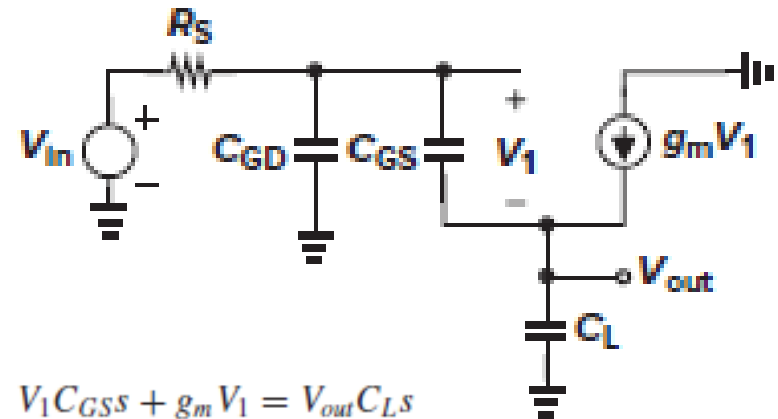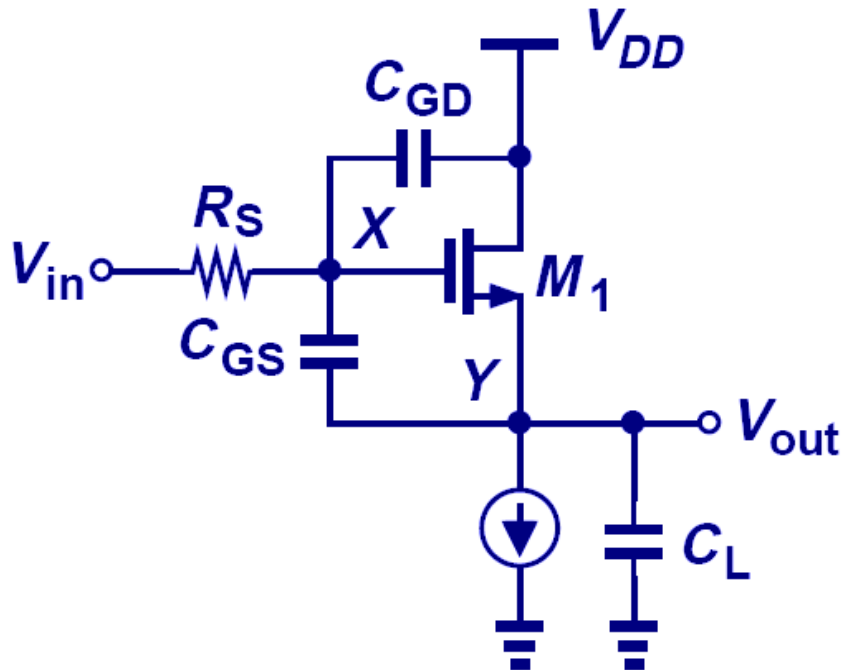

$$V_1 C_{GS} s + g_m V_1 = V_{out} C_L s$$

$$V_1 = \frac{C_L s}{g_m + C_{GS} s} V_{out}$$

$$V_{in} = R_S [V_1 C_{GS} s + (V_1 + V_{out}) C_{GD} s] + V_1 + V_{out}$$


$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS} s}{R_S (C_{GS} C_L + C_{GS} C_{GD} + C_{GD} C_L) s^2 + (g_m R_S C_{GD} + C_L + C_{GS}) s + g_m}$$

$$\frac{V_{out}}{V_{in}} = \frac{1 + \frac{C_{GS}}{g_m} s}{as^2 + bs + 1}$$

$$a = \frac{R_S}{g_m} (C_{GD} C_{GS} + C_{GD} C_L + C_{GS} C_L)$$

$$b = R_S C_{GD} + \frac{C_{GS} + C_L}{g_m}$$

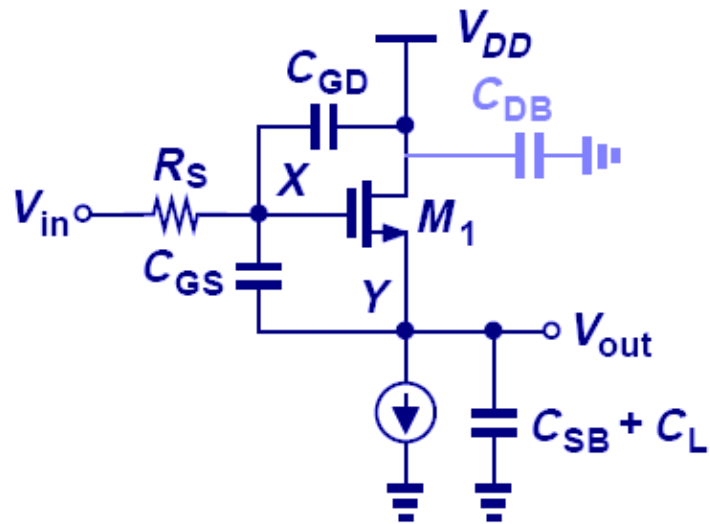Example: Frequency Response of Source Follower



$$R_S = 200\Omega$$

$$C_L = 100\text{ fF}$$


$$C_{GS} = 250\text{ fF}$$

$$C_{GD} = 80\text{ fF}$$

$$C_{DB} = 100\text{ fF}$$

$$g_m = (150\Omega)^{-1}$$


$$\lambda = 0$$

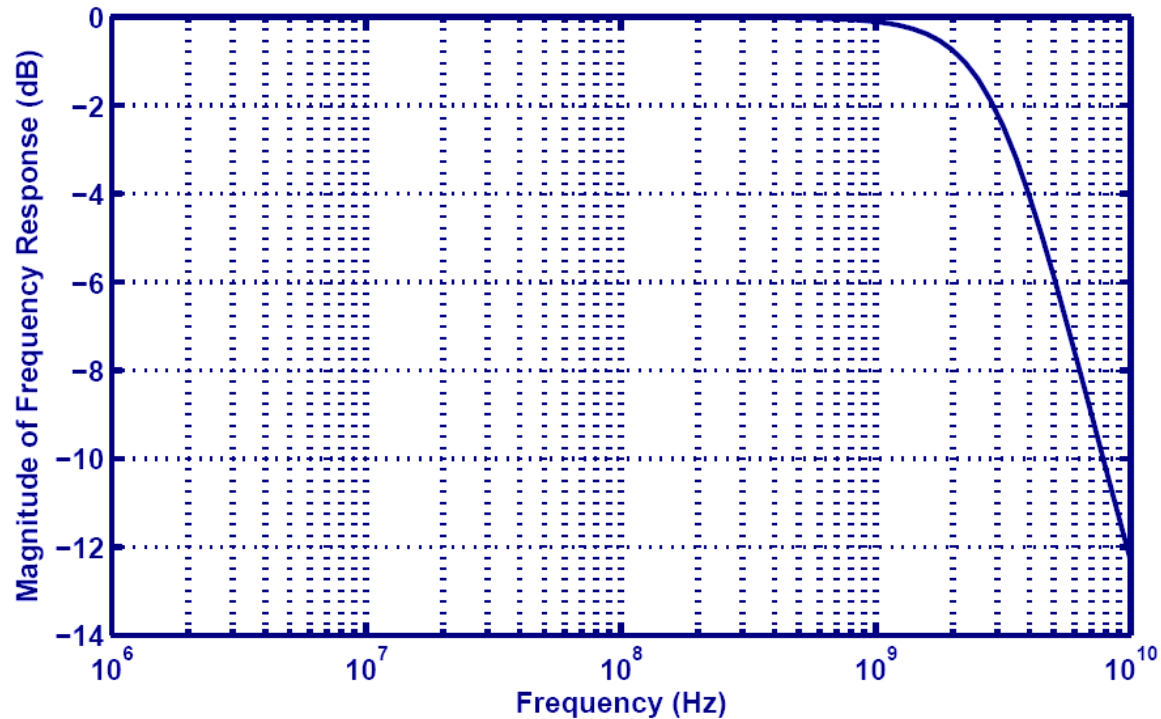

$$\omega_{p1} = 2\pi[-1.79\text{GHz} + j(2.57\text{GHz})]$$

$$\omega_{p2} = 2\pi[-1.79\text{GHz} - j(2.57\text{GHz})]$$

Example: Source Follower

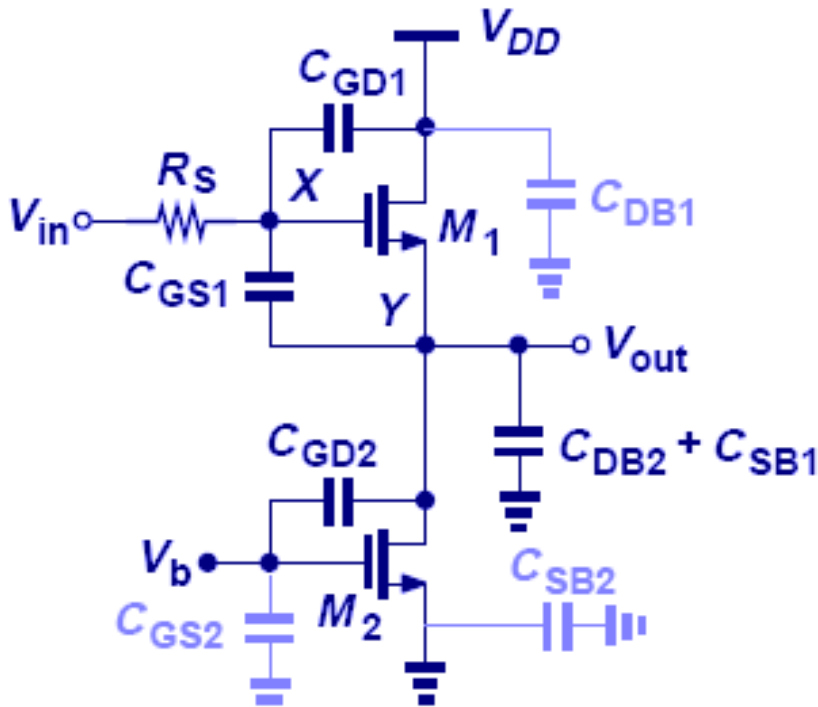


$$\frac{V_{out}}{V_{in}} = \frac{1 + \frac{C_{GS}}{g_m} s}{as^2 + bs + 1}$$

$$C_L = C_{DB2} + C_{SB1} + C_{GD2}$$

$$a = \frac{R_S}{g_{m1}} \left[C_{GD1} C_{GS1} + (C_{GD1} + C_{GS1})(C_{SB1} + C_{GD2} + C_{DB2}) \right]$$

$$b = R_S C_{GD1} + \frac{C_{GS1} + C_{SB1} + C_{GD2} + C_{DB2}}{g_{m1}}$$

Input Capacitance of Source Follower

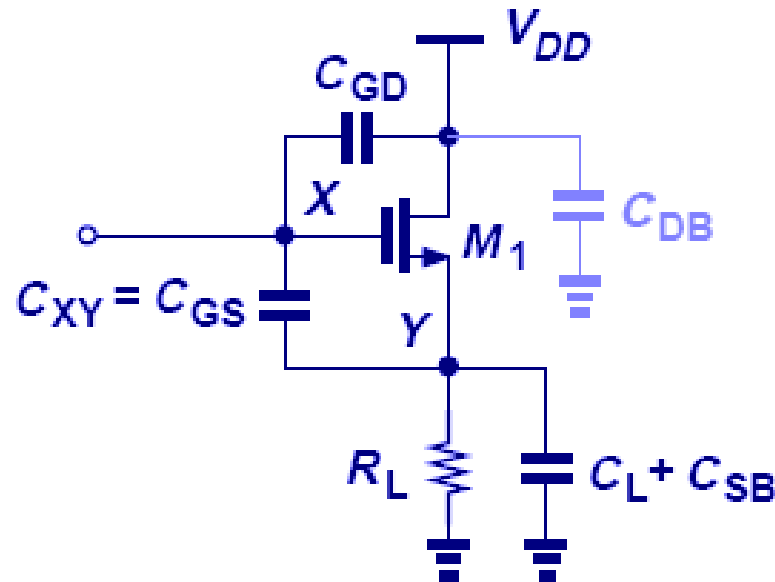



$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}}$$

$$C_X = (1 - A_v)C_{XY}$$

$$= \frac{1}{1 + g_m R_L} C_{XY}$$

$$C_{in} = C_{GD} + \frac{C_{GS}}{1 + g_m R_L}$$

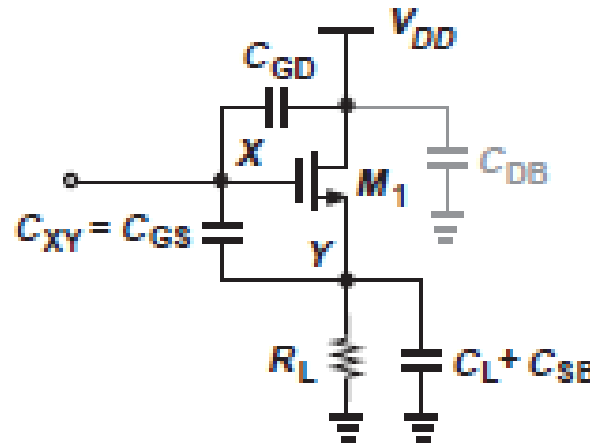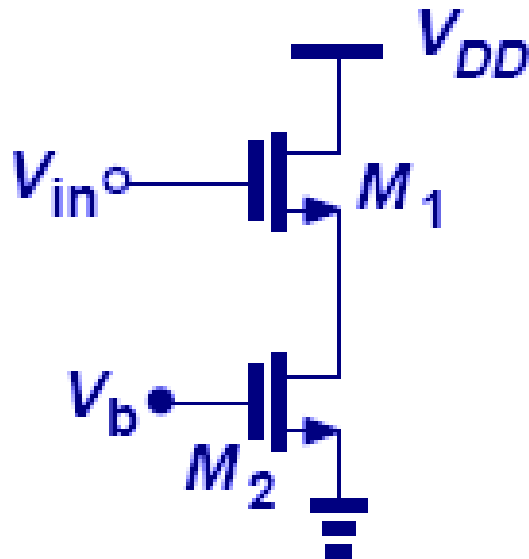Example: Source Follower Input Capacitance




$$A_v = \frac{r_{O1} || r_{O2}}{r_{O1} || r_{O2} + \frac{1}{g_{m1}}}$$

$$C_{in} = C_{GD1} + (1 - A_v)C_{GS1}$$

$$= C_{GD1} + \frac{1}{1 + g_{m1}(r_{O1} || r_{O2})}C_{GS1}$$



$$C_{in} = C_{GD1} + \frac{1}{1 + g_{m1}(r_{O1} || r_{O2})}C_{GS1}$$

Output Impedance of Source Follower

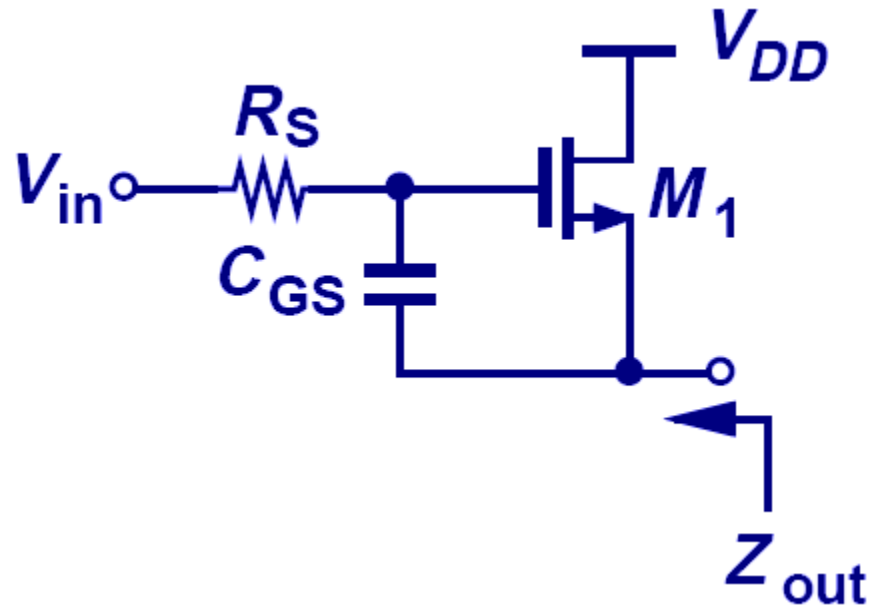


$$\frac{V_X}{I_X} = \frac{R_S C_{GS} s + 1}{C_{GS} s + g_m}$$

Active Inductor

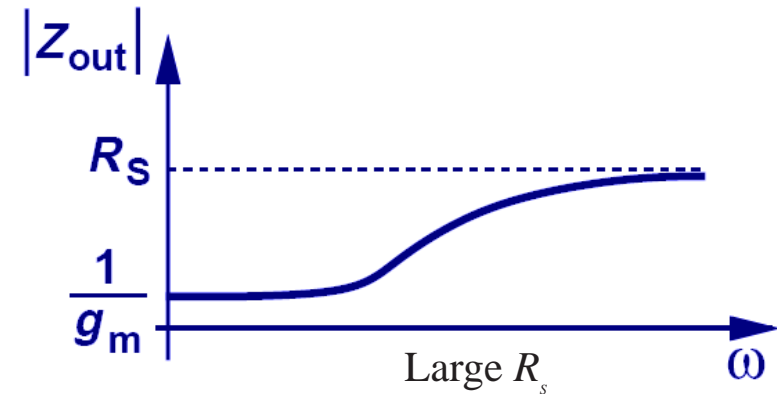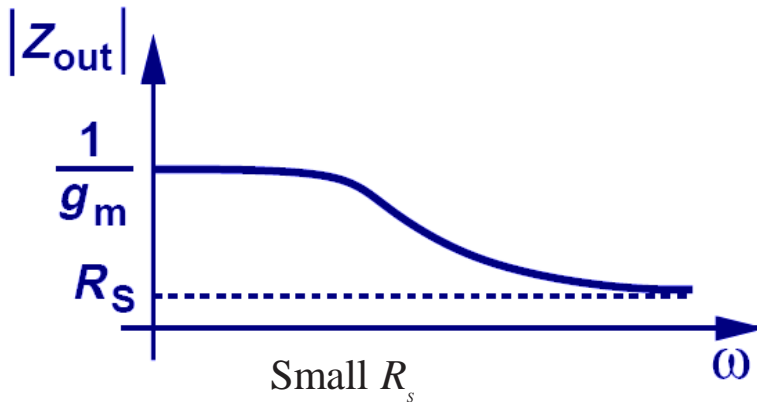


- The plot above shows the output impedance of source followers. Since a follower's primary duty is to lower the driving impedance ($R_s > 1/g_m$), the "active inductor" characteristic on the right is usually observed.

Example: Output Impedance

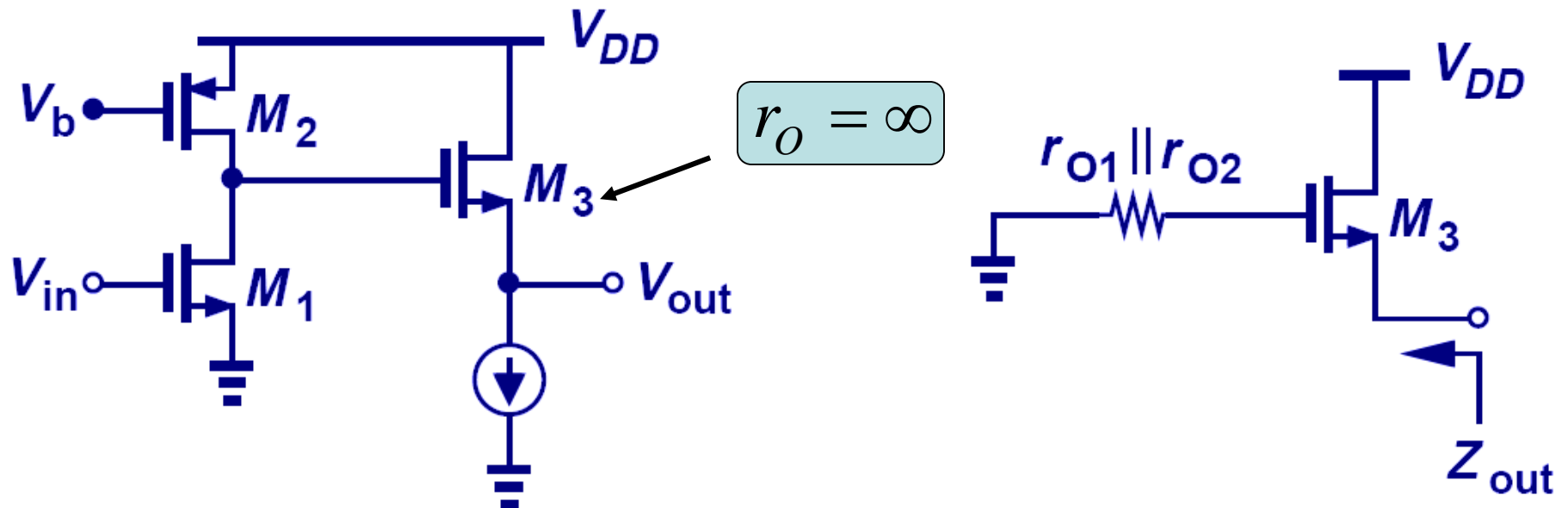

$$\frac{V_X}{I_X} = \frac{(r_{O1} \parallel r_{O2})C_{GS3}s + 1}{C_{GS3}s + g_{m3}}$$

Frequency Response of Cascode Stage

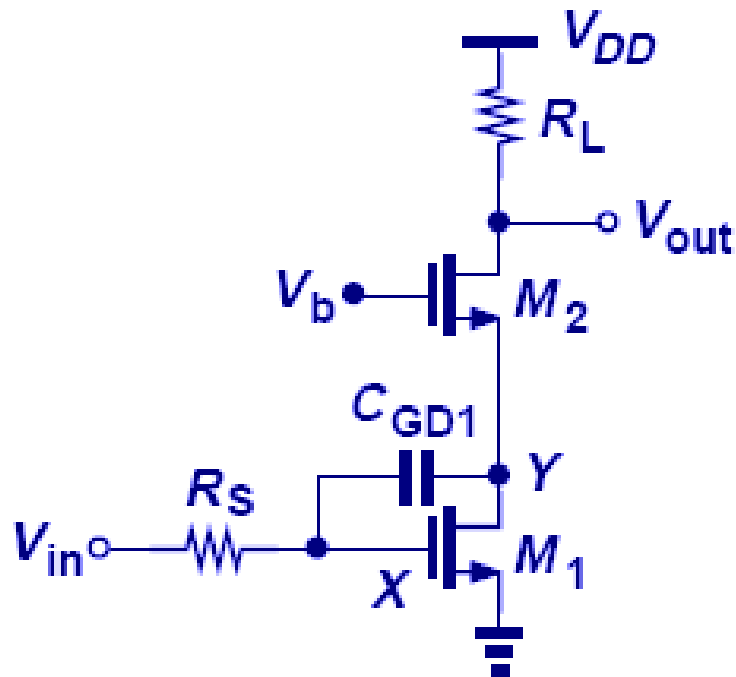

$$A_{v,XY} = \frac{-g_{m1}}{g_{m2}} \approx -1$$


$$C_x \approx 2C_{XY}$$

- For cascode stages, there are three poles and Miller multiplication is smaller than in the CE/CS stage.

Poles of MOS Cascode


$$\omega_{p,X} = \frac{1}{R_S \left[C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2}} \right) C_{GD1} \right]}$$
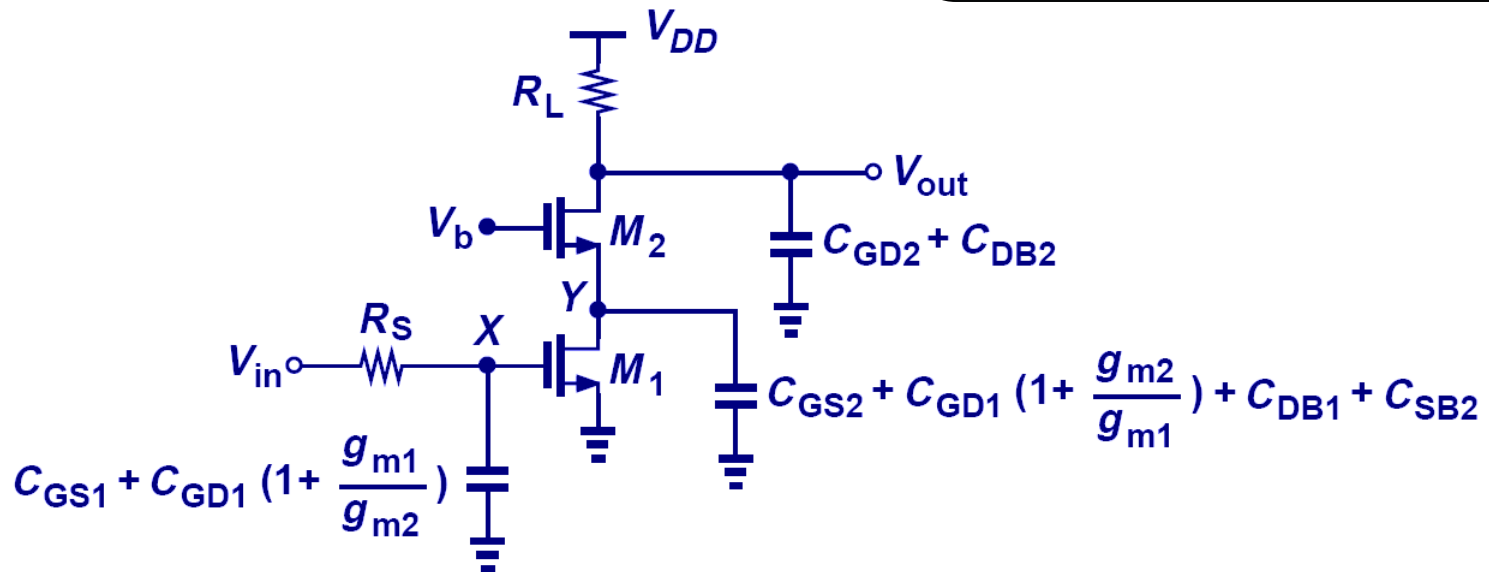
$$\omega_{p,out} = \frac{1}{R_L (C_{DB2} + C_{GD2})}$$



$$\omega_{p,Y} = \frac{1}{\frac{1}{g_{m2}} \left[C_{DB1} + C_{GS2} + \left(1 + \frac{g_{m2}}{g_{m1}} \right) C_{GD1} \right]}$$

Example: Frequency Response of Cascode

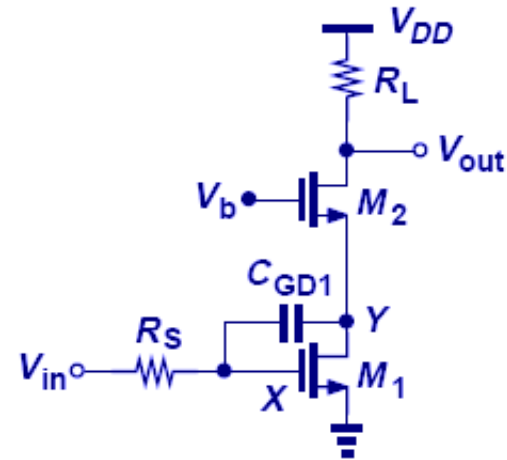

$$R_S = 200\Omega$$

$$C_{GS} = 250\text{fF}$$

$$C_{GD} = 80\text{fF}$$


$$C_{DB} = 100\text{fF}$$

$$g_m = (150\Omega)^{-1}$$

$$\lambda = 0$$

$$R_L = 2\text{K}\Omega$$

Frequency Response

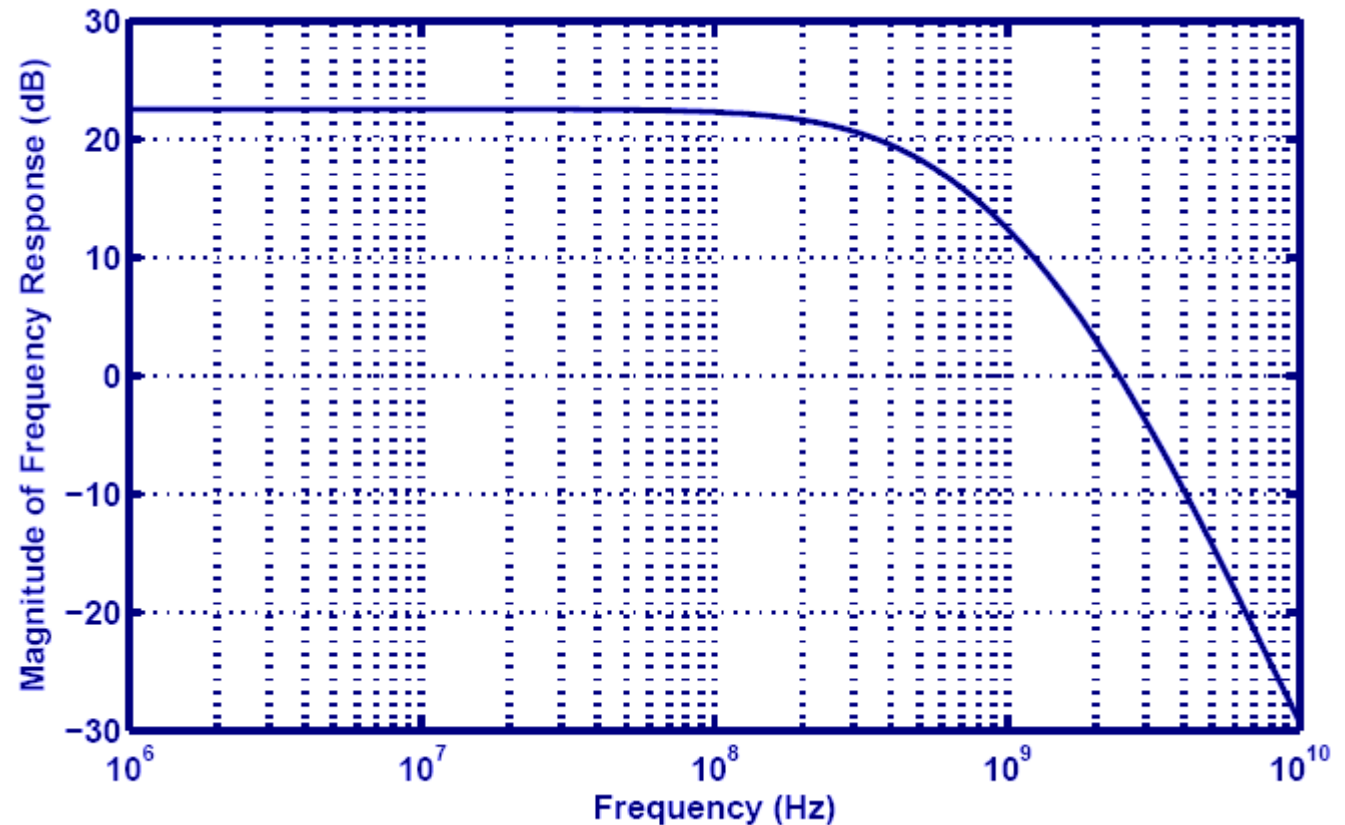

$$|\omega_{p,X}| = 2\pi \times (1.95\text{GHz})$$


$$|\omega_{p,Y}| = 2\pi \times (1.73\text{GHz})$$

$$|\omega_{p,out}| = 2\pi \times (442\text{MHz})$$

MOS Cascode Example


$$\omega_{p,X} = \frac{1}{R_S \left[C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2}} \right) C_{GD1} \right]}$$
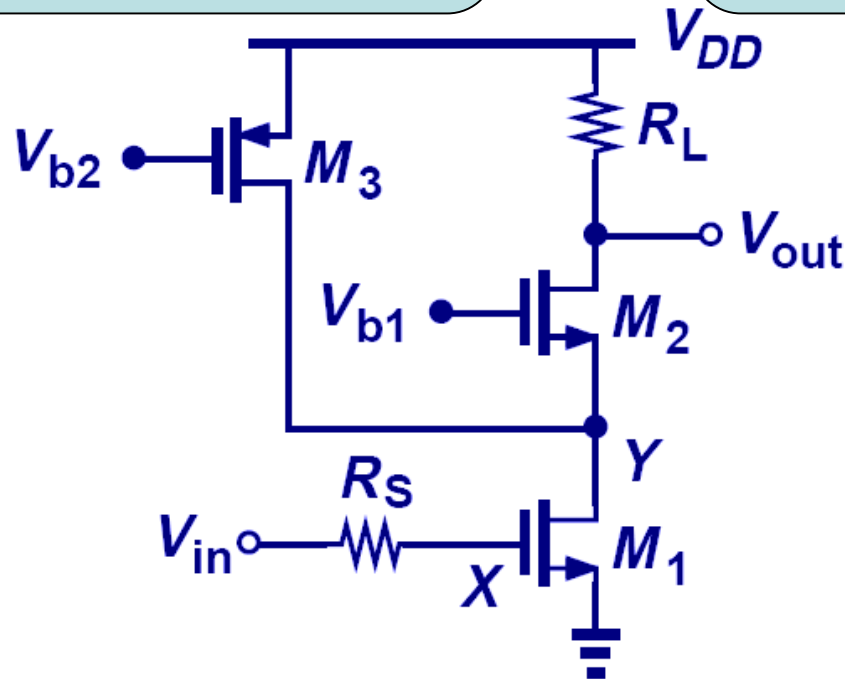
$$\omega_{p,out} = \frac{1}{R_L (C_{DB2} + C_{GD2})}$$



$$\omega_{p,Y} = \frac{1}{\frac{1}{g_{m2}} \left[C_{DB1} + C_{GS2} + \left(1 + \frac{g_{m2}}{g_{m1}} \right) C_{GD1} + C_{GD3} + C_{DB3} \right]}$$

I/O Impedance of MOS Cascode

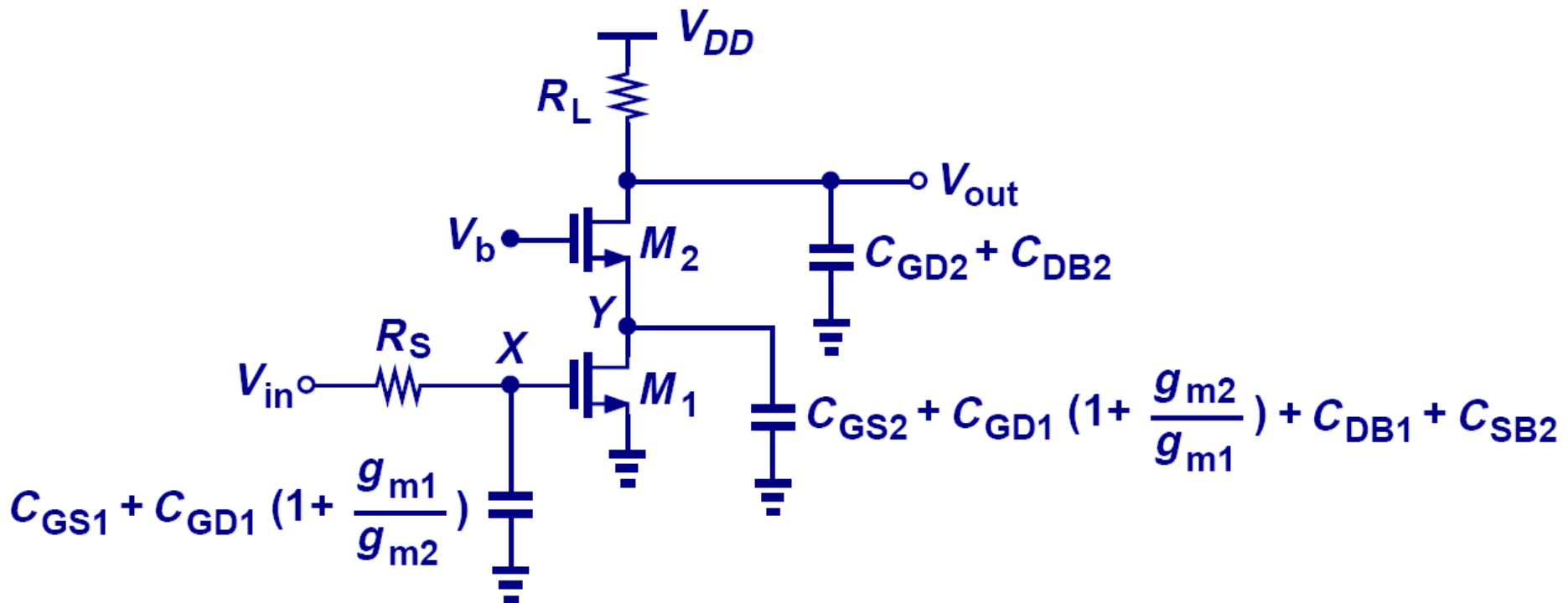


$$Z_{in} = \frac{1}{\left[C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2}} \right) C_{GD1} \right] s}$$

Frequency Response


$$Z_{out} = R_L \parallel \frac{1}{(C_{GD2} + C_{DB2})s}$$

MOS Differential Pair Frequency Response

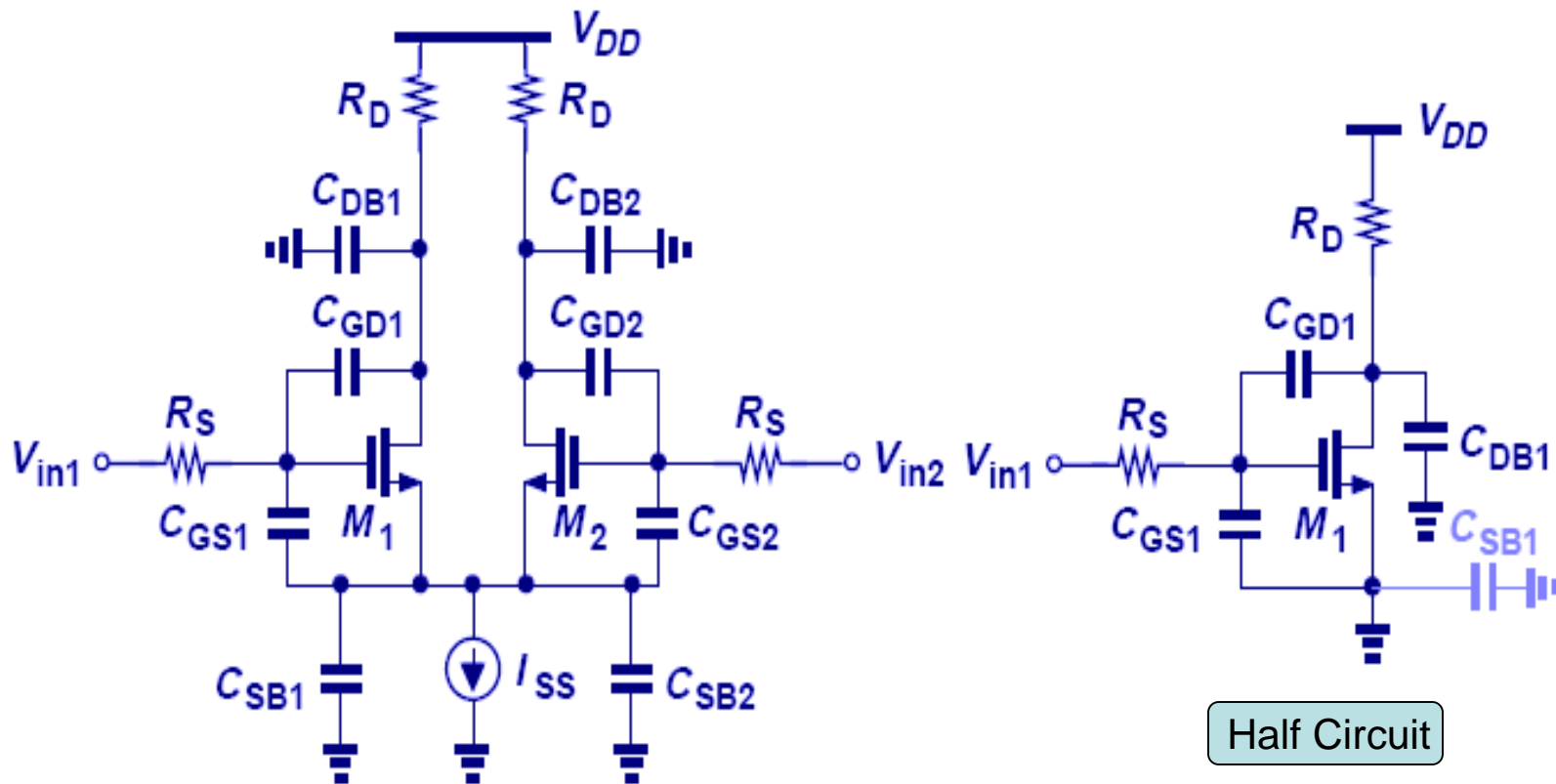

- Since MOS differential pair can be analyzed using half-circuit, its transfer function, I/O impedances, locations of poles/zeros are the same as that of the half circuit's.


Example: MOS Differential Pair

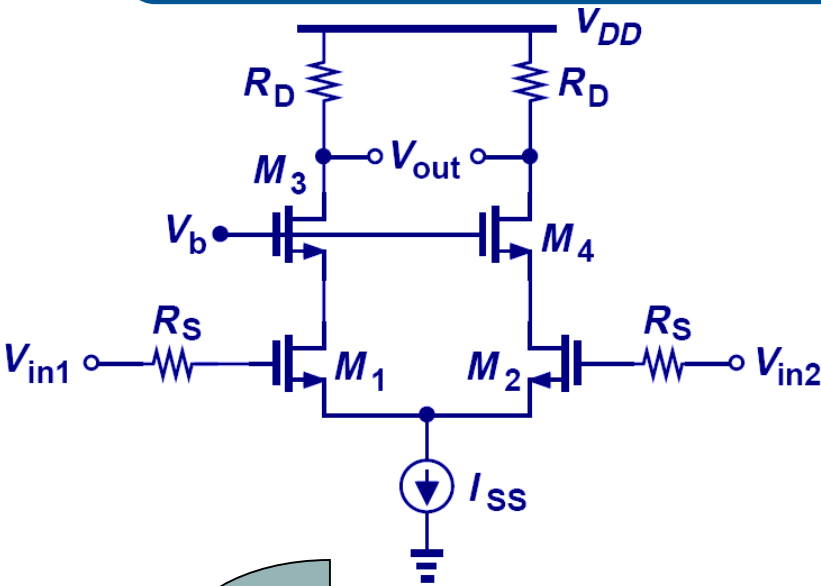


$$\omega_{p,X} = \frac{1}{R_S [C_{GS1} + (1 + g_{m1} / g_{m3}) C_{GD1}]}$$

$$\omega_{p,Y} = \frac{1}{\frac{1}{g_{m3}} \left[C_{DB1} + C_{GS3} + \left(1 + \frac{g_{m3}}{g_{m1}} \right) C_{GD1} \right]}$$

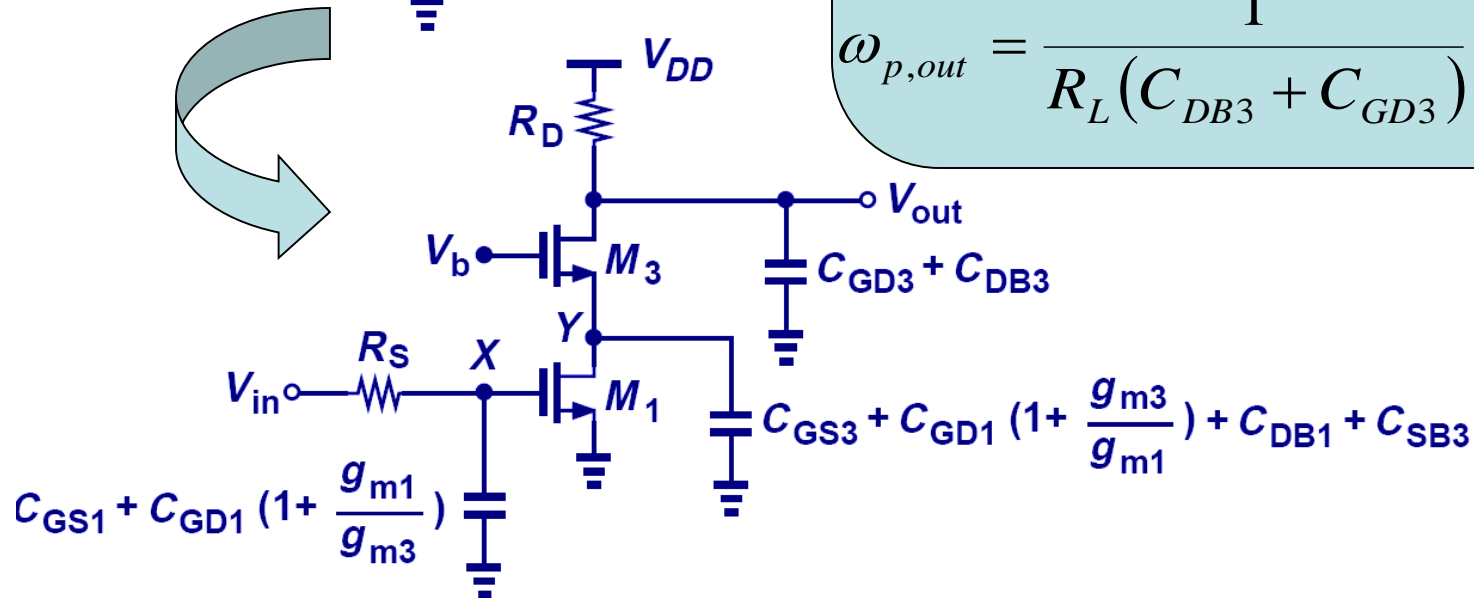
$$\omega_{p,out} = \frac{1}{R_L (C_{DB3} + C_{GD3})}$$



Common Mode Frequency Response

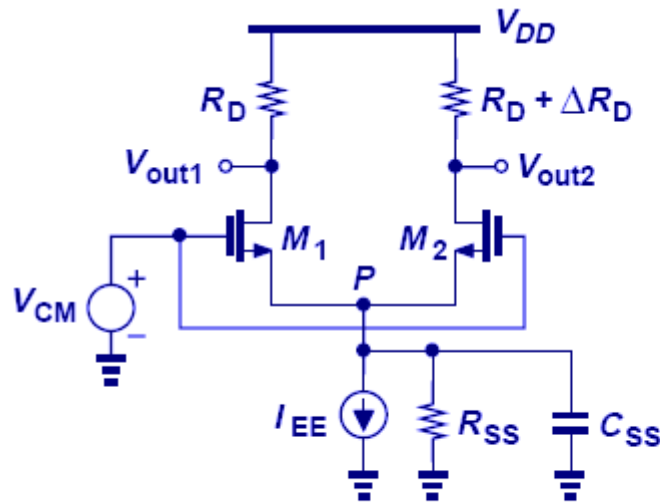

(a)

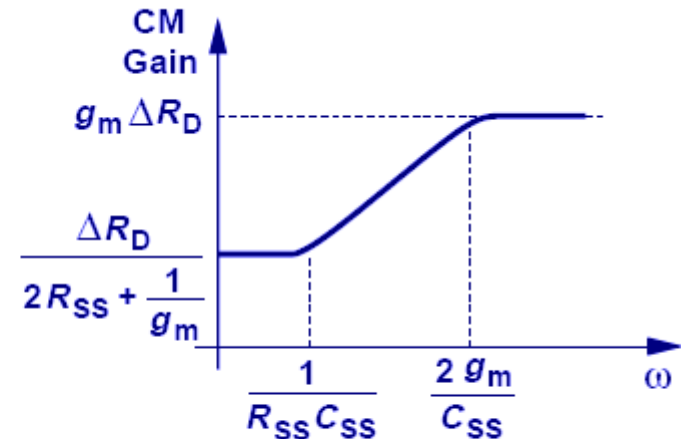

(b)


$$2g_m R_{SS} \gg 1$$

$$|\omega_z| = \frac{1}{R_{SS} C_{SS}} \quad |\omega_p| = \frac{2g_m}{C_{SS}}$$

$$\left| \frac{\Delta V_{out}}{\Delta V_{CM}} \right| = \frac{g_m \Delta R_D (R_{SS} C_{SS} s + 1)}{R_{SS} C_{SS} s + 2g_m R_{SS} + 1}$$


➤ C_{SS} will lower the total impedance between point P to ground at high frequency, leading to higher CM gain which degrades the CM rejection ratio.

Tail Node Capacitance Contribution

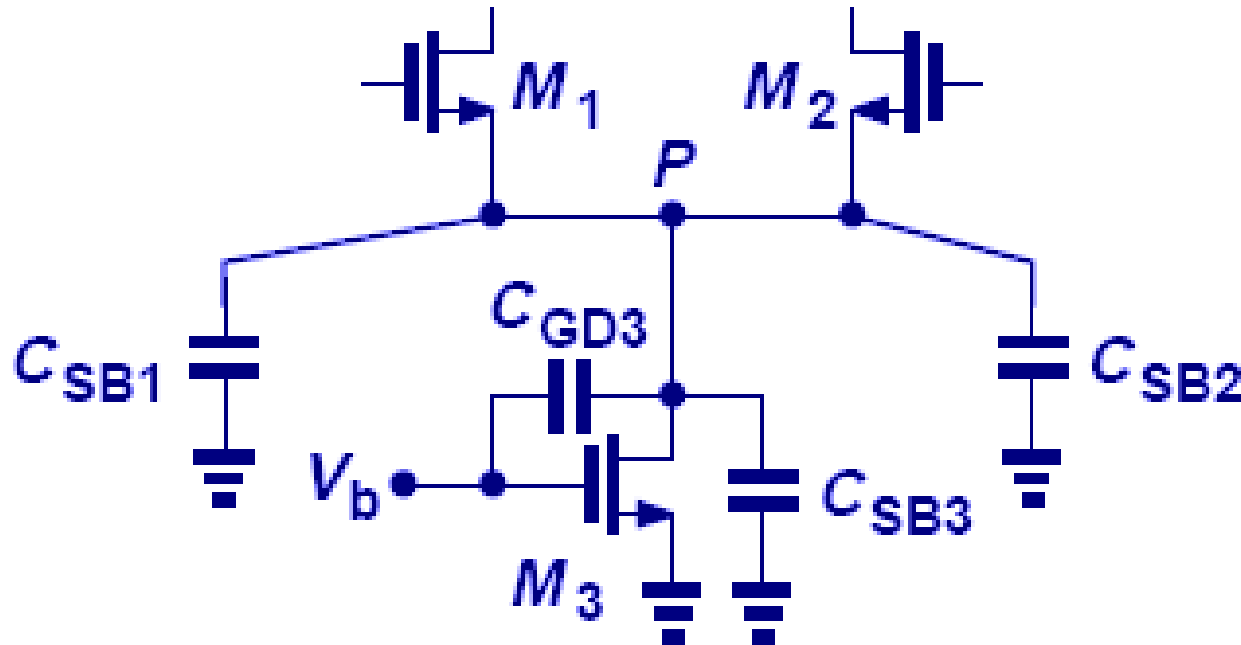

- Source-Body Capacitance of M_1 , M_2 and M_3
- Gate-Drain Capacitance of M_3

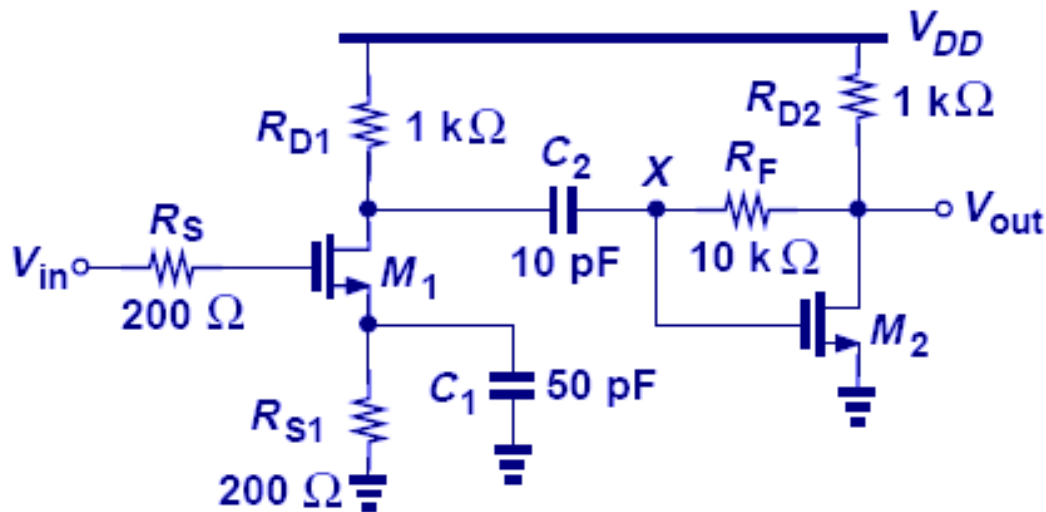Example: IC Amplifier – Low Frequency Design




$$R_{in2} = \frac{R_F}{1 - A_{v2}}$$

$$\omega_{L1} = \frac{g_{m1}R_{S1} + 1}{R_{S1}C_1} = 2\pi \times (42.4 \text{ MHz})$$




$$\omega_{L2} = \frac{1}{(R_{D1} + R_{in2})C_2} = 2\pi \times (6.92 \text{ MHz})$$

Example: IC Amplifier – Midband Design

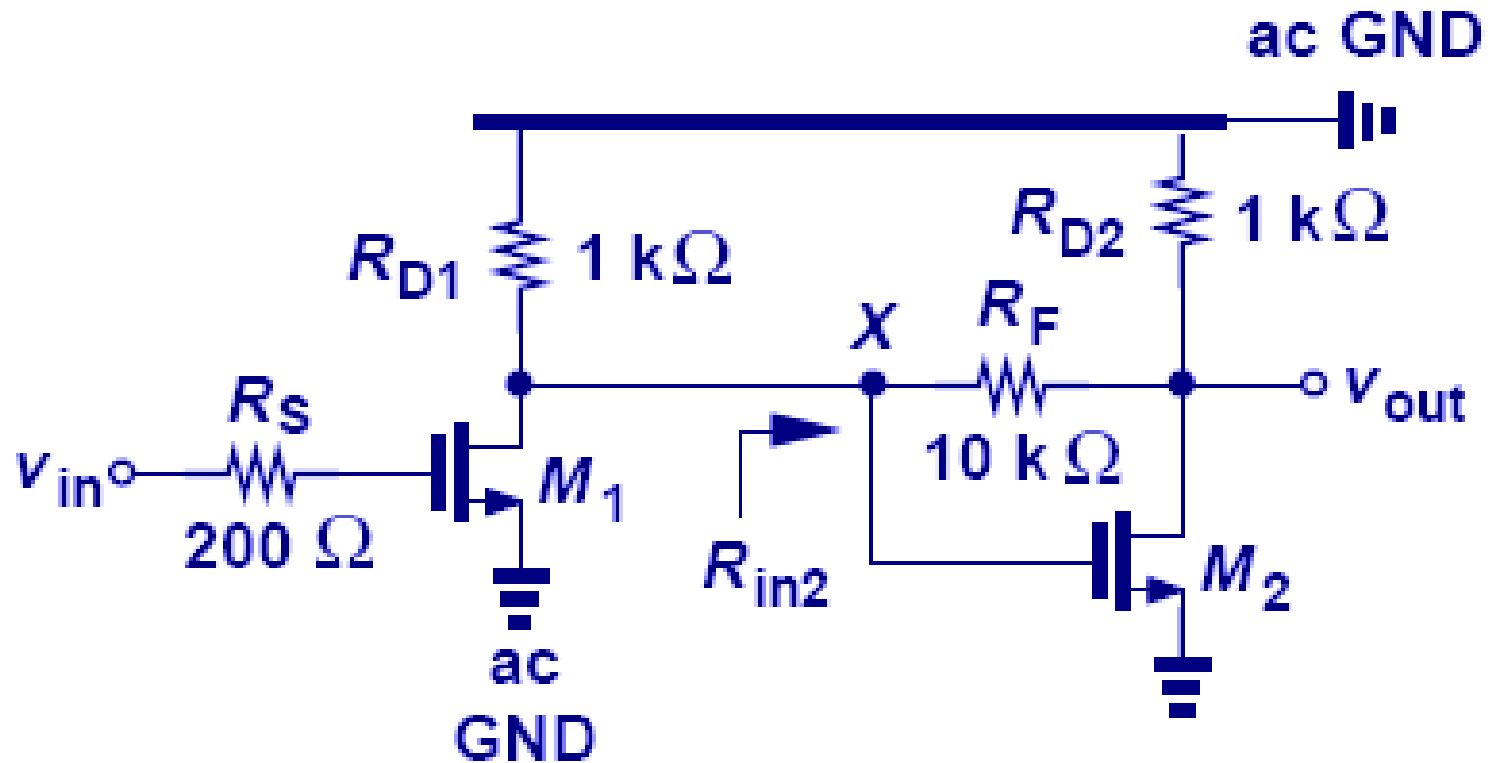

$$\frac{v_X}{v_{in}} = -g_{m1}(R_{D1} \parallel R_{in2}) = -3.77$$

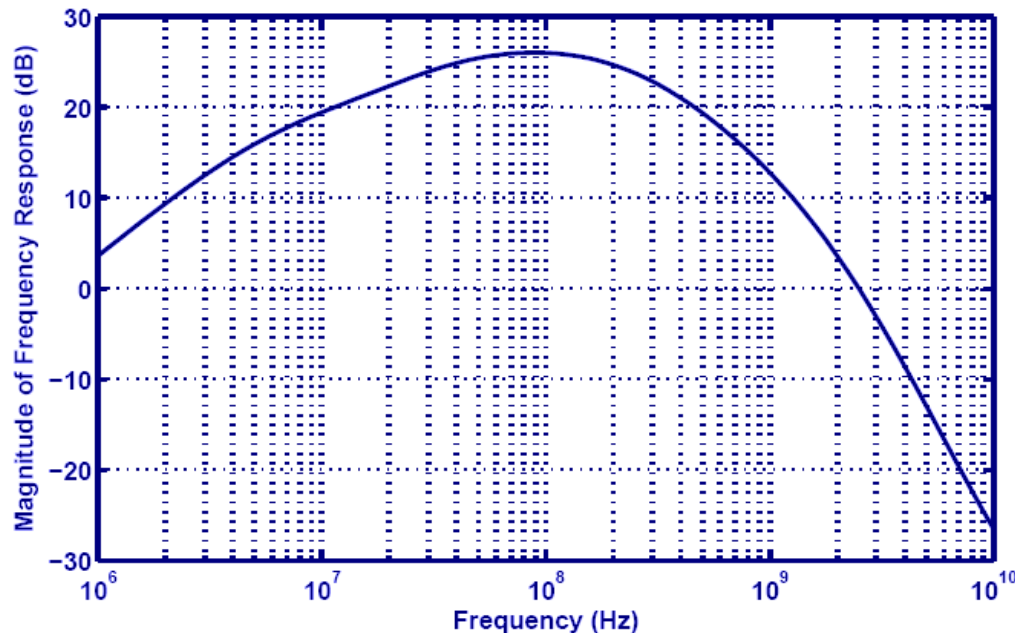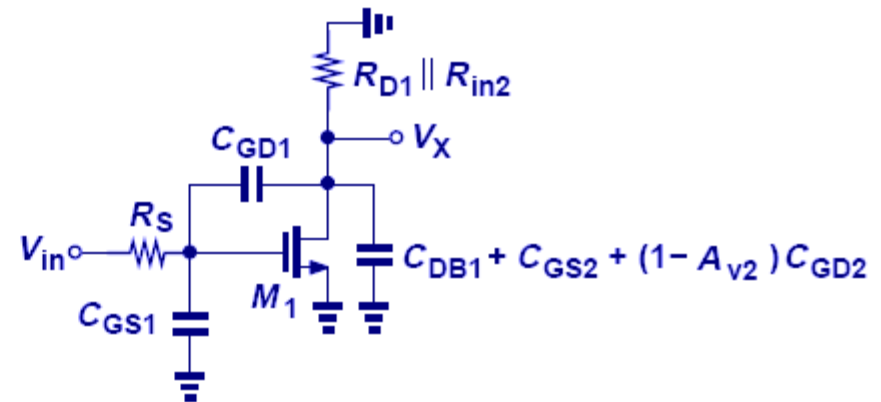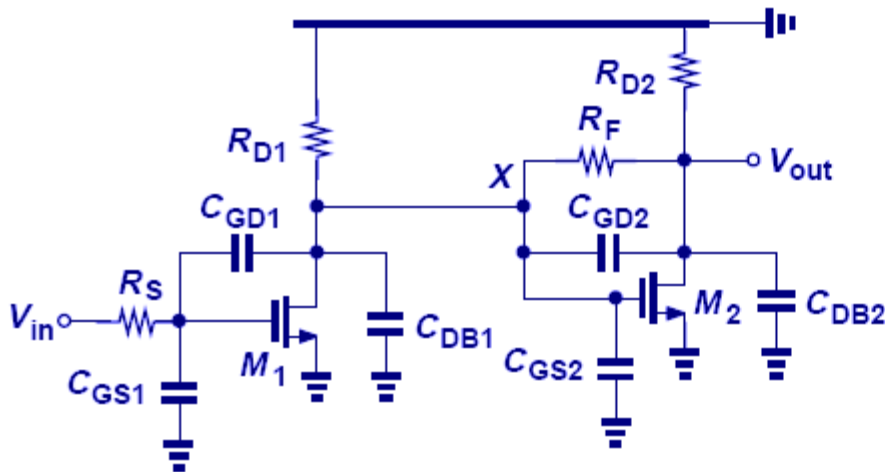Example: IC Amplifier – High Frequency Design



Frequency Response

$$|\omega_{p1}| = 2\pi \times (242 \text{ MHz})$$

$$|\omega_{p2}| = 2\pi \times (2.74 \text{ GHz})$$

$$|\omega_{p3}| = \frac{1}{R_{L2}(1.15C_{GD2} + C_{DB2})}$$

$$= 2\pi \times (0.829 \text{ GHz})$$