



电子科技大学
格拉斯哥学院
Glasgow College, UESTC

VLSI

Lab 1

Jiayi Feng
2016200103020
2288941F

Instructor: Lianping Hou, Hadi Heidari


Date Performed: 2019/09/14

1.

I only figure out how to make schematic in the lab session, and I spend 3 day's leisure time, to get familiar with the software and the layout, not to mention the time on lecture notes.


2.

NOR2 schematic:

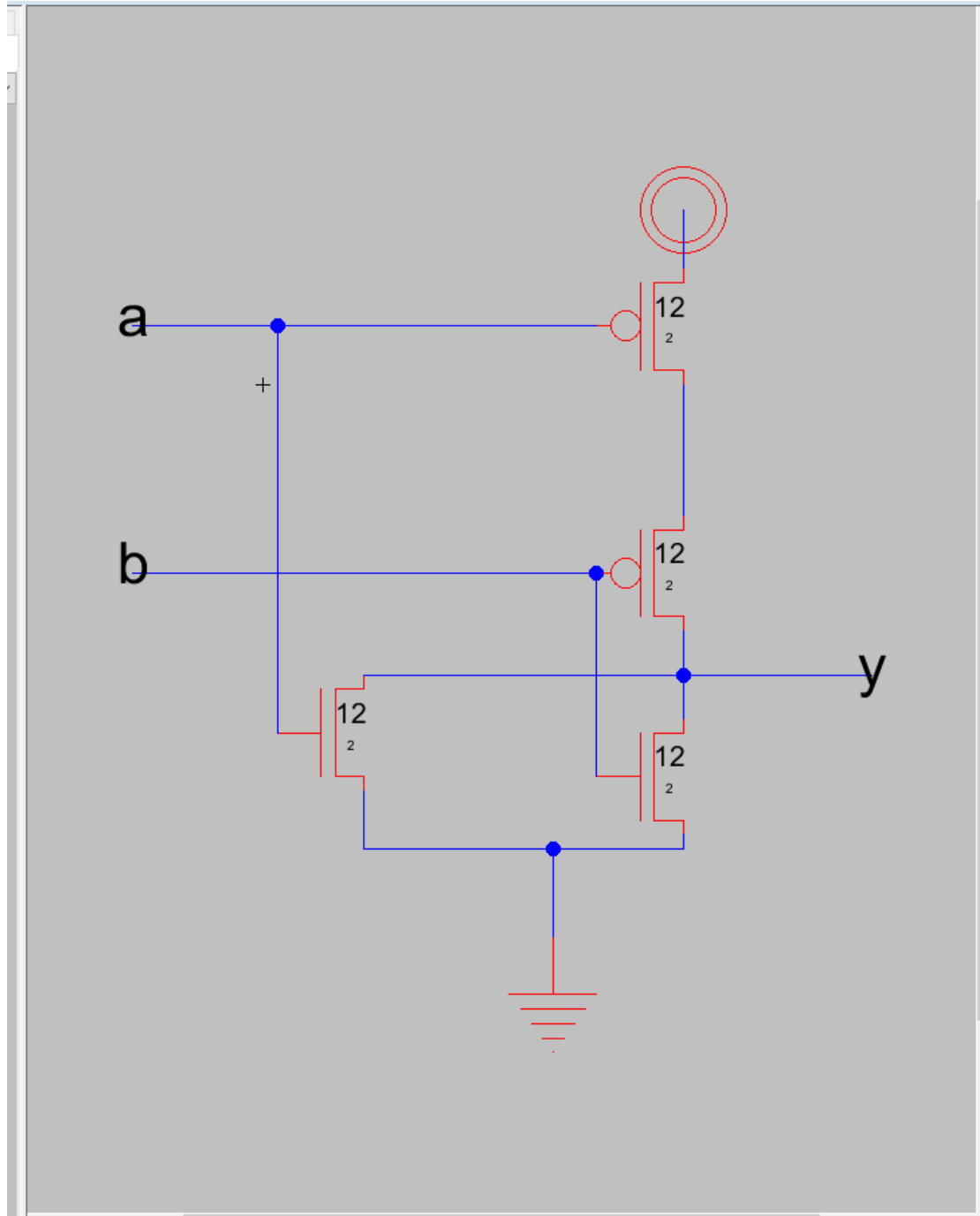


3.

NOR2 layout:

 

4.

OR2 schematic:

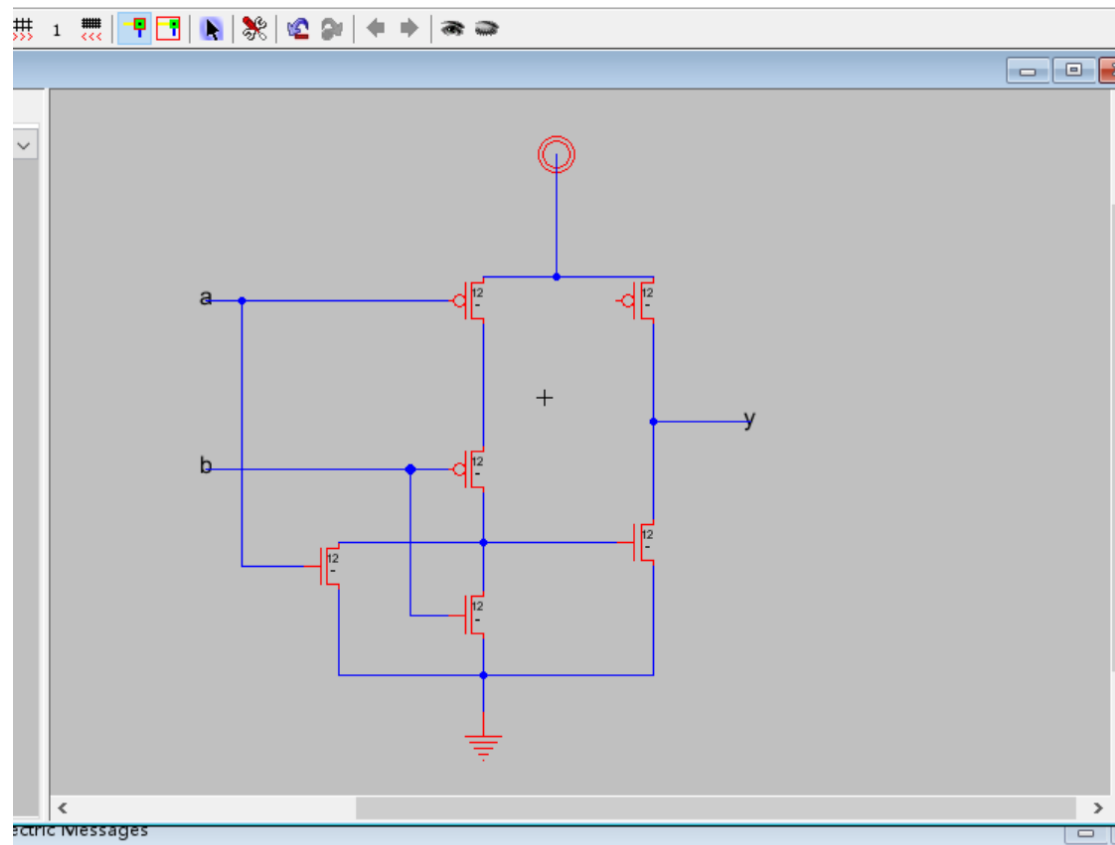


Electric Messages

ing: Aliasing nodes 'vdd' and 'Vdd'

les. 3 n-channel transistors. 3 n-channel transistors

5.

OR2 layout:

 

6.

