

Lecture 1: Introduction

Introduction

- ❑ Integrated circuits: many transistors on one chip.
- ❑ *Very Large Scale Integration (VLSI):*
 - How to design VLSI systems
- ❑ *Complementary Metal Oxide Semiconductor*
 - Fast, cheap, low power transistors
- ❑ Today: How to build your own simple CMOS chip
 - CMOS transistors
 - Building logic gates from transistors
 - Transistor layout and fabrication
- ❑ Rest of the course: How to build a good CMOS chip

Introduction

- ❑ Why is designing digital ICs different today than it was before?
- ❑ Will it change in future? https://en.wikipedia.org/wiki/Transistor_count

Processor	Transistor count	Date of introduction	Designer	Process	Area
10-core Core i7 Broadwell-E	3,200,000,000 ^[34]	2016	Intel	14 nm	246 mm ²
POWER9	8,000,000,000	2017	IBM	14 nm	695 mm ²
IBM z14 Storage Controller	9,700,000,000	2017	IBM	14 nm	696 mm ²
IBM z14	6,100,000,000	2017	IBM	14 nm	696 mm ²
Centriq 2400	18,000,000,000	2017	Qualcomm	10 nm	398 mm ²
Apple A11 Bionic (hexa-core ARM64 "mobile SoC")	4,300,000,000	2017	Apple	10 nm	89 mm ²
8-core Ryzen	4,800,000,000	2017	AMD	14 nm	192 mm ²
32-core AMD Epyc	19,200,000,000	2017	AMD	14 nm	768 mm ² (4 x 192 mm ²)
Apple A12 (hexa-core ARM64 "mobile SoC")	6,900,000,000	2018	Apple	7 nm	

What does it take to design VLSI systems?

1. idea (need)



2. write specifications




3. design system



4. analyze/ model system




5. Fabrication

 

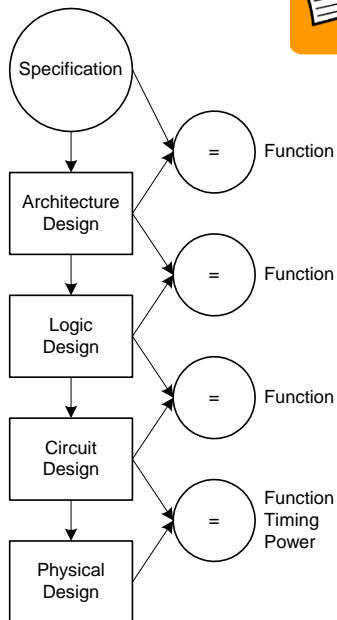
6. test / work as modeled?



Same engineering principles you learned so far



1. Applications / Ideas

 

2. Specifications

- Instruction set
- Interface (I/O pins)
- Organization of the system
- Functionality of each unit and how it to communicate to other unit

Format	Example	Encoding					
R	add \$rd, \$ra, \$rb	6	5	5	5	5	6
		0	ra	rb	rd	0	funct
I	beq \$ra, \$rb, imm	6	5	5	16		
		op	ra	rb	imm		
J	j dest	6	26				
		op	dest				

FIG 1.49 Instruction encoding formats

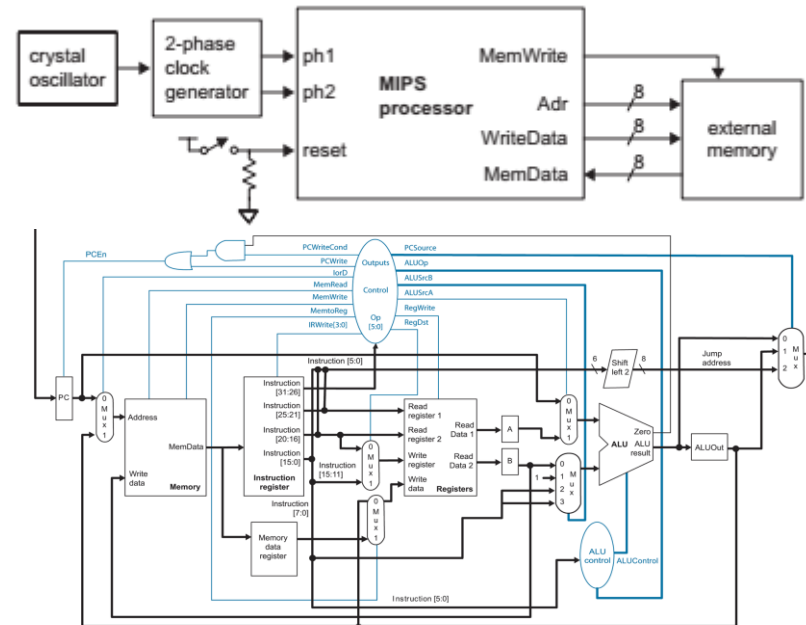
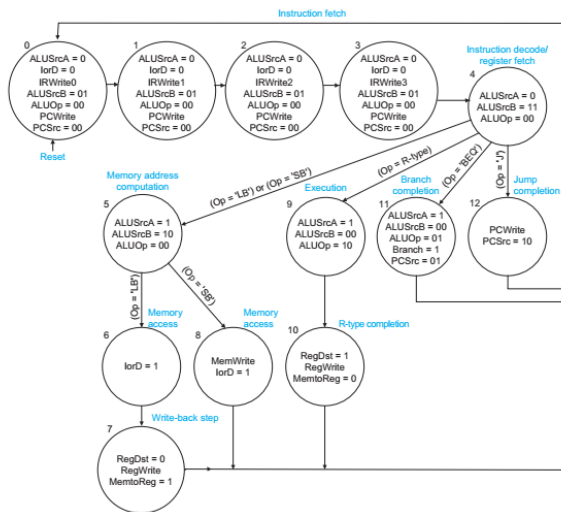


FIG 1.53 Multicycle MIPS microarchitecture. Reprinted from (Patterson04) with permission from Elsevier.


3/4. Design and Analysis

VHDL / Verilog / SystemC



```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3 use IEEE.NUMERIC_STD.all;
4
5 entity licensee is
6     port (
7         clk       : in  STD_LOGIC;
8         start     : in  STD_LOGIC;
9         stop      : in  STD_LOGIC;
10        gota      : in  STD_LOGIC;
11        dol       : in  STD_LOGIC;
12        cyfra_1   : out STD_LOGIC_VECTOR(0 downto 0);
13        cyfra_2   : out STD_LOGIC_VECTOR(0 downto 0);
14        wyjście   : out STD_LOGIC
15    );
16
17    attribute LOC : string;
18
19    attribute LOC of clk       : signal is "P00";
20    attribute LOC of start    : signal is "P13";
21    attribute LOC of stop     : signal is "P14";
22    attribute LOC of gota     : signal is "P15";
23    attribute LOC of dol      : signal is "P16";
24    attribute LOC of wyjście  : signal is "P4";
25    attribute LOC of cyfra_1  : signal is "P25 P26 P27 P28 P29 P30 P31 P32 P33";
26    attribute LOC of cyfra_2  : signal is "P26 P25 P24 P23 P22 P21 P20 P19";
27
28 end licensee;
29
30 architecture licensee of licensee is
31 begin
32     process (clk, gota, dol, start, stop) is
33     begin
34         variable licznik1 : unsigned(0 to 3) := "0000";
35         variable licznik2 : unsigned(0 to 3) := "0000";
36         variable licznik3 : unsigned(0 to 3) := "0000";
37         variable licznik4 : unsigned(0 to 3) := "0000";
38         variable cyfra1   : std_logic_vector(0 to 0);
39         variable cyfra2   : std_logic_vector(0 to 0);
40     end process;
41 end architecture licensee;
    
```


compilation/
synthesis

 


design schematics

  


mask layout patterns

 

find wire routes

 


device layout

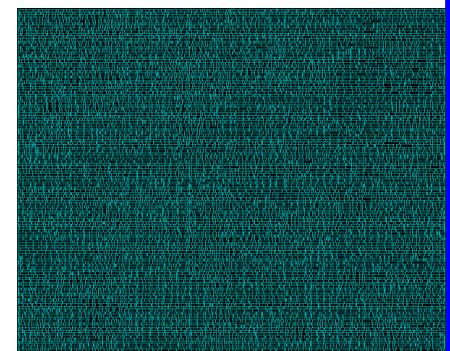




6. Evaluate design and compare to model

 

- Check signal integrity
- Power consumption
- Input/output behavior


- Does the chip function as it is supposed to be?
- Does it work at desired clock frequency? (can we overclock?)

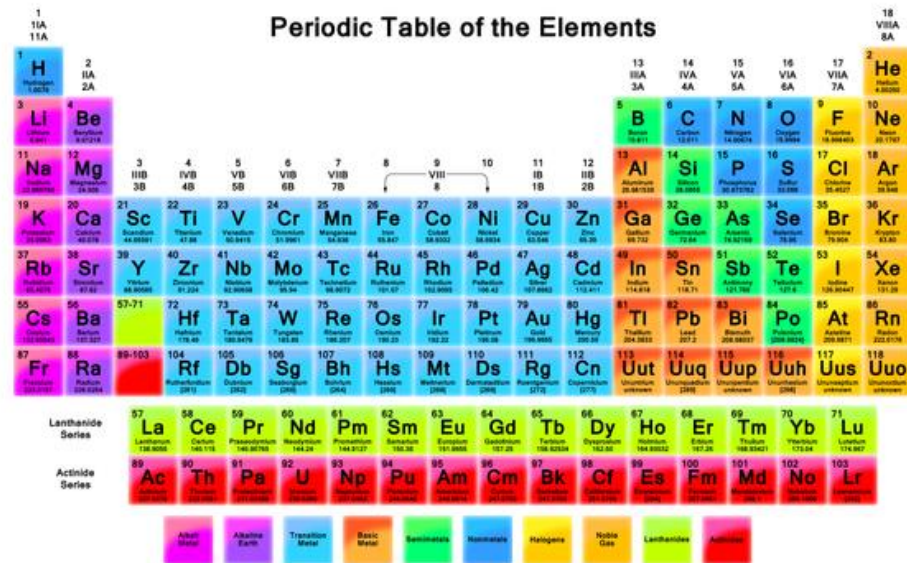- ❑ Transistors are built on a silicon substrate
- ❑ Silicon is a Group IV material
- ❑ Forms crystal lattice with bonds to four neighbors




Dopants

 - ❑ Silicon is a semiconductor
- ❑ Pure silicon has no free carriers and conducts poorly
- ❑ Adding dopants increases the conductivity
- ❑ Group V: As, extra electron (n-type)
- ❑ Group III: B(Boron) missing electron, called hole (p-type)




p-n Junctions

 - ❑ A junction between p-type and n-type semiconductor forms a diode.
- ❑ Current flows only in one direction




anode cathode

 


nMOS Transistor

 - ❑ Four terminals: gate, source, drain, body
- ❑ Gate – oxide – body stack looks like a capacitor
 - Gate and body are conductors
 - SiO_2 (oxide) is a very good insulator
 - Called metal – oxide – semiconductor (MOS) capacitor
 - Even though gate is no longer made of metal




nMOS Operation

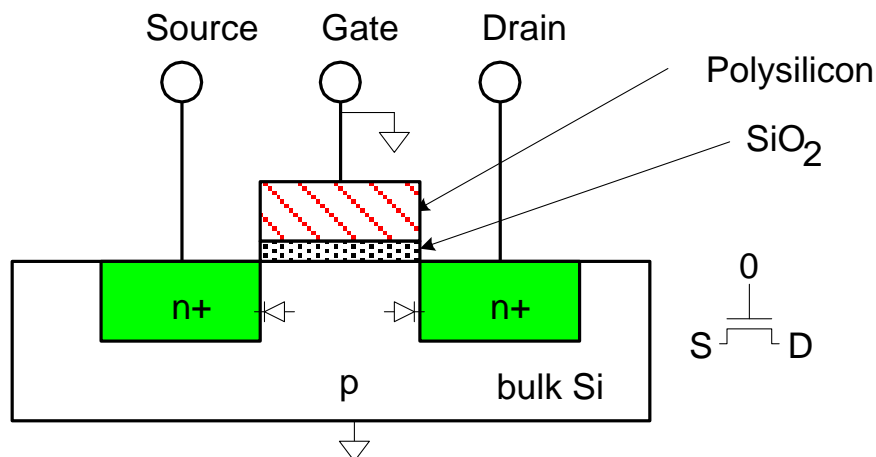- ❑ Body is usually tied to ground (0 V)
- ❑ When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body diodes are OFF
 - No current flows, transistor is OFF




nMOS Operation Cont.

 - When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



pMOS Transistor

 - ❑ Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior




Power Supply Voltage

- ❑ GND = 0 V
- ❑ In 1980's, $V_{DD} = 5V$
- ❑ V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- ❑ $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, 0.9, 0.8 \dots$

$$P_{\text{switching}} = CV_{DD}^2 f_{\text{sw}}$$



Transistors as Switches

 - ❑ We can view MOS transistors as electrically controlled switches
- ❑ Voltage at gate controls path from source to drain





CMOS Inverter

A	Y

  



CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  

CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  


3-input NAND Gate

- ☐ Y pulls low if ALL inputs are 1
- ☐ Y pulls high if ANY input is 0

CMOS Fabrication

- ❑ CMOS transistors are fabricated on silicon wafer
- ❑ Lithography process similar to printing press
- ❑ On each step, different materials are deposited or etched
- ❑ Easiest to understand by viewing both top and cross-section of wafer in a simplified manufacturing process

Photo masking

 


(lens system between mask and wafer)

Fabrication video

- ❑ From Sand to Silicon the Making of a Chip Intel


Inverter Cross-section

 - ❑ Typically use p-type substrate for nMOS transistors
- ❑ Requires n-well for body of pMOS transistors




Well and Substrate Taps

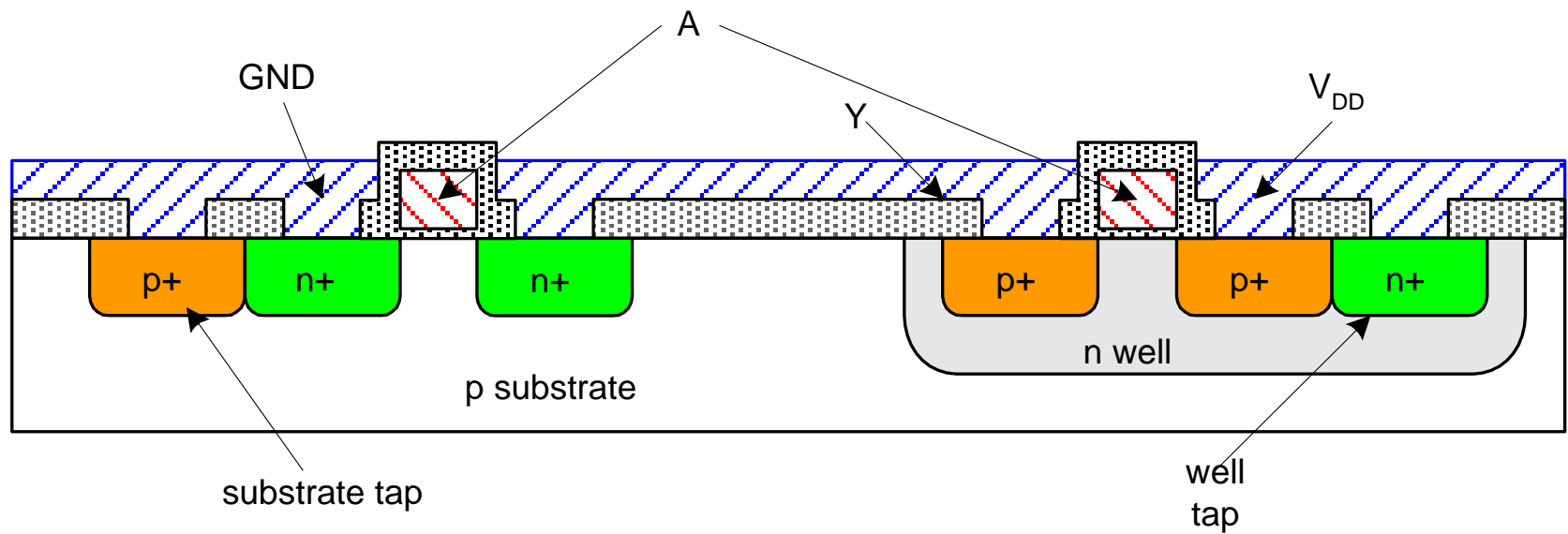- ❑ Substrate must be tied to GND and n-well to V_{DD}
- ❑ Metal to lightly-doped semiconductor forms poor connection called Shottky Diode
- ❑ Use heavily doped well and substrate contacts / taps




Inverter Mask Set

 - ❑ Transistors and wires are defined by *masks*
- ❑ Cross-section taken along dashed line



Detailed Mask Views

 - ❑ Six masks
 - n-well
 - Polysilicon
 - n+ diffusion
 - p+ diffusion
 - Contact
 - Metal



Fabrication

- ❑ Chips are built in huge factories called fabs
- ❑ Contain clean rooms as large as football fields



Courtesy of International
Business Machines Corporation.
Unauthorized use not permitted.

Fabrication Steps


- ❑ Start with blank wafer
- ❑ Build inverter from the bottom up
- ❑ First step will be to form the n-well
 - Cover wafer with protective layer of SiO_2 (oxide)
 - Remove layer where n-well should be built
 - Implant or diffuse n dopants into exposed wafer
 - Strip off SiO_2



p substrate


Oxidation

 - ❑ Grow SiO_2 on top of Si wafer
 - 900 – 1200 C with H_2O or O_2 in oxidation furnace




Photoresist

 - ❑ Spin on photoresist
 - Photoresist is a light-sensitive organic polymer
 - Softens where exposed to light




Lithography

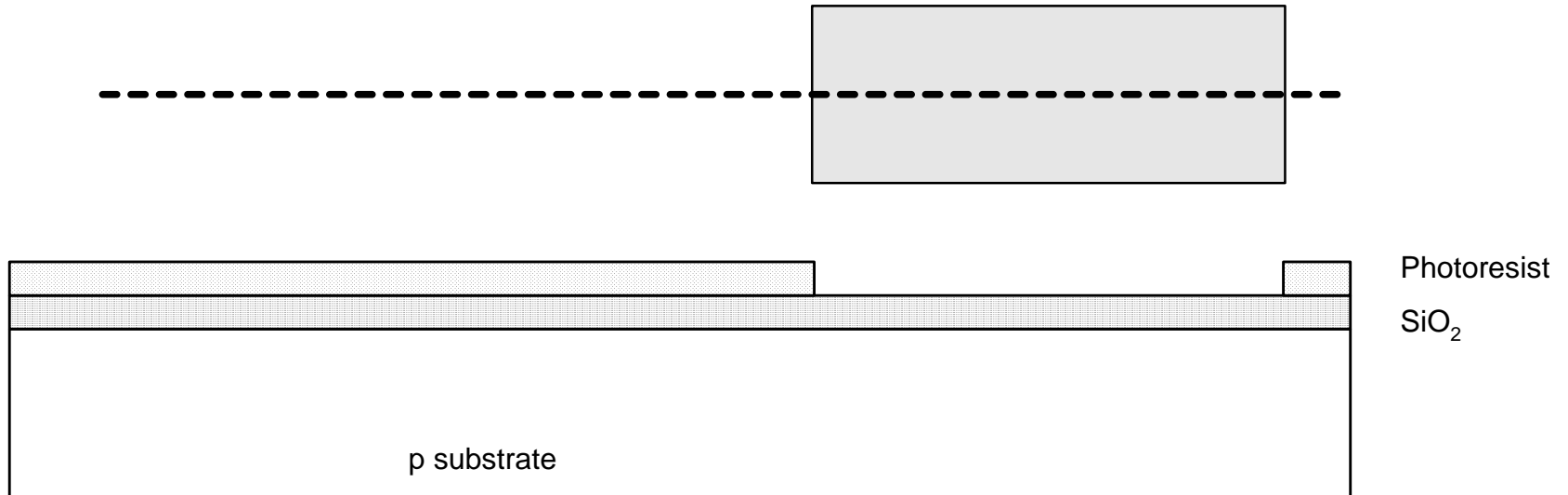- ☐ Expose photoresist through n-well mask
- ☐ Strip off exposed photoresist




Etch

 - ❑ Etch oxide with hydrofluoric acid (HF)
 - Seeps through skin and eats bone; nasty stuff!!!
- ❑ Only attacks oxide where resist has been exposed




Strip Photoresist

 - ❑ Strip off remaining photoresist
 - Use mixture of acids called piranha etch
- ❑ Necessary so resist doesn't melt in next step




n-well

 - ❑ n-well is formed with diffusion or ion implantation
- ❑ Diffusion
 - Place wafer in furnace with arsenic gas
 - Heat until As atoms diffuse into exposed Si
- ❑ Ion Implantation
 - Blast wafer with beam of As ions
 - Ions blocked by SiO_2 , only enter exposed Si




Strip Oxide

 - ❑ Strip off the remaining oxide using HF
- ❑ Back to bare wafer with n-well
- ❑ Subsequent steps involve similar series of steps




Polysilicon

 - ❑ Deposit very thin layer of gate oxide
 - $< 20 \text{ \AA}$ (6-7 atomic layers)
- ❑ Chemical Vapor Deposition (CVD) of silicon layer
 - Place wafer in furnace with Silane gas (SiH_4)
 - Forms many small crystals called polysilicon
 - Heavily doped to be good conductor




Polysilicon Patterning

 - ❑ Use same lithography process to pattern polysilicon




Self-Aligned Process

 - ❑ Use oxide and masking to expose where n+ dopants should be diffused or implanted
- ❑ N-diffusion forms nMOS source, drain, and n-well contact




N-diffusion

 - ❑ Pattern oxide and form n+ regions
- ❑ *Self-aligned process* where gate blocks diffusion
- ❑ Polysilicon is better than metal for self-aligned gates because it doesn't melt during later processing




N-diffusion cont.

 - ❑ Historically dopants were diffused
- ❑ Usually ion implantation today
- ❑ But regions are still called diffusion




N-diffusion cont.

 - ❑ Strip off oxide to complete patterning step




P-Diffusion

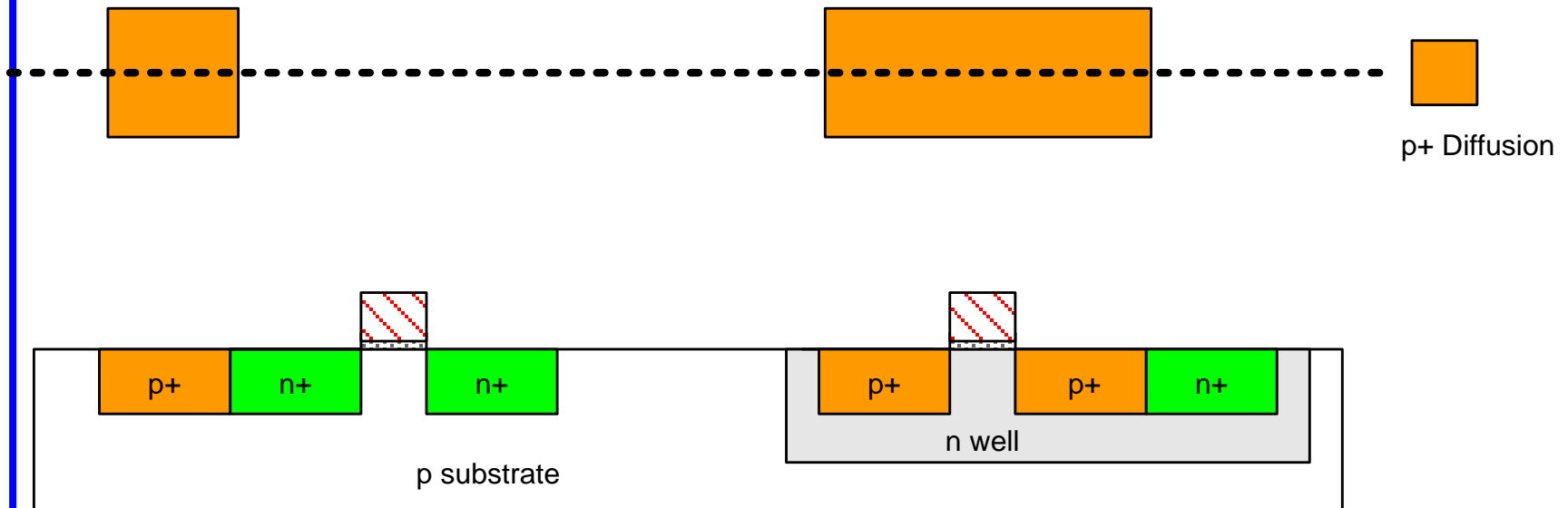- ❑ Similar set of steps form p+ diffusion regions for pMOS source and drain and substrate contact




Contacts

 - ❑ Now we need to wire together the devices
- ❑ Cover chip with thick field oxide
- ❑ Etch oxide where contact cuts are needed



Metalization

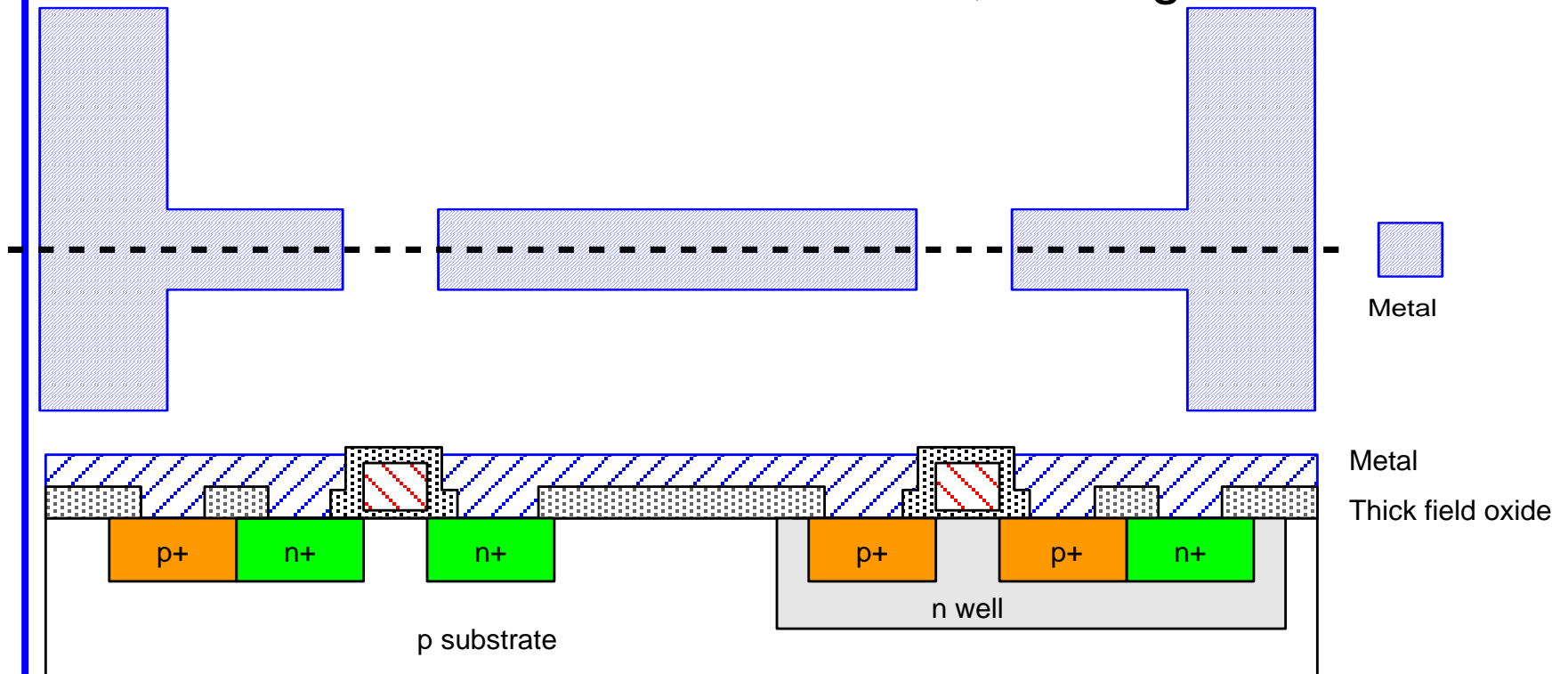
- ❑ Sputter on aluminum over whole wafer
- ❑ Pattern to remove excess metal, leaving wires



Manufacturing in the Fab




Advanced Metallization

 


Advanced Metallization

Dual damascene IC process


- Oxide deposition

 


- Stud lithography and reactive ion etch

 


- Wire lithography and reactive ion etch

 


- Stud and wire metal deposition

 

- Metal chemical-mechanical polish

 

Source: IBM Corp.

 

Layout


- ❑ Chips are specified with set of masks
- ❑ Minimum dimensions of masks determine transistor size (and hence speed, cost, and power)
- ❑ Feature size f = distance between source and drain
 - Set by minimum width of polysilicon
- ❑ Feature size improves 30% every 3 years or so
- ❑ Normalize for feature size when describing design rules
- ❑ Express rules in terms of $\lambda = f/2$
 - E.g. $\lambda = 0.3 \mu\text{m}$ in $0.6 \mu\text{m}$ process

Simplified Design Rules

- Metal and diffusion have minimum width and spacing of 4λ .
- Contacts are $2\lambda \times 2\lambda$ and must be surrounded by 1λ on the layers above and below.
- Polysilicon uses a width of 2λ .
- Polysilicon overlaps diffusion by 2λ where a transistor is desired and has a spacing of 1λ away where no transistor is desired.
- Polysilicon and contacts have a spacing of 3λ from other polysilicon or contacts.
- N-well surrounds pMOS transistors by 6λ and avoids nMOS transistors by 6λ .




Simplified Design Rules

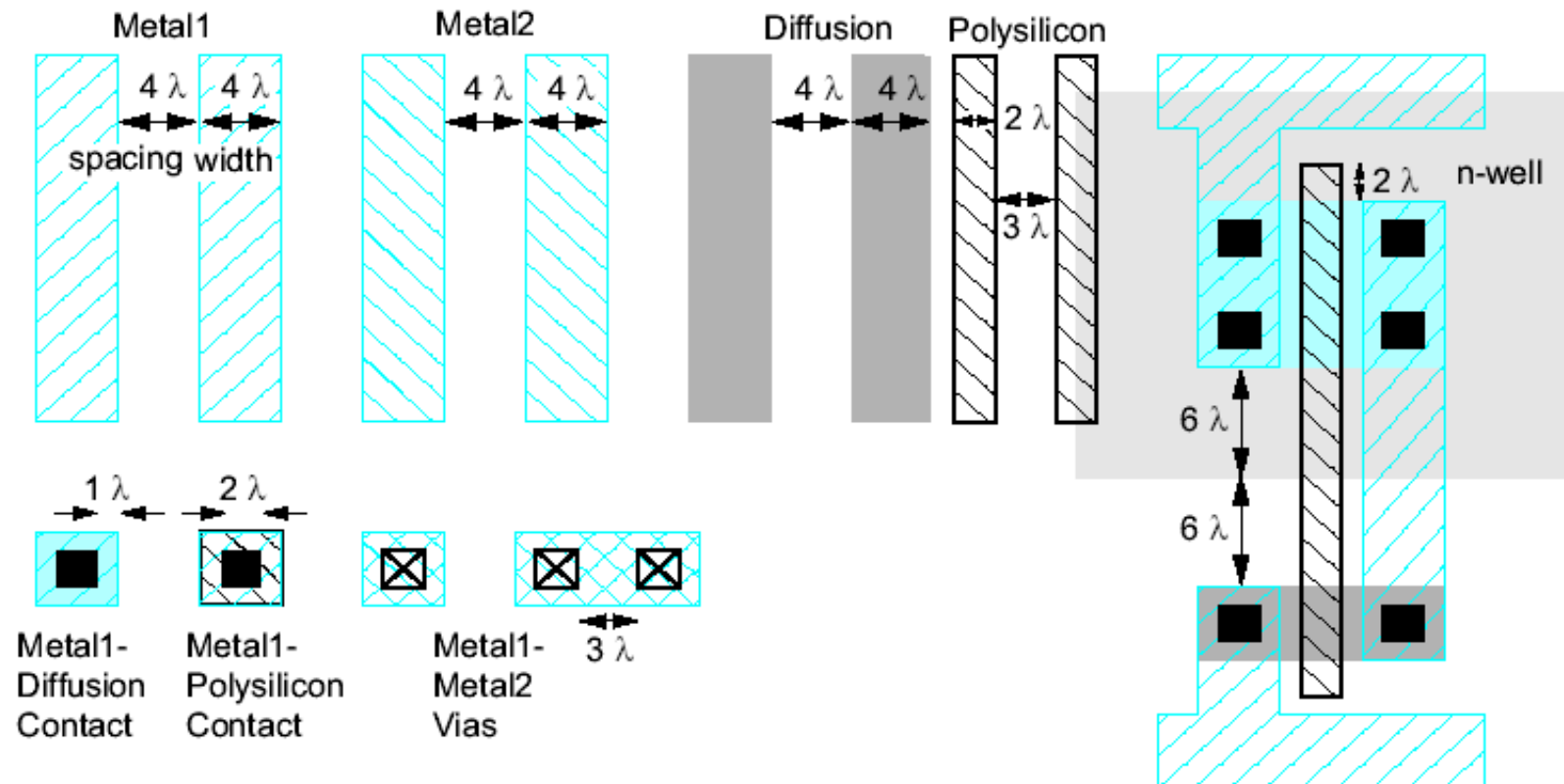- ❑ Conservative rules to get you started



Inverter Layout

   - ❑ Transistor dimensions specified as Width / Length
 - Minimum size is $4\lambda / 2\lambda$, sometimes called 1 unit
 - In $f = 0.6 \mu\text{m}$ process, this is $1.2 \mu\text{m}$ wide, $0.6 \mu\text{m}$ long





$$\begin{aligned}
 I_{ds} &= \frac{Q_{\text{channel}}}{L/v} \\
 &= \mu C_{\text{ox}} \frac{W}{L} (V_{gs} - V_t - V_{ds}/2) V_{ds} \\
 &= \beta (V_{GT} - V_{ds}/2) V_{ds} \\
 \beta &= \mu C_{\text{ox}} \frac{W}{L}; \quad V_{GT} = V_{gs} - V_t
 \end{aligned}$$

Summary

- ❑ MOS transistors are stacks of gate, oxide, silicon
 - ❑ Act as electrically controlled switches
 - ❑ Build logic gates out of switches
 - ❑ Draw masks to specify layout of transistors
-
- ❑ Now you know everything necessary to start designing schematics and layout for a simple chip!

Textbooks

  

Videos

- ❑ How Microchips Are Made by Learn Plus Fun

<http://www.dailymotion.com/video/x3xm5k9>

- ❑ From Sand to Silicon: Integrated Circuit Design and Manufacturing by Jas Lonnnquist and Jon Plutte

<http://www.computerhistory.org/revolution/digital-logic/12/288/2220>

- ❑ The Fabrication of Integrated Circuits

<http://www.dailymotion.com/video/x2mhml2>

- ❑ How a CPU is Made by Global Foundries

<http://www.wimp.com/how-a-cpu-is-made/>

- ❑ (Very old) Fairchild Briefing on Integrated Circuits

<http://www.computerhistory.org/collections/catalog/102651800>

Grading

- ☐ 80% written Exam
- ☐ 10% Witten Assignment, including homework
- ☐ 10% Lab Report