

# Layout of Analog CMOS Integrated Circuit

# Outline


- Introduction
- Process and Overview Topics
- Transistors and Basic Cells Layout
- Passive components: Resistors, Capacitors
- System level Mixed-signal Layout

# Part I: Process and Overview Topics



- CMOS process Overview
  - Generic CMOS cross-section
  - How layers form parasitic effects
  - Process gradients: die and wafer
- General Constrains
  - Design rules
  - Failure mechanisms
- High frequency/radio frequency considerations
  - EM fields near traces
  - Grounding, Shielding

# CMOS process Overview


 
## Single metal, single poly cross-section


  
## Triple metal, double poly cross-section





# CMOS Transistor

  

Improves the latch-up immunity

# Extended-drain Transistor

  


For high voltage performances  
(not symmetrical)

# Parasitic Elements in MOS

Series resistance

Overlap cap

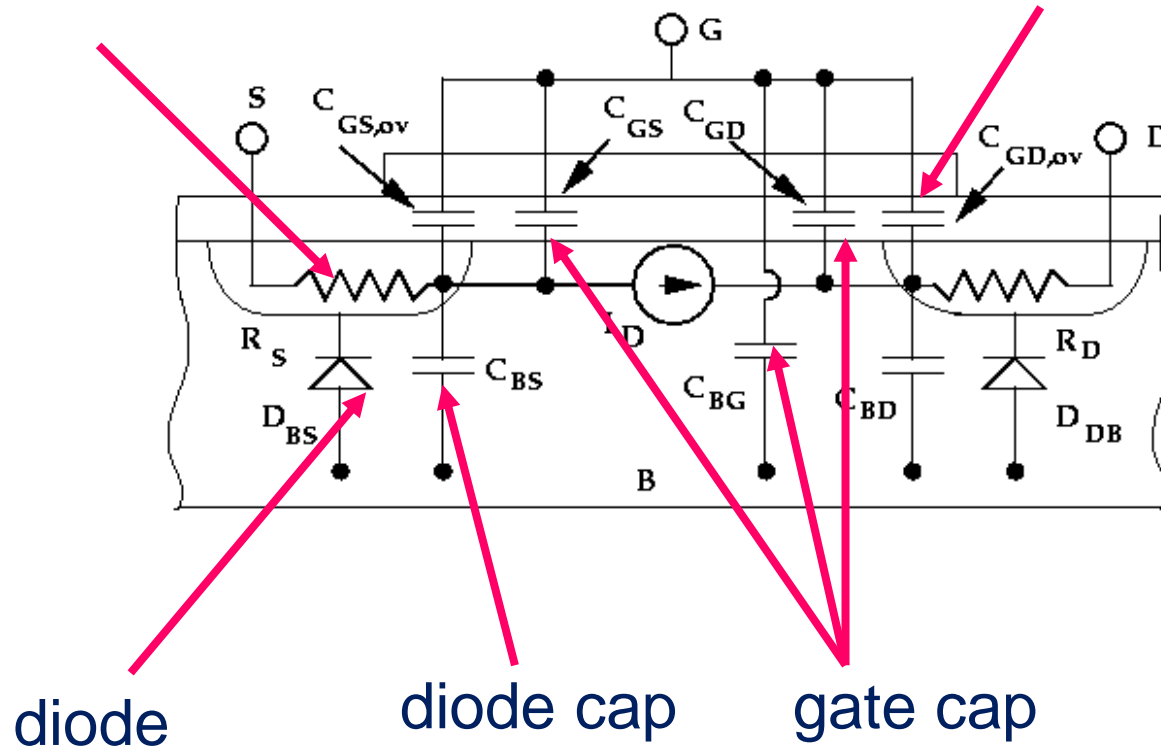

# Parasitic Resistance and Diode

Parasitic resistance: depends on the source or drain diffusion specific resistance

$$R_D \approx R_S \approx 10 - 50 \, \Omega$$

Diodes reversely biased; the reverse current is dominated by generation recombination term

$$I_{GR} = A \frac{q n_i x_j}{2 \tau_0}$$

$A$  : area of the junction

$x_j$  : depletion region width

$\tau_0$  : mean lifetime for minority carriers

$I_{GR}$  doubles for an increase of 10 K typically at room temperature



$$I_{GR}/A = 10^{-15} \, \text{A}/\mu\text{m}^2.$$



# How Layers form Parasitic

  
## ■ Coupling capacitance same layers

- lateral capacitance
- depends distance
- depends on layer thickness




 
## ■ Coupling between layers

- metals, poly, substrate
- layer-layer 5-10 aF/ $\mu^2$
- fringing cap 10-15 aF/ $\mu^2$




# Electrostatic Shield

  


Be sure that the shield bias is not a noise source!

# Cross-talk from Package

 


Metal lid  
Filling  
Ceramic Package

 

Plastic package  
low impedance at high freq.  
Interference paths  
Use shield on the top
 
# Long Interconnections

The distributed resistance and capacitance introduce a dispersion of the signal



$$T_D = \frac{1}{2} R_U C_U L^2$$

$R_U, C_U$  resistance and capacitance per unit length

# Part I: Process and Overview Topics

## ■ Basic Materials

- Silicon, Polysilicon,
- Silicon dioxide, Silicon nitride

## ■ CMOS process Overview

- Generic CMOS cross-section
- How layers form parasitic effects
- Process gradients: die and wafer

## ■ General Constrains

- Design rules
- Failure mechanisms


## ■ High frequency/radio frequency considerations

- EM fields near traces
- Grounding, Shielding

 
# Design Rules

- Design rules guarantee a proper yield despite tolerances in each step of the technology flow

- Minimum width and length
  - imposed by lithography and etching
- Minimum spacing
  - geometry's on the same mask
  - geometry's on different masks
- Minimum enclosure
  - a geometry must completely surround another
- Minimum extension
  - a geometry must completely cross another one



# Design Rules

 


# Failure Mechanisms

- Electrical Overstress
  - The antenna effect
- Corrosion
- Hot Carrier Effect
- Substrate Debiasing
- Electro-migration


 
# Electrical Overstress: antenna effect



- Electrical stress can break the gate oxide. Assuming  $4 \times 10^6$  V/cm dielectric strength, the maximum voltage across a 40 nm oxide is 16 V.
- During dry etching an ionized plasma charges conductors proportionally to their area. For large areas the resulting voltage can be disruptive (antenna effect)



The large metal 1 area is etched when the gate is not connected
  
# Corrosion

- Moisture favor the corrosion (oxidation) of aluminum
  - Minimize protective overcoat opening
  - Testpad for evaluation on a special mask
  - Scribe-line seal




# Hot Carrier Effect


High electric fields in the pinched-off region produce hot electrons

Hot electrons injected into the gate oxide shift the threshold voltage of the transistor

threshold shift:  
**AGING**

 

 
Hot carriers colliding with lattice atoms are deflected away from the drain




Low doped drain  
or drain extension
 
# Substrate Debiasing




- Current in the high resistive substrate lead to significant drop voltages
  - bias solidly the substrate (or epi)
  - but a protection ring around devices that can suffer by current injection



# Latch-up

 

 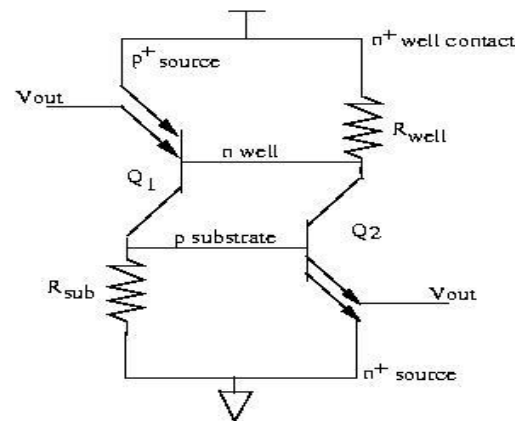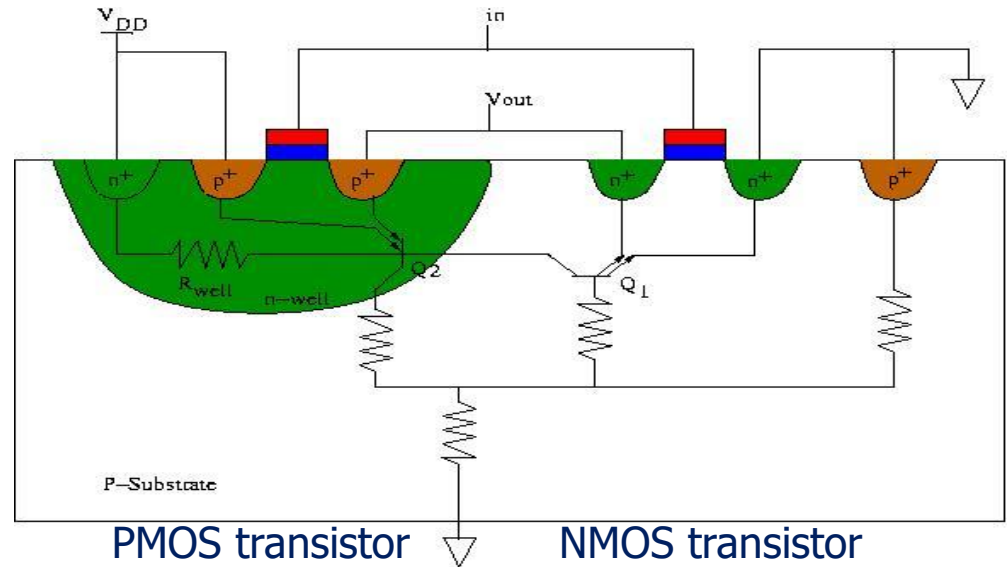Latch is the generation of a low-impedance path in CMOS chips between the power supply and the ground rails due to interaction of parasitic pnp and npn bipolar transistors.




# Electro-migration

- Electron flowing through the metal collide with atoms of the lattice. When the current density exceeds many  $10 \mu\text{A}/\mu^2$  metal atoms begin to move
- The displacement of atoms can produce a local thinning of the metal or gaps and, eventually, cause an open circuit
- A fraction of percent of copper added to the aluminum improves the electro-migration resistance
  - Large current requires thick or wide metal lines

# Part I: Process and Overview Topics


- CMOS process Overview
  - Generic CMOS cross-section
  - How layers form parasitic effects
  - Process gradients: die and wafer
- General Constrains
  - Design rules
  - Failure mechanisms
- High frequency/radio frequency considerations
  - EM fields near traces
  - Grounding, Shielding

# EM Field Near Traces

 



# Grounding, Shielding

 

The technique shown here creates a shield surrounding the signal traces that are connected to ground. This prevents signals from radiating out to other parts on the chip.

# Outline

- Introduction
- Process and Overview Topics
- **Transistors and Basic Cells Layout**
- Passive components: Resistors, Capacitors
- System level Mixed-signal Layout

# Part II: Transistor and Basic Cell Layout

## ■ Transistors and Matched Transistors

- ★ Layout of a single transistor
- ★ Use of multiple fingers
- ★ Interdigitated devices
- ★ Common Centroid
- ★ Dummy devices on ends
- ★ Matched interconnect (metal, vias, contacts)
- ★ Surrounded by guard ring

## ■ Design for Layout



- ★ Stacked layout of analog cells
- ★ Stick diagram of analog cells
- ★ Example 1: two stages op-amp
- ★ Example 2: folded cascode

# Single Transistor Layout

- A CMOS transistor is the crossing of two rectangles, polysilicon and active area
- but, ... we need the drain and source connections and we need to bias the substrate or the well


*Polysilicon gate*

*diffusion*

  

# Source and Drain Connections



- Ensure good connections

 



- Multiple contacts or one big contact?
  
# Multiple or single contacts?

- Curvature in the metal layer can lead to micro-fractures



- Not important for large areas

  


*Reliability problems, possible electro-migration*

# Matching single Transistors(Geometric Effects)

- Regular (rectangular shape)


- the W and L matter!!

 

**don't do!**


- Parallel elements

- silicon is unisotropic

 

 **don't do!**

- Possibly, the current flowing in the same direction





**OK!**

**OK!**

**Geometric Effects**
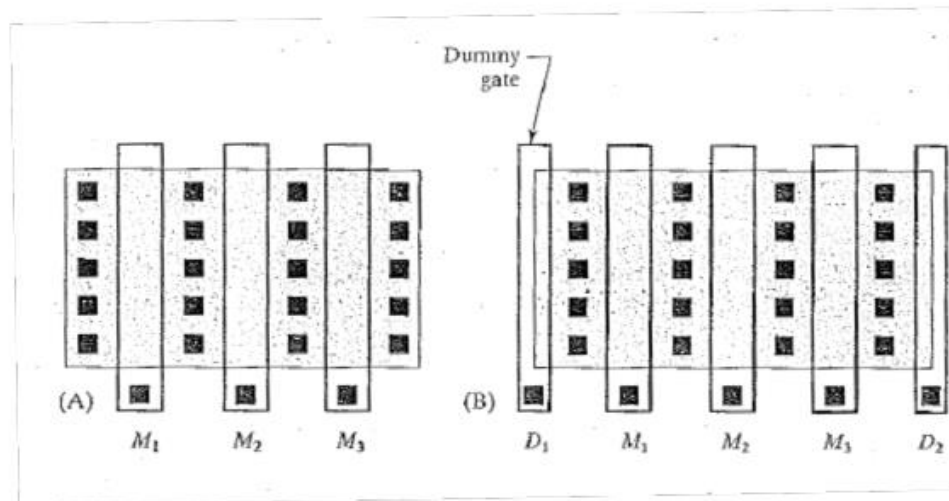 
# Etch Effects


- ❑ Polysilicon does not always etch uniformly
  - Large openings etch faster than small openings in mask
  - Solution is to use dummy structures





 
# Diffusion Effects

- ❑ Diffusion widens implanted region
  - Can affect doping of neighboring devices
  - Solution is to increase distance and use dummy structures that affect all transistors the same


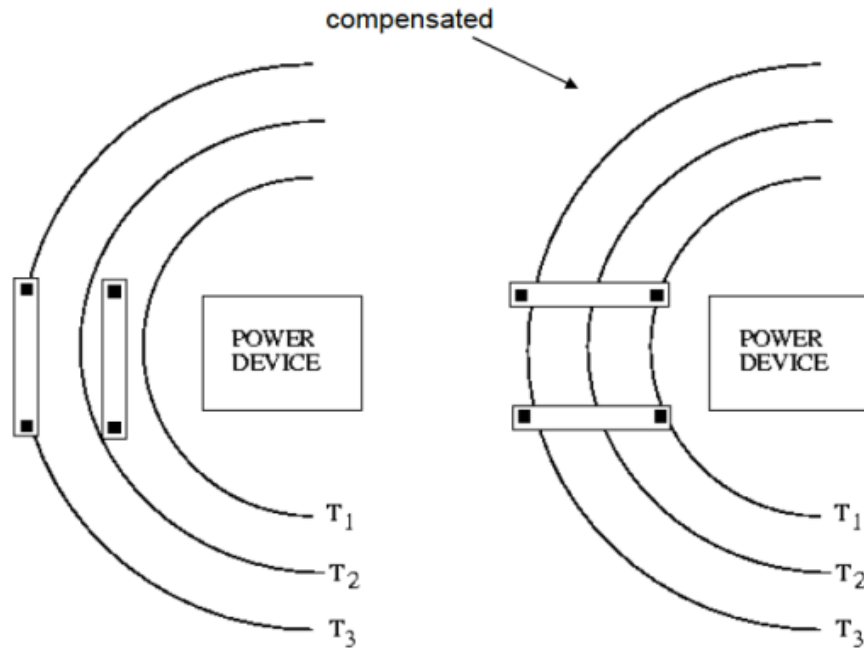
# Thermal Effects

- ❑ Temperature affects
  - Mobility and threshold voltage
  - Resistance value



# Stress Effects


- ❑ The fabrication under high temperatures may leave residual stresses in chip
- ❑ Packaging can cause stress in chip

## Solutions

- ❑ Keep critical matched devices in centre of chip or on centerlines
- ❑ Avoid using corners for matched devices
 
# Oxide Thickness Gradients


- ❑ Thermally grown oxides depend on temperature and oxidizing atmosphere
- ❑ Modern oxidation furnaces, although well controlled in temperature still have temperature gradients.



Oxide thickness on 200 mm wafer


# Common Centroid

❑ Matching Won't be good!!!

 
 
# Common Centroid


- Break and distribute parts of a transistor so as to cancel out the effects of oxide / doping gradient profiles.



# Transistor Matching


□ Example of Differential Pair

✗ Not matching with thermal gradients!!!

 

# Common Centroid Layouts


- Averages Process Variations

 


 
# Asymmetry due to Fabrication


An MOS transistor is not a symmetrical device. To avoid channeling of implanted ions the wafer is tilted by about  $7^\circ$ .



Source and drain are not equivalent
 
# Parasitics in Transistors

- Analog transistors often have a large W/L ratio




- Capacitance diffusion substrate

$$C_{SB} = C_{DB} = (W + 2l_{diff})(L_D + 2l_{diff})$$


- Resistance of the poly gate

$$R_{gate} = L_{gate} R_{sq, poly}$$

# Use of multiple fingers

 


$W/2$

 

$$C_{SB} = \frac{1}{2} C_{DB}; C_{DB} = C'_{DB}$$

$W/3$

 

$$C_{SB} = \frac{2}{3} C'_{SB}$$


$$C_{DB} = \frac{2}{3} C'_{DB}$$

# Parasitic in Transistors: Exercise


- Calculate the parasitic capacitance diffusion-substrate for a 40 micron width transistor
  - ★ one finger
  - ★ 5 finger
  - ★ 8 finger
- ★ Use the design rules available and minimum diffusion length
 
# Interdigitated Devices


- Two matched transistors with one node in common
  - split them in an equal part of fingers (for example 4)
  - interdigitate the 8 elements: AABBAABB or ABBAABBA



# Axis of Symmetries

 


# Common Centroid

 


- Gradients in features are compensated for (at first approximation)
  - metal and poly interconnections are more complex

# Common Centroid Arrays

 

Cross coupling

 

Tiling (more sensitive to high-order gradients)




# Common Centroid Patterns

ABBA BAAB	ABBAABBA BAABBAAB	ABBAABBA BAABBAAB ABBAABBA	ABBAABBA BAABBAAB BAABBAAB ABBAABBA
ABA BAB	ABAABA BABBAB	ABAABA BABBAB ABAABA	ABAABAABA BABBABBAB BABBABBAB ABAABAABA
ABCCBA CBAABC	ABCCBAABC CBAABCCBA	ABCCBAABC CBAABCCBA ABCCBAABC	ABCCBAABC CBAABCCBA CBAABCCBA ABCCBAABC
AAB BAA	AABBAA BAAAAB	AABBAA BAAAAB AABBAA	AABBAA BAAAAB BAAAAB AABBAA
 
# Dummy Devices on Ends


- Ending elements have different boundary conditions than the inner elements -> use dummy




- Dummies are shorted transistors
  - Remember their parasitic contribution!
 
# Matched interconnections


- Specific resistance of metal lines
  - Specific resistance of poly
  - Resistance of metal-contact
  - Resistance of via
- $$\Delta V = Z_{int} I$$
- Minimize the interconnection impedance
  - Achieve the same impedance in differential paths
  - Keep short the width of fingers for high speed applications



# Matched Metal Connection

 

# Waffle Transistor

 

Minimum capacitance  
drain-substrate and  
source-substrate

W not accurate  
L not well defined

To be used in wide transistors  
whose aspect ratio is not  
relevant

# Part II: Transistor and Basic Cell Layout

## ■ Transistors and Matched Transistors

- ★ Layout of a single transistor
- ★ Use of multiple fingers
- ★ Interdigitated devices
- ★ Common Centroid
- ★ Dummy devices on ends
- ★ Matched interconnect (metal, vias, contacts)
- ★ Surrounded by guard ring

## ■ Design for Layout



- ★ Stacked layout of analog cells
- ★ Stick diagram of analog cells
- ★ Example 1: two stages op-amp
- ★ Example 2: folded cascode

# Stacked Layout


- Systematic use of stack or transistors (multi-finger arrangement)
- Same width of the fingers in the same stack, possibly different length
- Design procedure
  - ★ Examine the size of transistors in the cell
  - ★ Split transistors size in a number of layout oriented fingers
  - ★ Identify the transistors that can be placed on the same stack
  - ★ Possibly change the size of non-critical transistors
  - ★ Use (almost) the same number of finger per stack
  - ★ place stacks and interconnect




# Stick Representation (one transistor)

  

EVEN

 


Ending drain

 

Ending source

ODD

 


S/D ending



D/S ending




# Multi-transistor Stick Diagram

 

1 | 2 | 3 | 4  
Same width

2 | 1 | 2 | 3 | 4  
M1 double

1 | 2 | 1 | 2 | 3 | 2 | 3 | 4 | 3 | 4  
M1 M2 M3

 


3 | 4 | 3 | 2 | 1 | 2 | 3 | 4 | 3  
M3 M2 M1 M2 M3

3 | 4 | 3 | 2 | 1 | 2 | 1 | 2 | 3 | 4 | 3  
M3 M2 M1 M2 M3


# Example 1 (2 stages OTA)

Assume to layout a two stages OTA

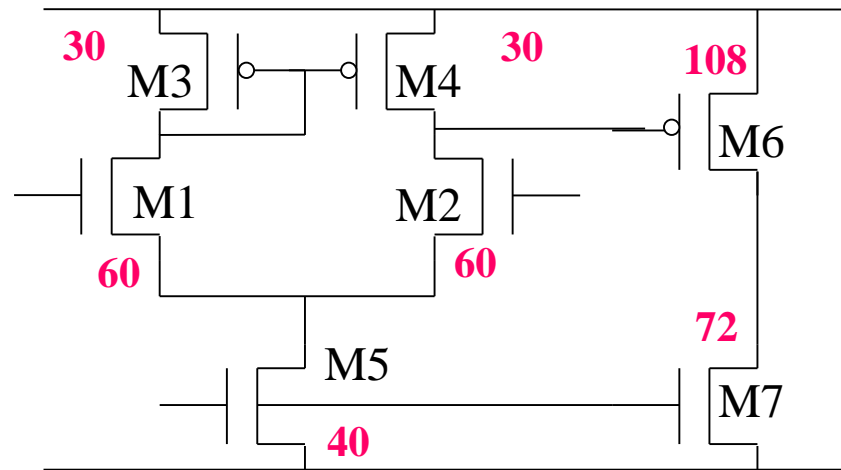

Width only are shown;  
Compensation network and bias are missing (!)

# Layout Oriented Design

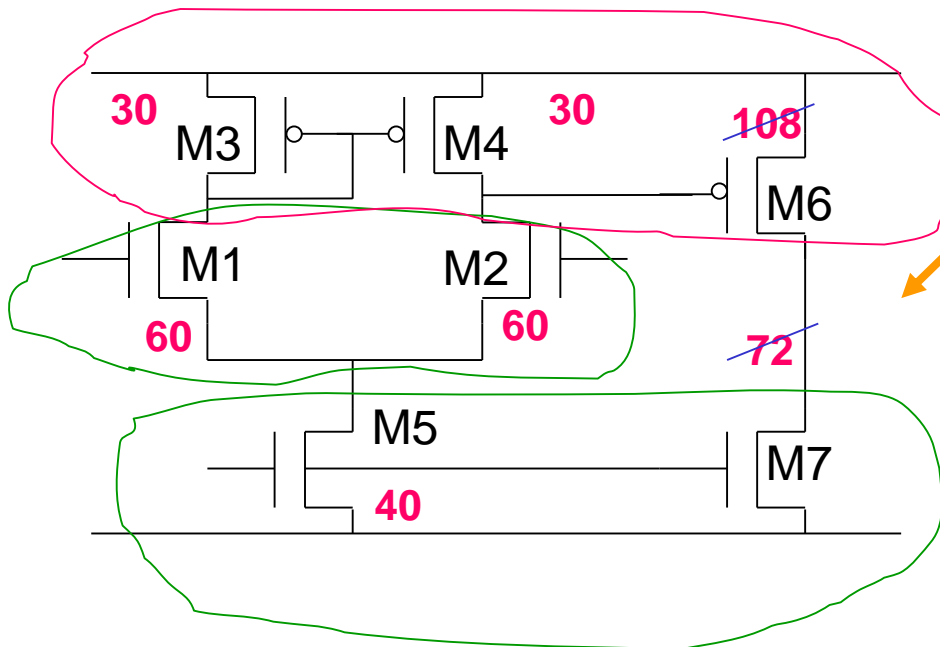

Only width matters

Possible stacks:  
1 p-channel, 2 n-channel

change the size of M6 and M7  
to 80 and 120 respectively

Width of each finger?

We want the same number of  
fingers per stack (k).

$$W_{p1} = 180/k$$

$$W_{n1} = 120/k$$

$$W_{n2} = 120/k$$

for M3 and M4 use 2 fingers



M3, M4, M6





M1, M2





M5, M7

# Stack Design and Interconnections

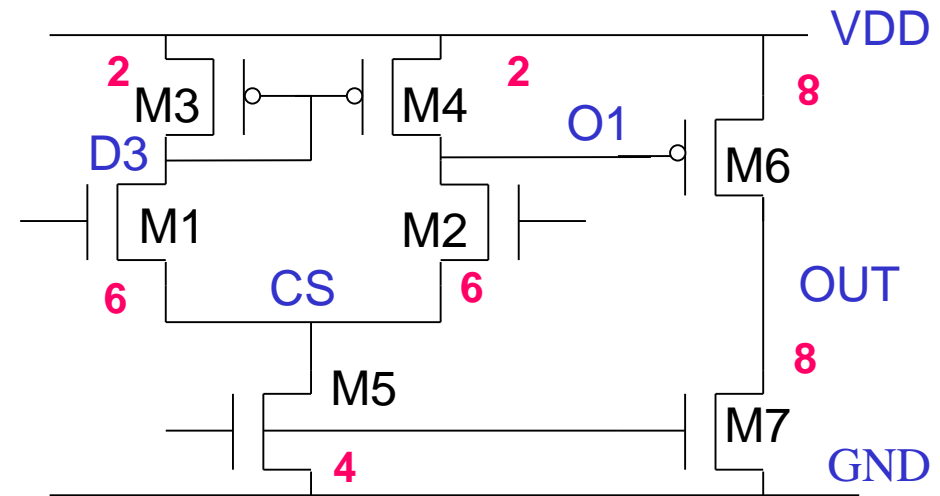 

First attempt of interconnections (not completed)

# Use of one Metal Layer

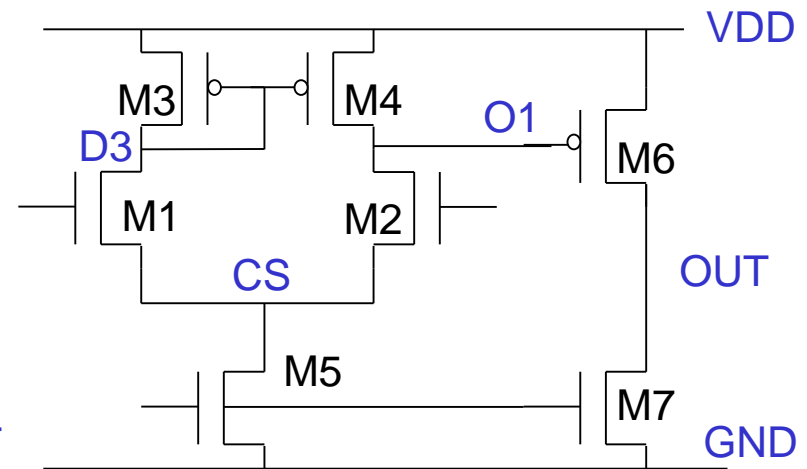 


Use metal for carrying current!  
Poly connections are not a problem (usually)

# Stick Layout: Exercise


Draw the stick diagram of the two stages OTA in the following three cases:

- fingers of M6 and M7 all together
- $M6 = 90$   $M7 = 60$
- M1 and M2 in a common centroid arrangement

# From Stick to Layout

 


## Example 2 (Folded Cascode)


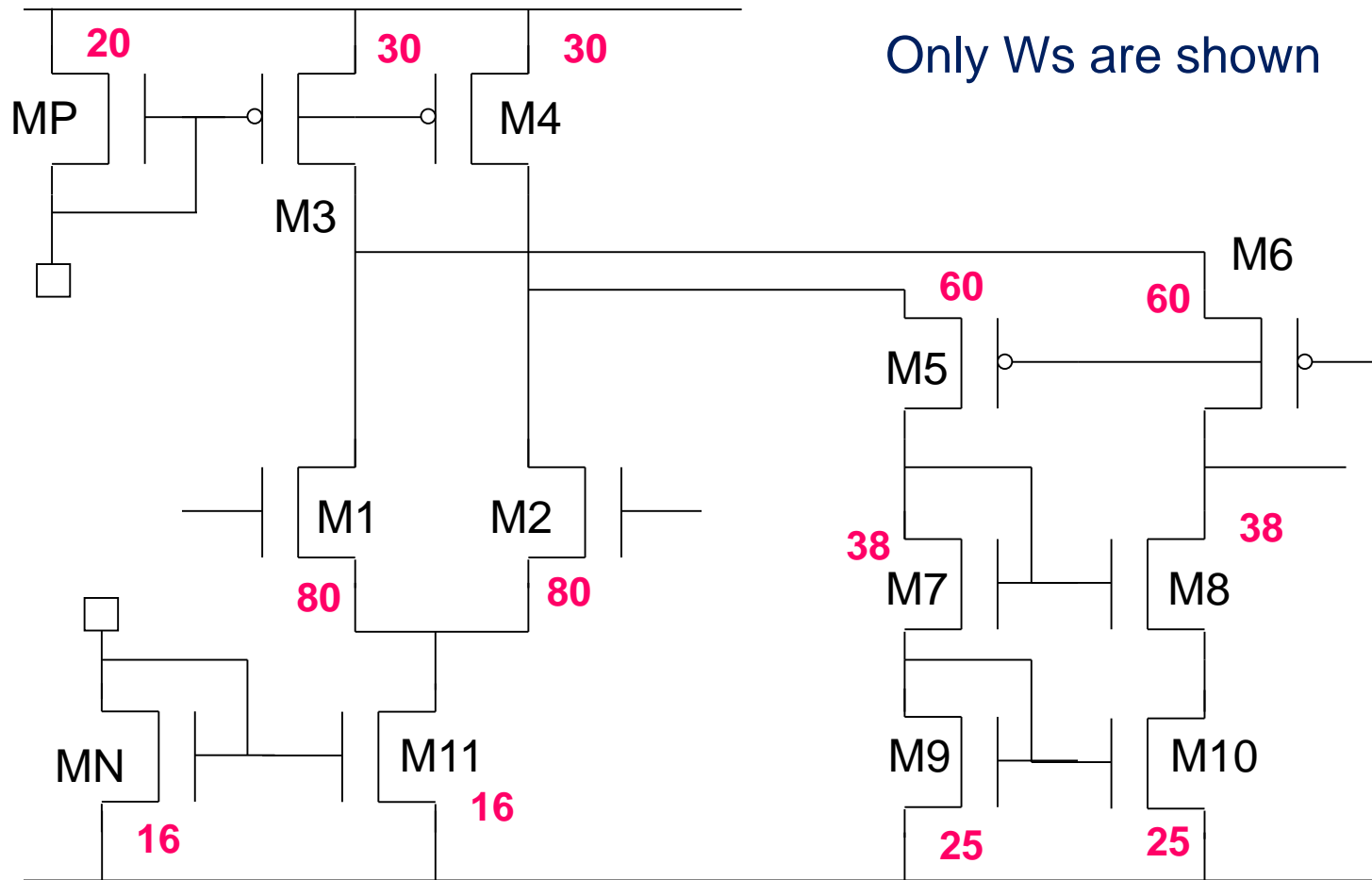




# Split of Transistors

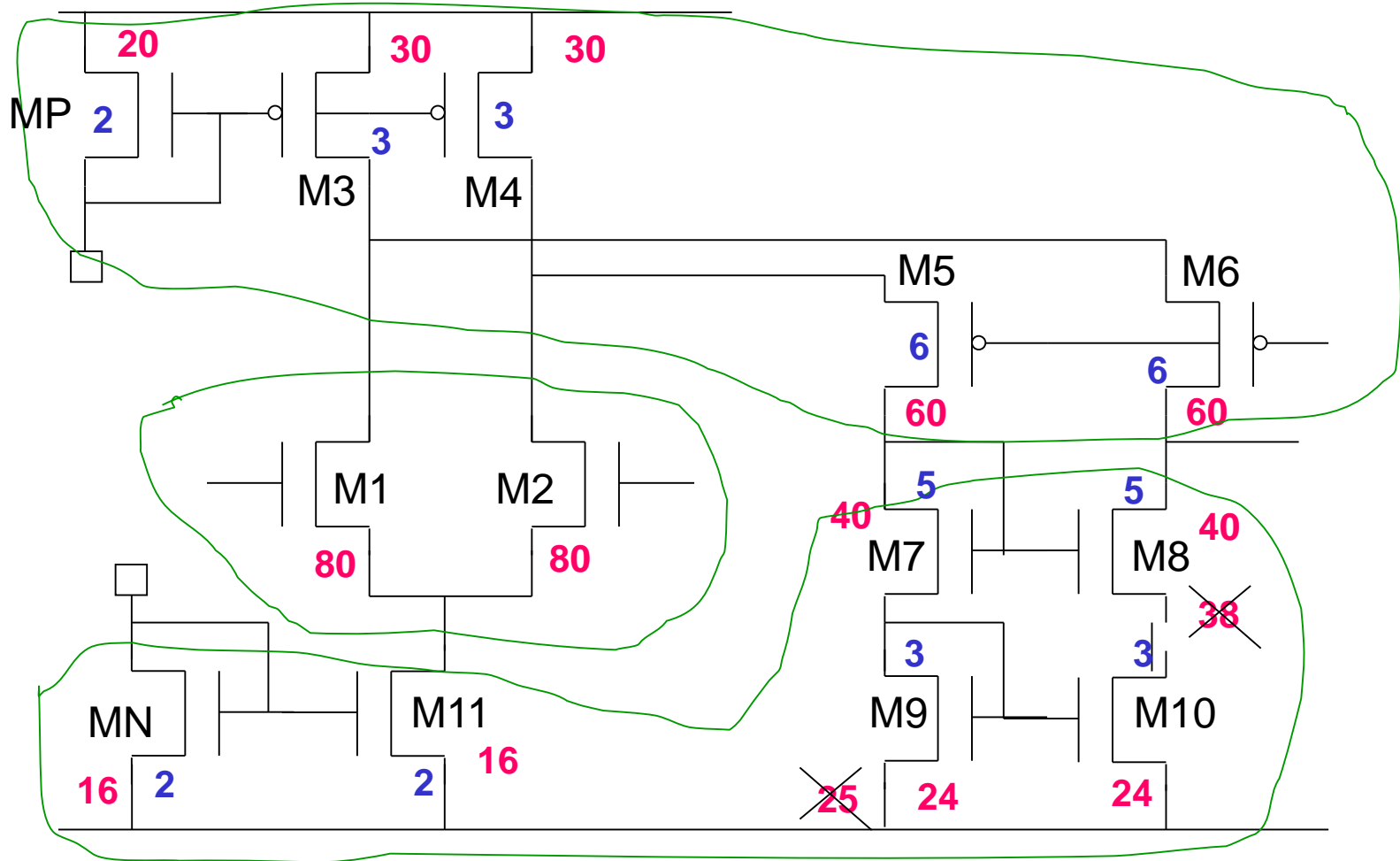


# Stack Design

 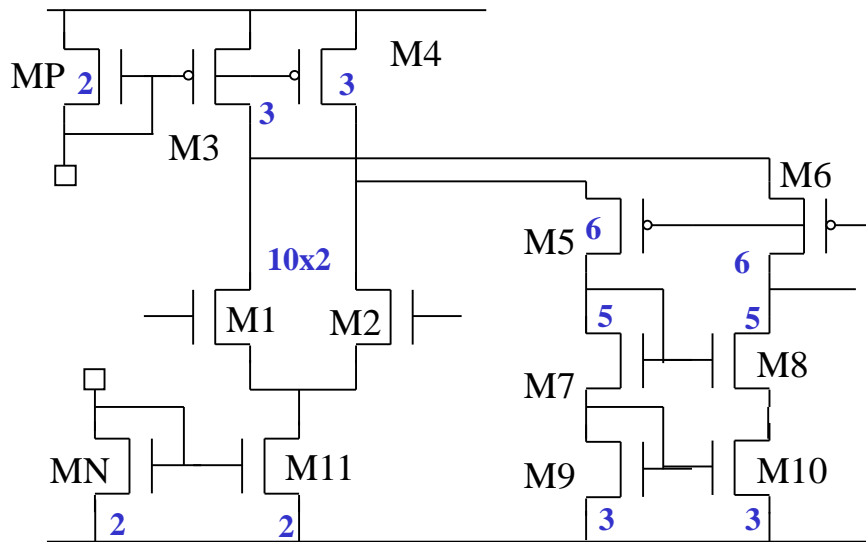

$X=11; o=10$
 
# Interconnection: Exercise

Sketch the source-drain interconnections of the folded-cascode



# Basic Cell Design: check-list


- Draw a well readable transistor diagram
- Identify critical elements and nodes
  - Absolute and relative accuracy
  - Minimum parasitic capacitance
  - Minimum interference
- Mark transistors that must match
- Mark symmetry axes
- Analyze transistor sizing (W's)
- Possibly, change transistor size for a layout oriented strategy
- Group transistors in stacks
- Define the expected height (or width) of the cell
- Sketch the stick diagram
  - transistors of the same type in the same region
- Foresee room for substrate and well biasing
  - substrate bias around the cell
  - well-bias surrounding the well
- Define the connection layer for input-output (horizontal, vertical connections)
- **Begin the layout now!!**

# Outline


- Introduction
- Process and Overview Topics
- Transistors and Basic Cells Layout
- **Passive components: Resistors, Capacitors**
- System level Mixed-signal Layout
 
# Integrated Capacitors

Capacitors in IC are parallel plate capacitors



No fringing effect →

 


$$C = \frac{\epsilon_0 \epsilon_r}{t_{ox}} WL$$

Material	Rel. Permittivity	Diel. Strength
SiO <sub>2</sub> Dry Oxide	3.9	11 V/nm
SiO <sub>2</sub> Plasma	4.9	3-6 V/nm
Si <sub>3</sub> N <sub>4</sub> LPCVD	6-7	10 V/nm
Si <sub>3</sub> N <sub>4</sub> Plasma	6-9	5 V/nm


# Types of Integrated Capacitors



Poly-poly

 


Sandwich

 

Lateral plates  
(flux capacitor)




Poly- diffusion

 

Poly-channel

# Layout of Capacitors

 


## To achieve good matching :

- Use of unity capacitors connected in parallel
- Use  $W = L$  fairly large





# Flux Capacitor Layout

 

- Use of the same metal layer
- Exploit the lateral flux
- The parasitic capacitance plate -substrate is low because the metal sits on thick oxide
- Use thick metal layers
- Maximize the perimeter (use of fractals)
- Very good matching!


# Common Centroid Structures

  

$$\begin{aligned} C_2 &= C_1 \\ C_3 &= 2C_1 \\ C_4 &= 4C_1 \\ C_5 &= 8C_1 \end{aligned}$$
 
# Fringing Effect

- Equation  $C = \frac{\epsilon_0 \epsilon_r}{t_{ox}} WL$  is an approximation



$$C = \frac{\epsilon_0 \epsilon_r}{t_{ox}} (W - t_{ox})(L - t_{ox}) + C_{fring}$$

- Fringing depends on the boundary conditions

# MOS Capacitors Features


Type	$t_{\text{ox}}$ nm	Accuracy %	Temperature Coefficient ppm/°C	Voltage Coefficient ppm/V
poly - diff.	15 - 20	7 - 14	20 - 50	60 - 300
poly I - poly II	15 - 25	6 - 12	20 - 50	40 - 200
metal - poly	500 - 700	6 - 12	50 - 100	40 - 200
metal - diff.	1200 - 1400	6 - 12	50 - 100	60 - 300
metal I - metal II	800 - 1200	6 - 12	50 - 100	40 - 200

# Rules for Capacitor Matching

- Use identical geometries
- Use large unit capacitance (minimize fringing)
- Use common centroid arrangement
- Use dummy capacitors
- Use shielding
- Account for the connections' contribution
- Don't run connections over capacitor
- Place capacitor in low stress areas
- Place capacitors far from power devices
 
# Integrated Resistor Cross-section


- A resistor is made of a strip of resistive layer.




$$R = 2R_{\text{cont}} + \frac{L}{W} R_{\square}$$

- The endings resistance can be significant!


# Diffusion/Well Resistors

 

**Diffused resistance**

 


**well resistance**

 


**Pinched n-well resistance**


# Polysilicon Resistances

 


e) **First polysilicon resistance**

 

 f) **First polysilicon resistance with a well shielding**



g) **Second polysilicon resistance**

 


h) **Second polysilicon resistance with a well shielding**

Conductive layers can be used to shield the conductor-oxide-conductor structure




# Well or Pinched-well Resistors

 

- Well layers have a large specific resistance

but

 - They have a large voltage and temperature coefficient
- They are weakly insulated from the surrounding
- Layers close to the surface contribute to the conductivity



# Large Value Resistors

In order to have large value resistors :

- Use of long strips (large  $L/W$ )
- Use of layers with high sheet resistance (bad performances)


Layout : rectangular “snake”

(!!)


Resistance at the corners

Current flows in different directions

 **DON'T USE IT IN PRECISE  
APPLICATIONS!**



# Prevent Current Leakage!

 

# Features of Resistors

Type of layer	Sheet Resistance $\Omega/\square$	Accuracy %	Temperature Coefficient ppm/ $^{\circ}\text{C}$	Voltage Coefficient ppm/V
n + diff	30 - 50	20 - 40	200 - 1K	50 - 300
p + diff	50 - 150	20 - 40	200 - 1K	50 - 300
n - well	2K - 4K	15 - 30	5K	10K
p - well	3K - 6K	15 - 30	5K	10K
pinched n - well	6K - 10K	25 - 40	10K	20K
pinched p - well	9K - 13K	25 - 40	10K	20K
first poly	20 - 40	25 - 40	500 - 1500	20 - 200
second poly	15 - 40	25 - 40	500 - 1500	20 - 200

# Effect of Etching


Wet etching : isotropic (undercut effect)

$H_F$  for  $SiO_2$  ;  $H_3PO_4$  for Al

$\Delta x$  for polysilicon may be  $0.35 - 0.5 \mu$  with standard deviation  $0.02 \mu$ .

Reactive ion etching (R.I.E.)(plasma etching associated to “bombardment”) : unisotropic.

 
$\Delta x$  for polysilicon is  $0.2 \mu$  with standard deviation  $0.015 \mu$




## Boundary :

The etching depends on the boundary conditions

Use of dummy strips

 

# Interdigitized and Common Centroid

 


**Exercise:** draw a 121212121212 connection and compare the two solutions



**Exercise:** draw a common centroid structure (12 elements per resistor)
 
# Adjusting Resistor Values

Sliding contact:  
requires to change the  
contact mask only



Metal fuse  
and  
Poly-fuse

  


# Outline


- Introduction
- Process and Overview Topics
- Transistors and Basic Cells Layout
- Passive components: Resistors, Capacitors
- **System level Mixed-signal Layout**



# Layout of Switches

 


# Reference Current Distribution

 

$V_{GS}$  voltage  
distribution

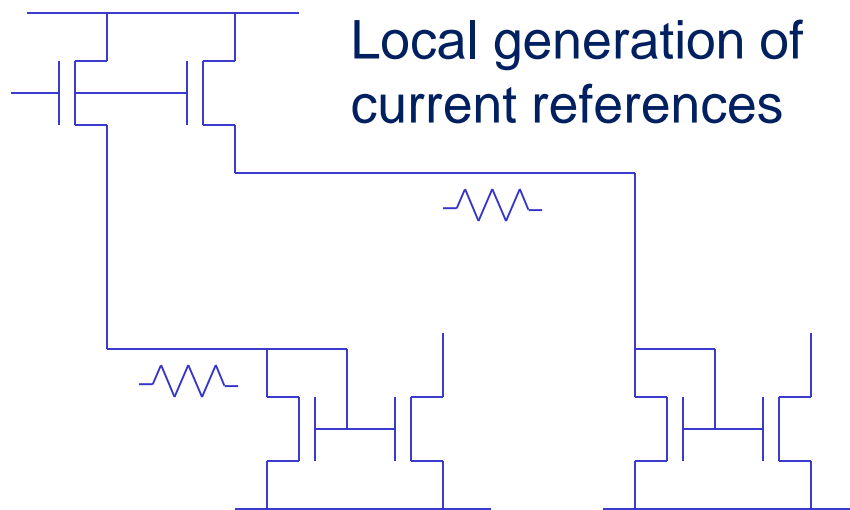Drop voltage on the  
“ground” connection





Reference currents  
distribution

Drop voltage on the  
wire connection
  
# Cross-talk and Shielding

- Crossing of metal lines carrying analog and digital signals cause cross-talk between signals.
  - ★ Make disturbances differential
  - ★ Use shielding lines in mixed signal busses



# Switched Capacitor Circuits

- **Floor plan of a SC circuit**
  - ★ Single ended circuits
  - ★ Fully differential circuits
  - ★ Respect symmetries
  - ★ Wide supply routes
  - ★ Separation between analog and digital


# Standard Cell like Approach

Cells with the same width and different length

$V_{DD}$  and  $V_{SS}$  on the top and bottom

Input and output on the two sides

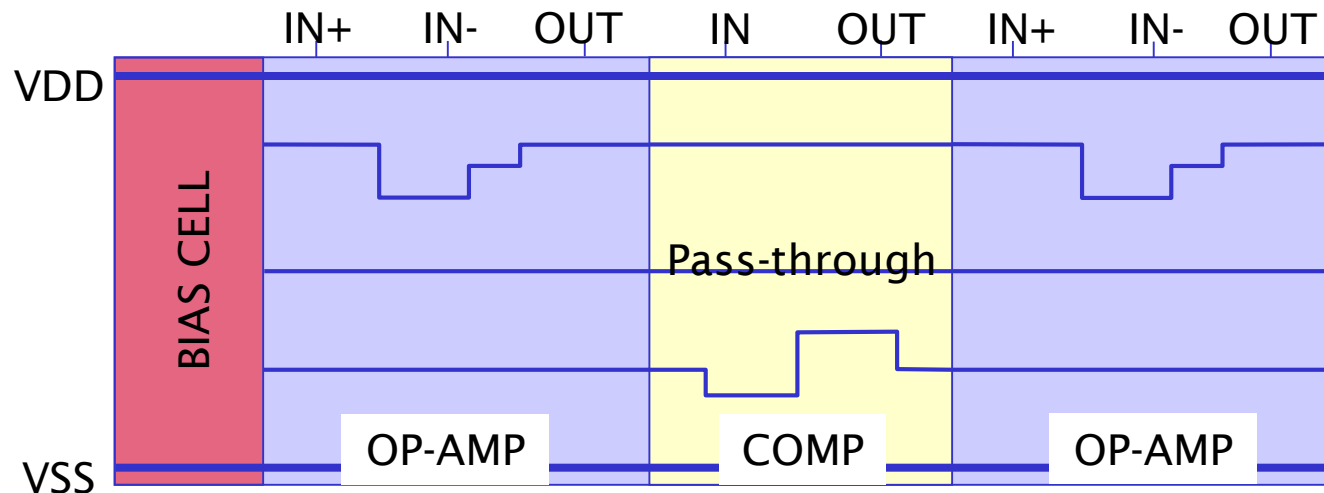- Layout of basic blocks Standard cell oriented



# Single-ended SC Floor Plan


Clock phases  
Switches

Capacitor array  
Underneath well  
Substrate bias around

Analog bus

Analog cells

Analog bus

 

# Fully-Differential SC Floor Plan

Clock phases

Switches

Capacitor array

Analog bus


Analog cells

Analog bus


Capacitor array

Switches

Clock phases

 

# Fully-Differential SC Floor Plan (2)

 




# Analog Floor-plan

- List of active cells: op-amp, comparators, biases
- Area estimation (interconnection/biasing area ~ 50%)
- List of passive components & switches
  - ★ accuracy requests and shielding needs
  - ★ Matching of resistors/capacitors
- Estimate the silicon area
- Define the aspect ratio of the analog section
- Placement of active cells
- Placement of passive components
- Placement of switches


# Analog Floor-plan: Example

## 10-bit two-step flash converter

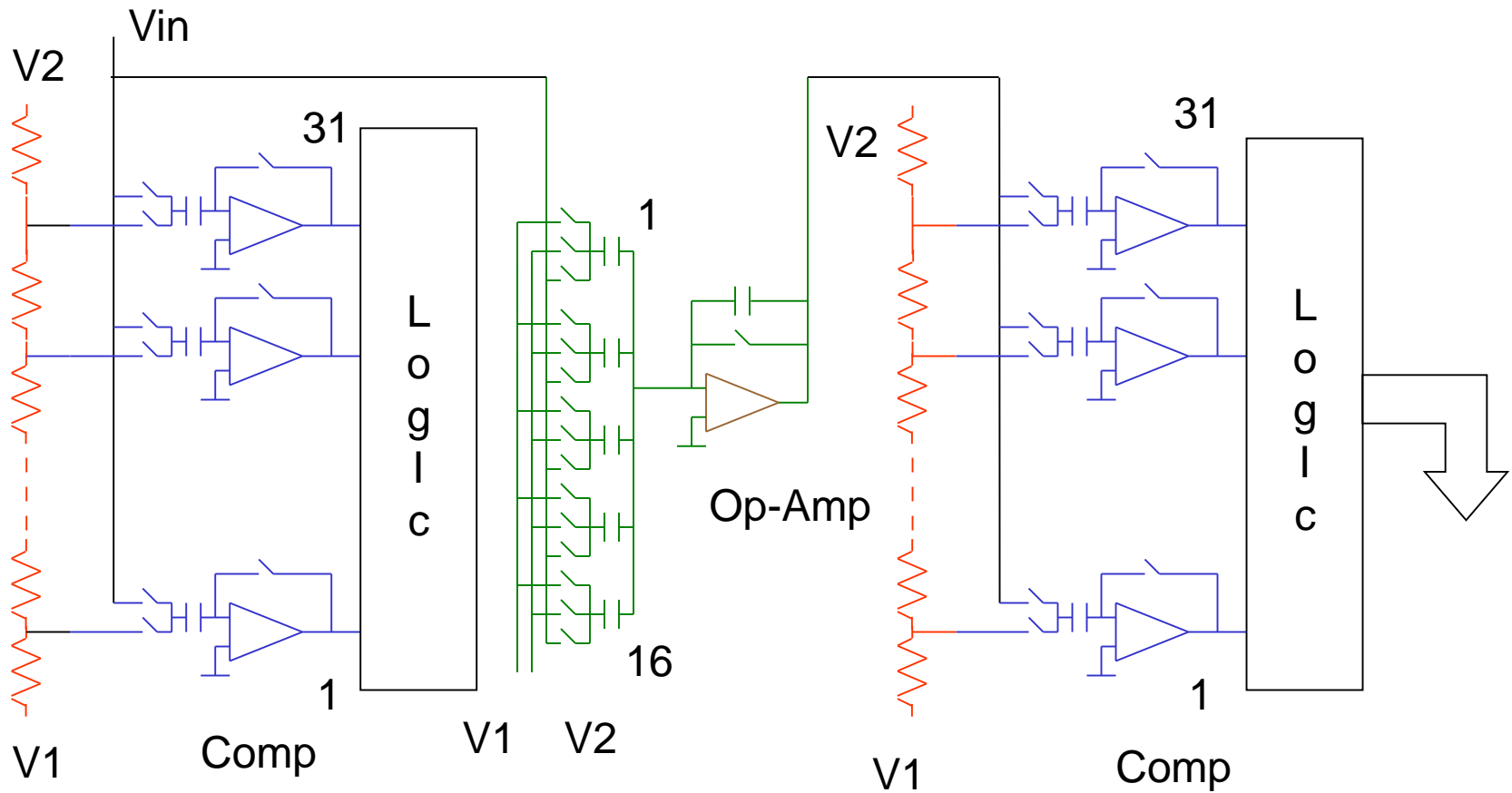

# Analog Floor-plan: Example (2)

## 10-bit two-step flash converter

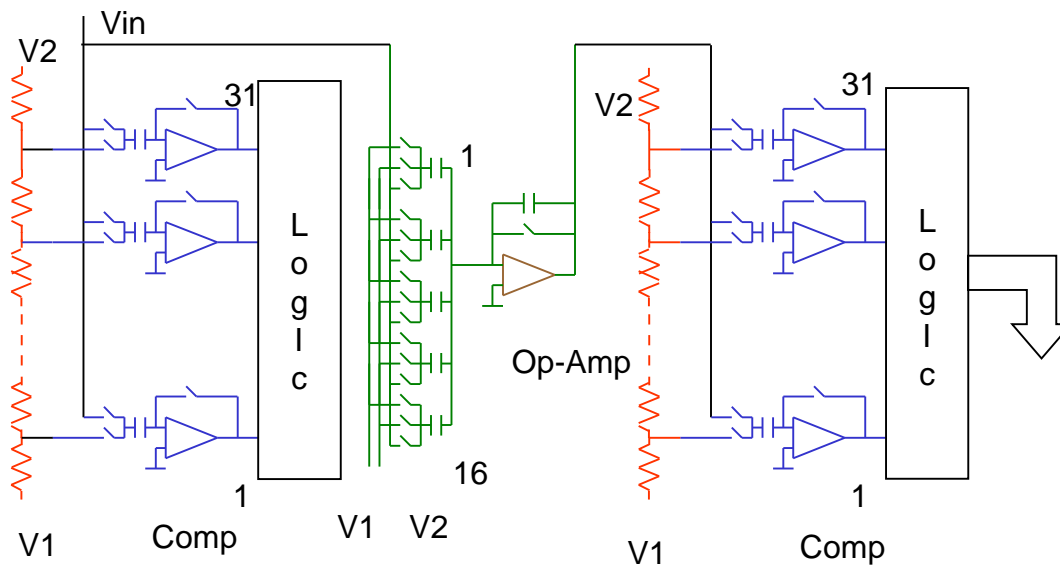


62 Comparators  
1 Op-amp

62 autozero nets  
2 Res. String (32)  
1 Cap. Array 32

2 Logic

# Analog Floor-plan: Example (3)

## 10-bit two-step flash converter

 


62 Comparators  
1 Op-amp

62 autozero nets  
2 Res. String (32)  
1 Cap. Array 32

2 Logic


Logic (shape is flexible)

# Analog Floor-plan: Example (3)

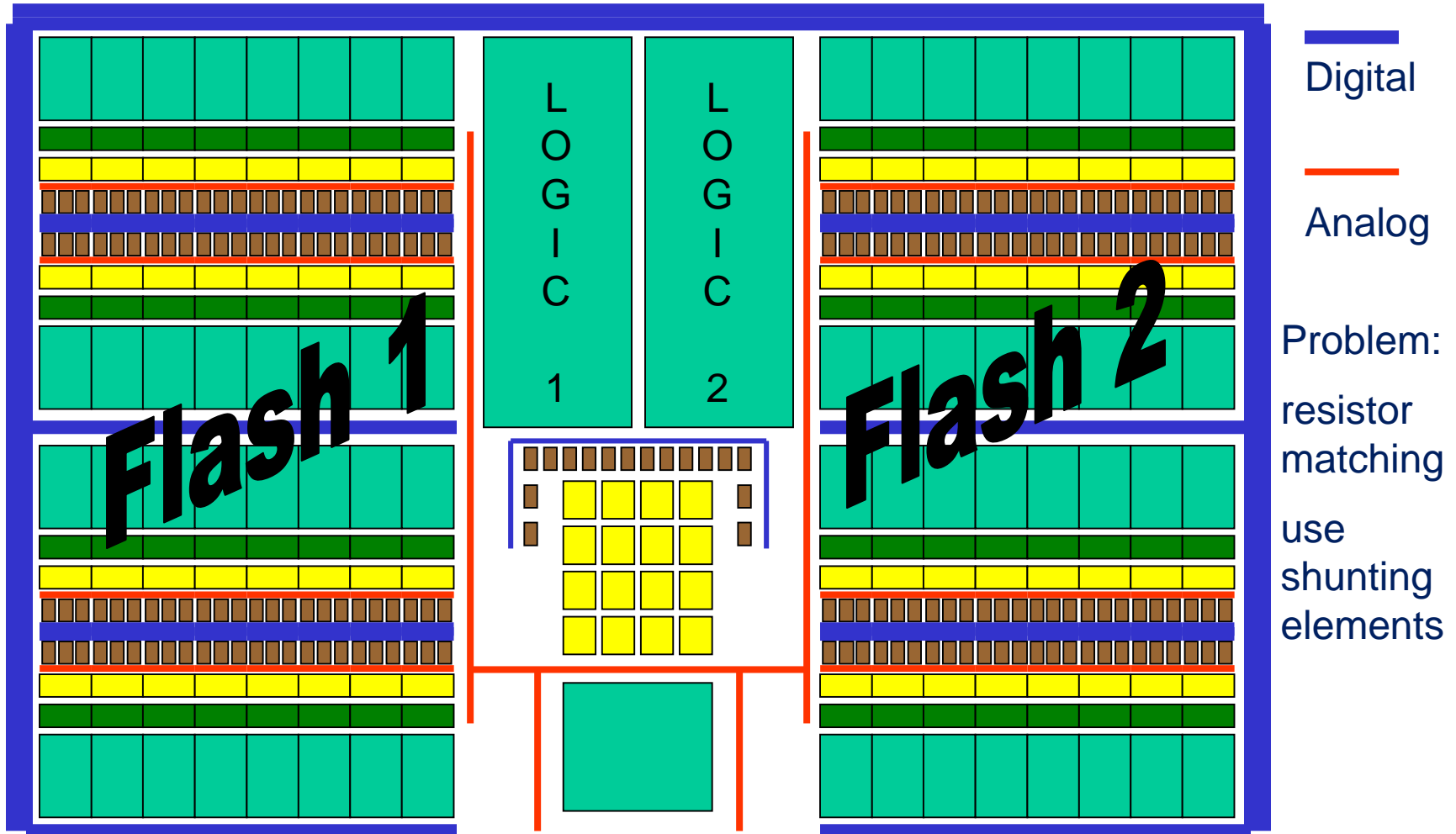

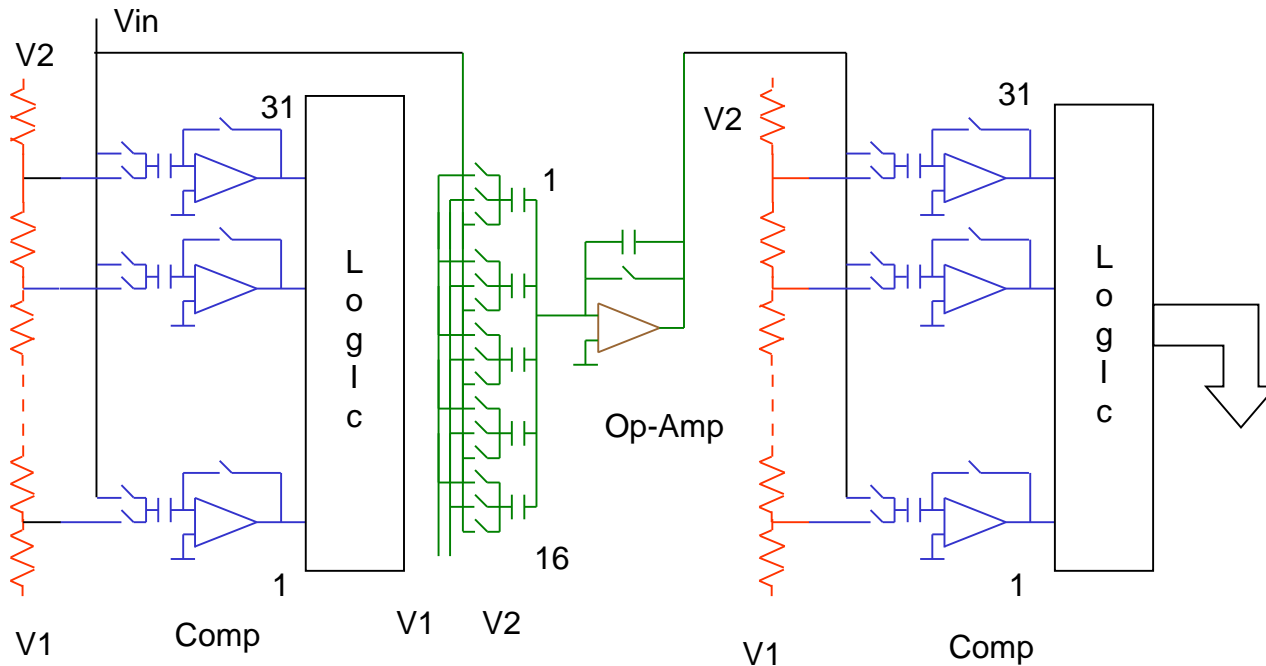
# Analog Floor-plan: Exercise

Sketch a new floor-plan of the 10 bit two-step flash. The goal is to have a good integral non-linearity (the resistor strings used in the previous slide are affected by a large gradient error).



# Mixed-signal floor-plan

 

# Mixed-signal Layout: check-list

- Draw a well readable system diagram
- Identify critical blocks and connections
  - ★ sensitive nodes
  - ★ critical paths
- Mark passive components that must match
- Mark symmetry axes
- Roughly estimate area of active cells
- Roughly estimate area of passive elements
- Study a possible placement and change the aspect ration of basic cells accordingly
- Define the analog and digital routing path
- **Begin the layout of the basic cells now!!**
- Change the Floor plan of the system in feedback
- Place plenty of guard rings
- Fill all the empty spaces with substrate bias